



Frequency Agile Ferroelectric Filters, Power Dividers, and Couplers

International Microwave Symposium 2009

R. Weigel and E. Lourandakis




Outline

- Motivation
- Tunable Passive Components
 - Ferroelectric Varactors
- Frequency Agile Filters
- Frequency Agile Power Dividers & Couplers
- Prototype Implementation & Results
- Reconfigurable Amplifier Concept
- Conclusion & Outlook





Motivation

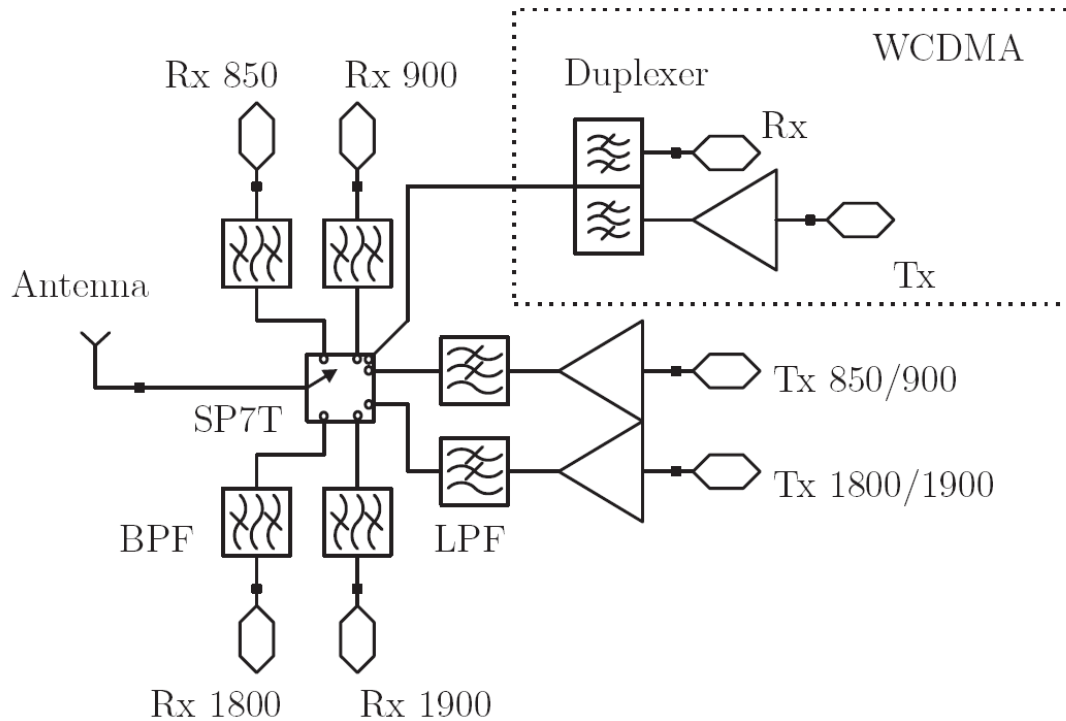


- Increasing number of communication bands
- Additional wireless services, e.g. GPS, WiMAX
- Demand for reconfigurable front-end solutions




Ferroelectric Materials - BST

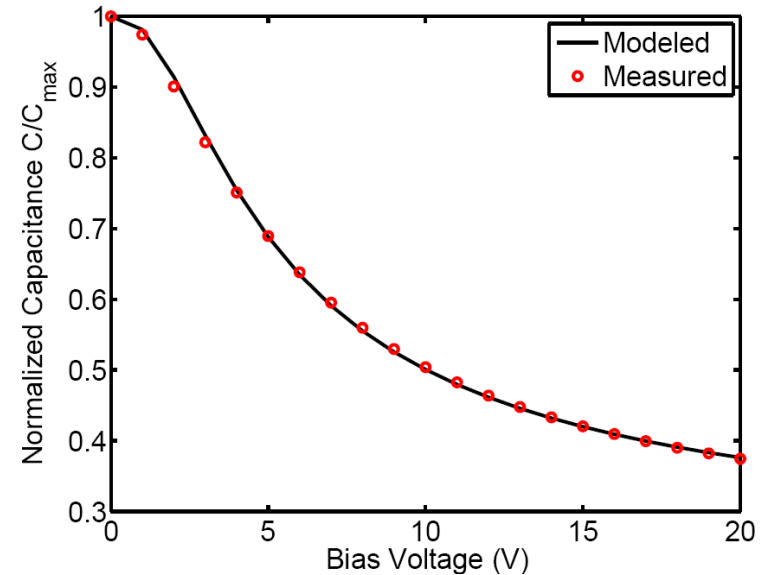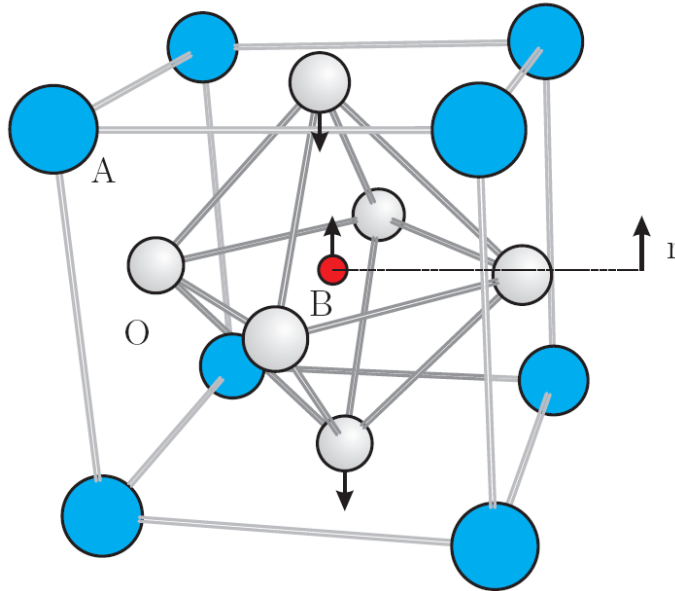

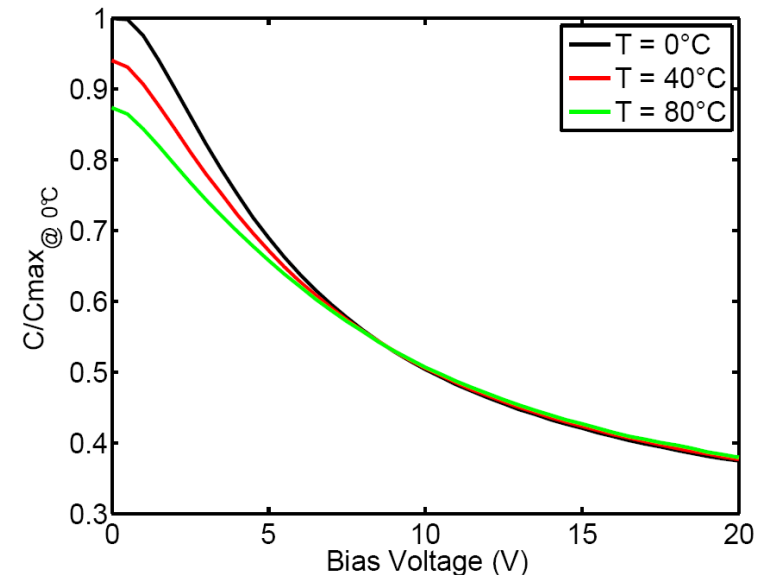- Nonlinear response to E field variation
- Tunability of 60% at 20V
- Voltage and temperature dependence
- Piezoelectric behavior





Ferroelectric Thin-Film Varactors

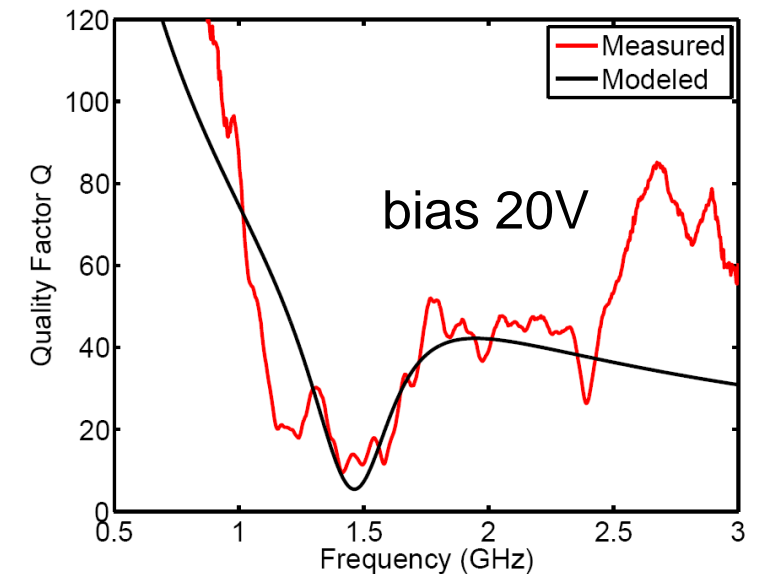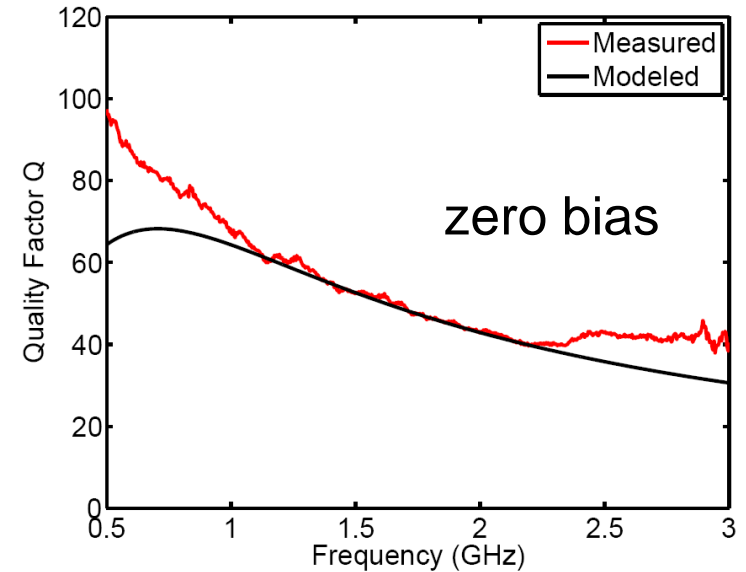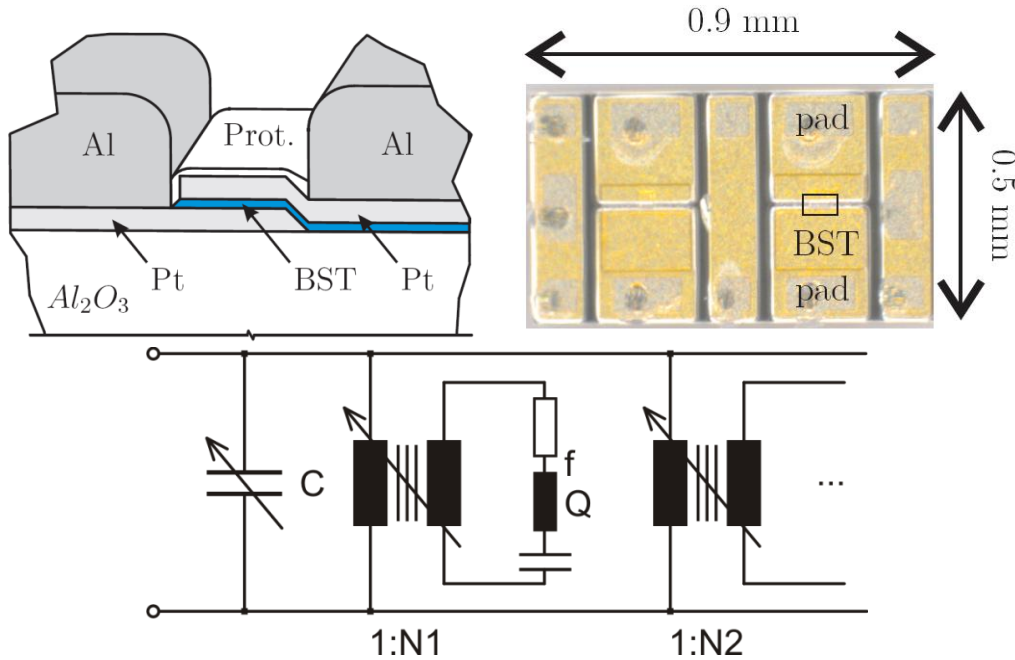



- Metal-Insulator-Metal (MIM)
- Compact dimensions
- Q around 40 @ 2 GHz
- Acoustic resonance
- ADS model available

Ferroelectric Thin-Film Varactors

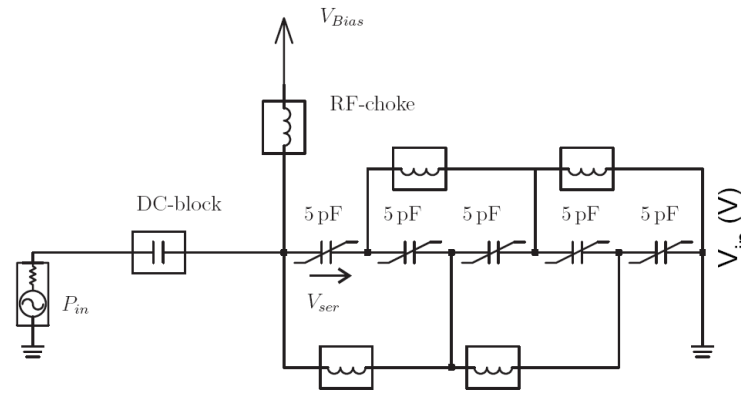
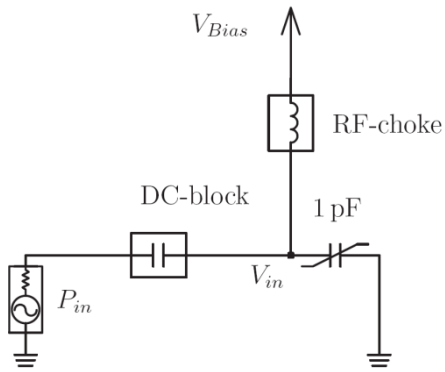


$$C_{cas} = n \times C$$

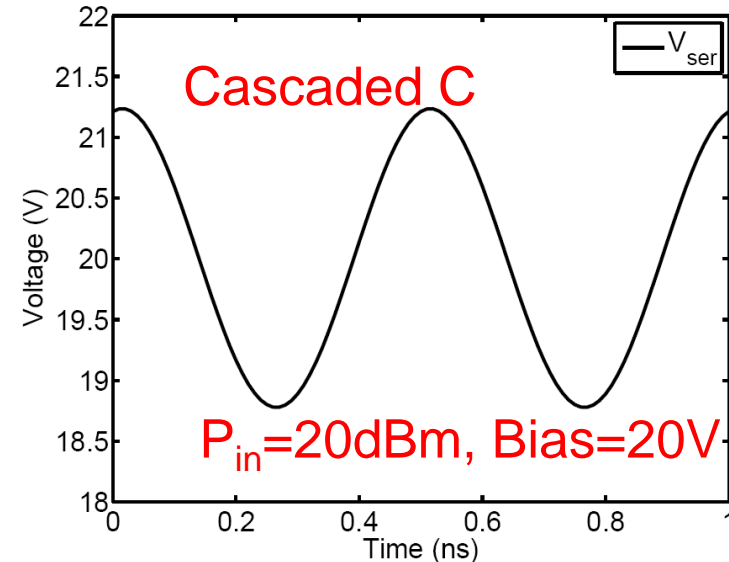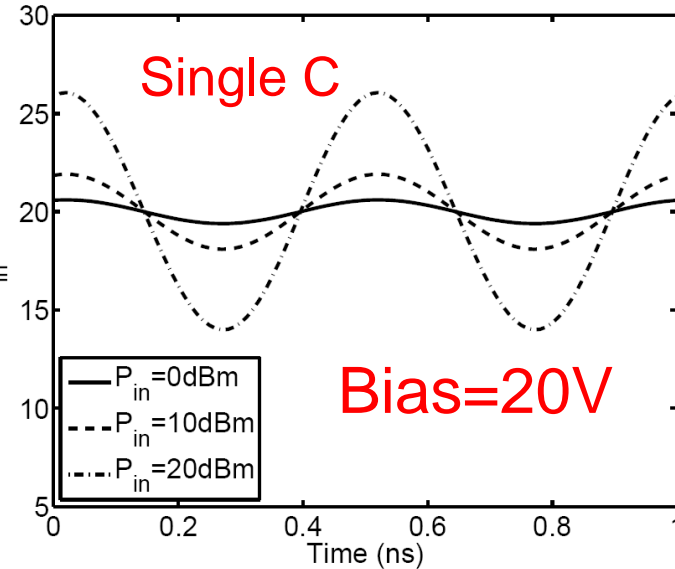- RF “modulates” capacitance
- RF swing is reduced by cascaded varactors
- Large capacitances are needed
- Possible for MIM capacitor



Analytical Filter Design – Lowpass

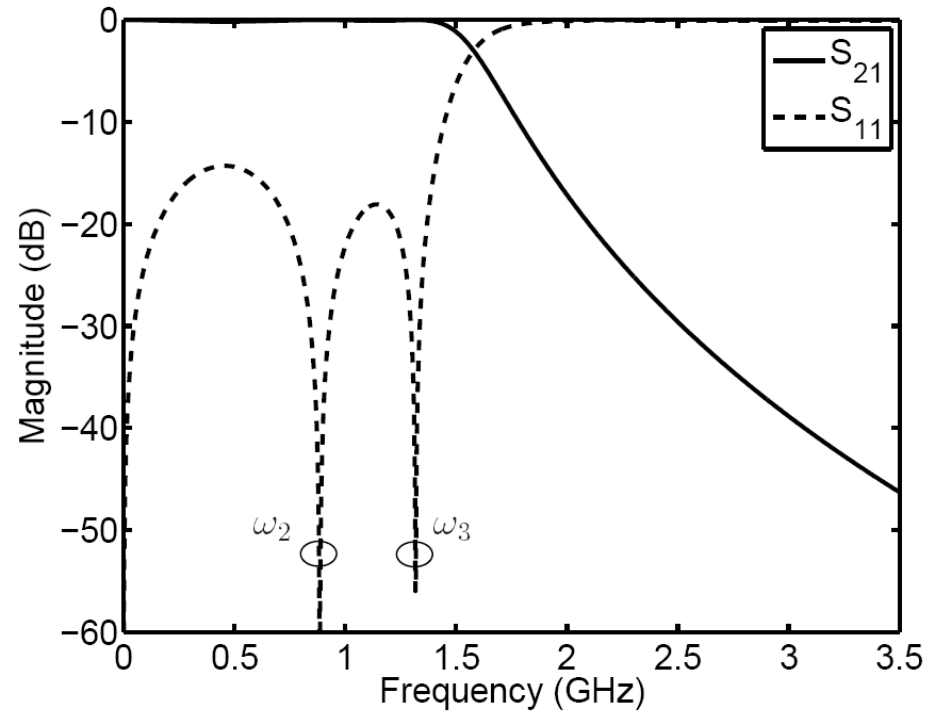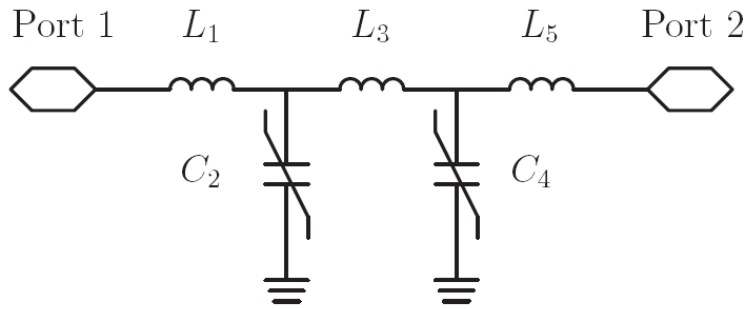

$$M_{i=1,3,5} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_i \\ 0 & 1 \end{bmatrix}$$

$$M_{j=2,4} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_j & 1 \end{bmatrix}$$

$$M_{total} = M_1 \cdot M_2 \cdot M_3 \cdot M_4 \cdot M_5$$


- Chebyshev lowpass filter
- Analytical formulas for zero locations

$$z_2 = j\omega_2 = \pm \frac{\sqrt{2CL_3(-2L_1L_3 - 2L_1^2 + Z_0^2CL_3 + \alpha)}}{2CL_1L_3}$$

$$z_3 = j\omega_3 = \pm \frac{\sqrt{2CL_3(-2L_1L_3 - 2L_1^2 + Z_0^2CL_3 - \alpha)}}{2CL_1L_3}$$

$$\alpha = \sqrt{-4L_1L_3^2Z_0^2C + 4L_1^4 + 4L_1^2L_3Z_0^2C + L_3^2Z_0^4C^2}$$


Frequency Agile Lowpass

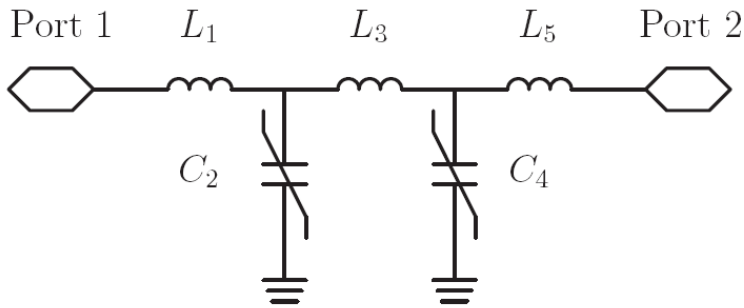

$$z_2 = j\omega_2 = \pm \frac{\sqrt{2CL_3(-2L_1L_3 - 2L_1^2 + Z_0^2CL_3 + \alpha)}}{2CL_1L_3}$$


$$z_3 = j\omega_3 = \pm \frac{\sqrt{2CL_3(-2L_1L_3 - 2L_1^2 + Z_0^2CL_3 - \alpha)}}{2CL_1L_3}$$
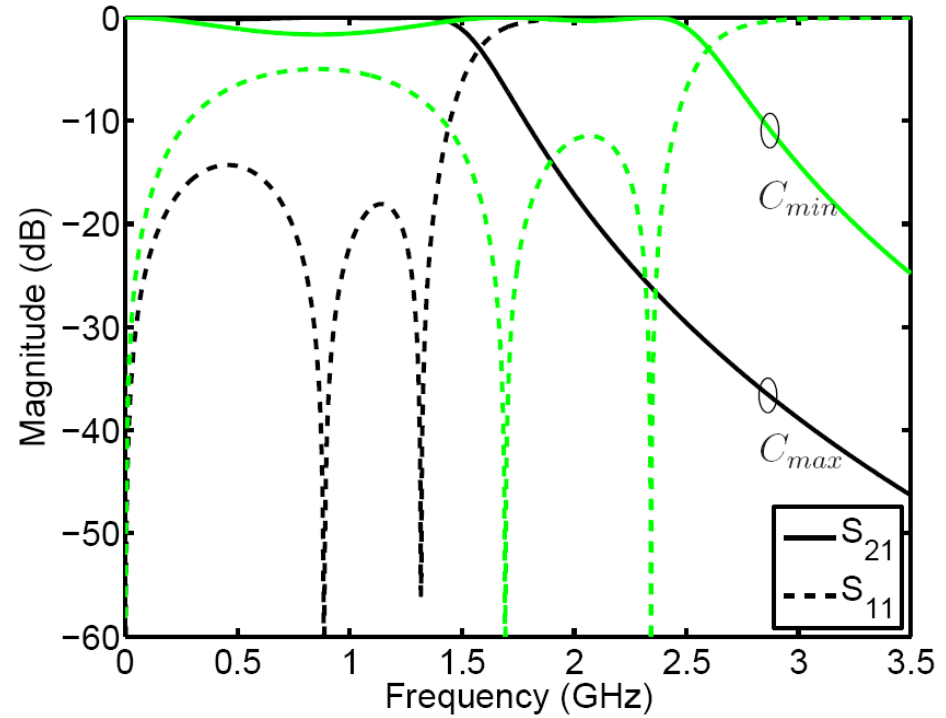
$$\alpha = \sqrt{-4L_1L_3^2Z_0^2C + 4L_1^4 + 4L_1^2L_3Z_0^2C + L_3^2Z_0^4C^2}$$



- Assumed tunability of 60% for BST varactors
- Multiband tuning from 1.5 – 2.3 GHz
- Changing C results in shifted zero locations


Analytical Filter Design – Notch Filter

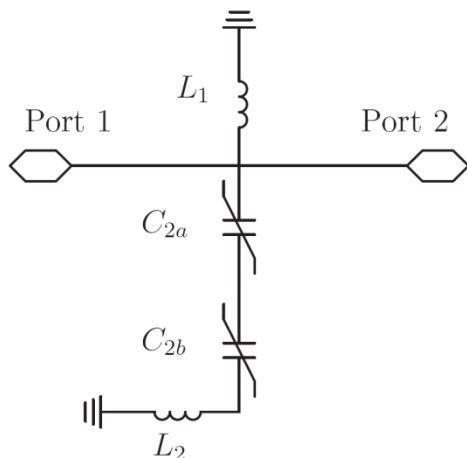

$$M_1 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix}$$

$$M_2 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix}$$

$$Y_2 = 1 / [2 / (pC) + pL_2]$$


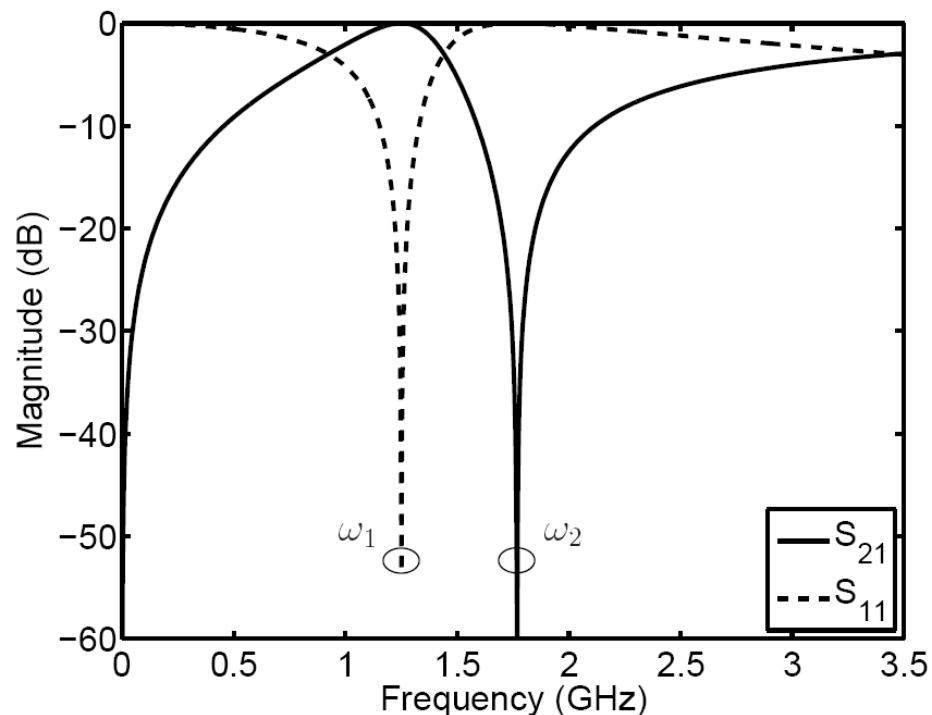


- Notch filter
- Analytical formulas for zero and pole locations

zero $z_1 = j\omega_1 = \pm \sqrt{-2 / [(L_1 + L_2)C]}$

pole $p_2 = j\omega_2 = \pm \sqrt{-2 / (L_2C)}$

Frequency Agile Notch Filter

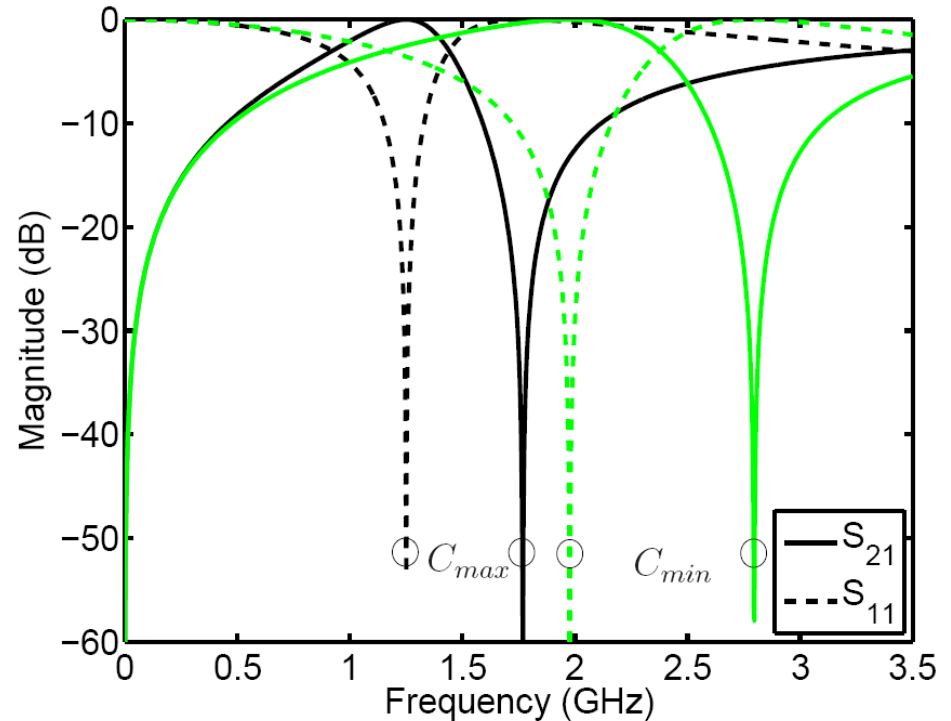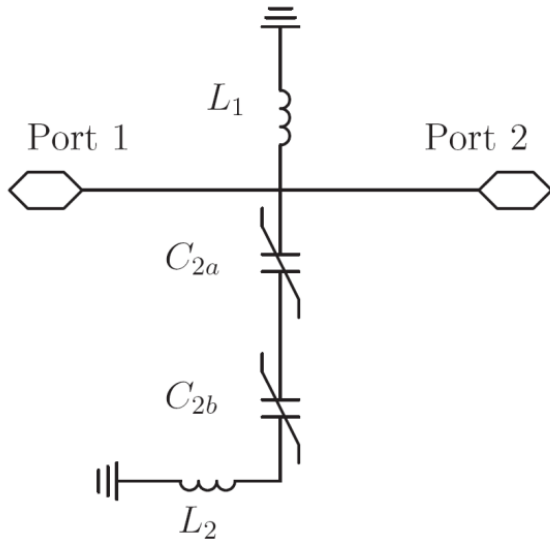


$$z_1 = j\omega_1 = \pm \sqrt{-2/[(L_1 + L_2)C]}$$


$$p_2 = j\omega_2 = \pm \sqrt{-2/(L_2C)}$$

- Assumed tunability of 60% for BST varactors
- Multiband tuning from 1.7 – 2.7 GHz
- Changing C results in shifted zeros and poles

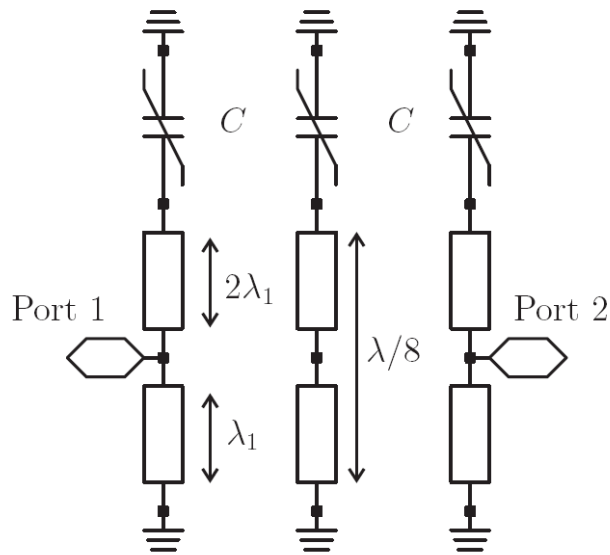
Analytical Filter Design – Comblines Filter



Tuning principle

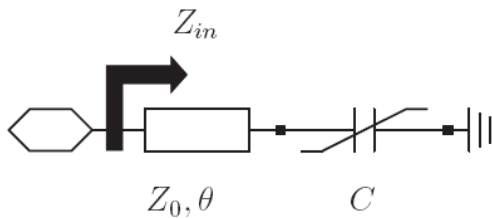

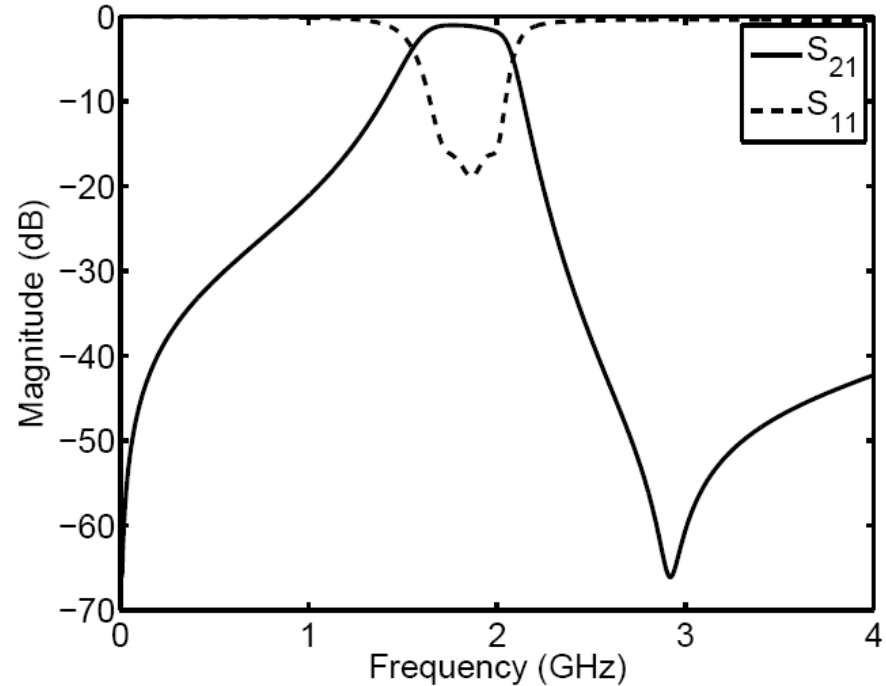
$$f = \frac{1}{2\pi C Z_0 \tan(\theta)}$$



- Compact filter dimensions
- Most suitable topology
- Asymmetric pole allocation



Modified Comblines Filter

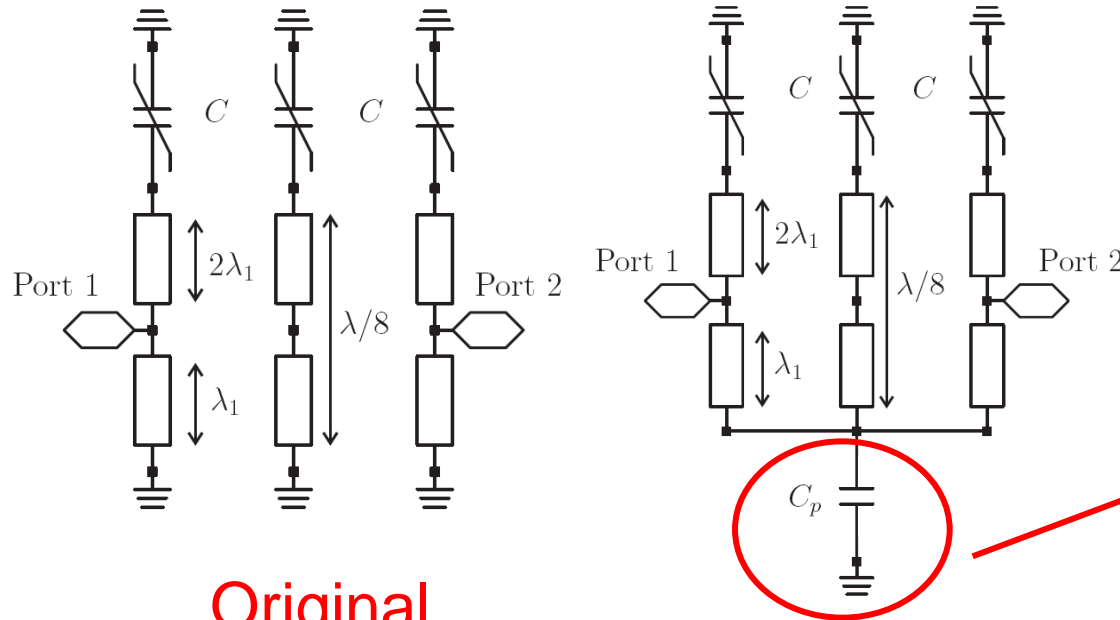

Original


Modified

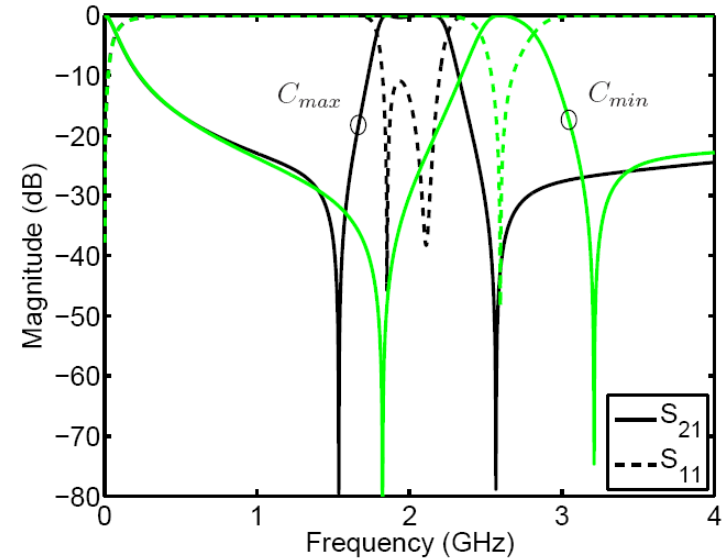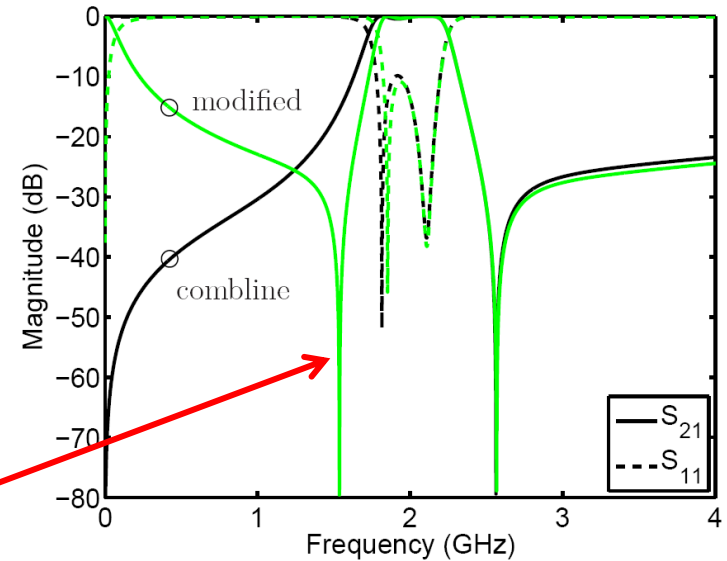- Second attenuation pole is shifted from DC to lower stopband
- Symmetric pass- to stopband transition




$\lambda/4$ Based Microwave Circuits

Wilkinson divider

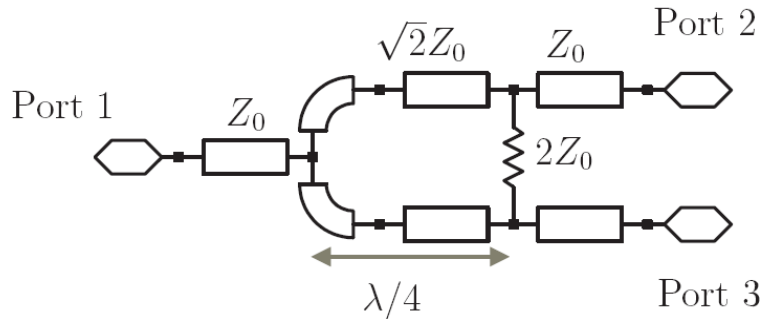



$\Delta\phi=0$ deg

Branch-Line coupler

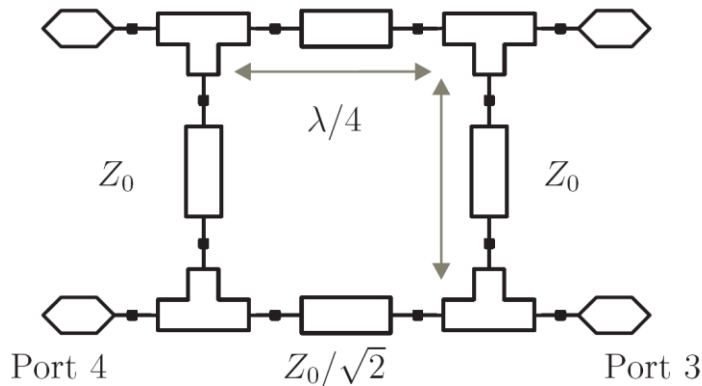


$\Delta\phi=90$ deg

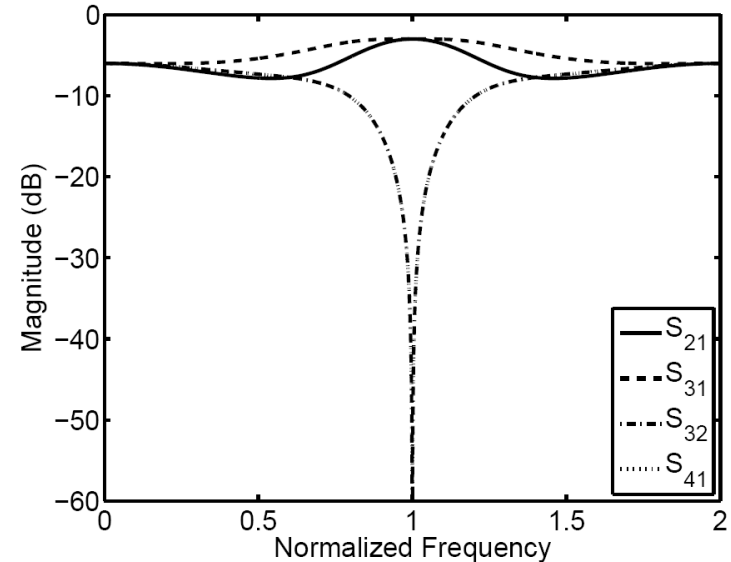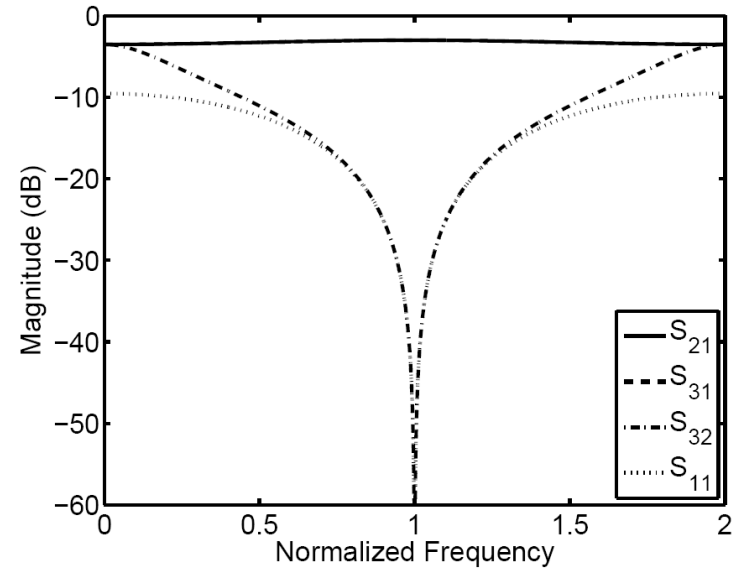- Well known 3dB couplers
- Based on $\lambda/4$ segments



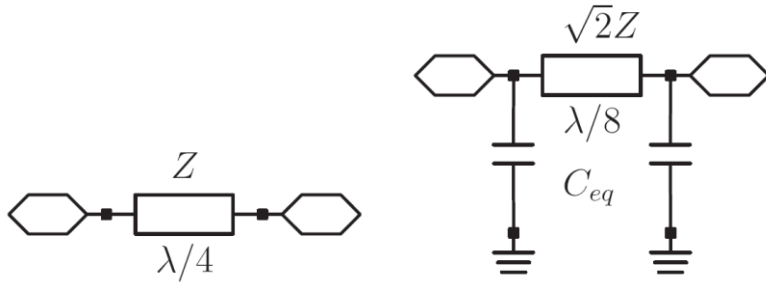Equivalent $\lambda/4$ Segments – Distributed Lowpass



Quarter-wavelength segment

$$M = \begin{bmatrix} 0 & jZ \\ j/Z & 0 \end{bmatrix} \quad (1)$$



Equivalent lowpass segment

$$\begin{bmatrix} -\omega C_{eq}Z + 1/\sqrt{2} & jZ \\ j[\omega\sqrt{2}C_{eq}Z + (1/2) - \omega^2 C_{eq}^2 Z^2]/Z & -\omega C_{eq}Z + 1/\sqrt{2} \end{bmatrix} \quad (2)$$


Comparing (1) and (2) results in

$$C_{eq} = \frac{1}{\omega\sqrt{2}Z} = \frac{1}{2\pi f\sqrt{2}Z}$$

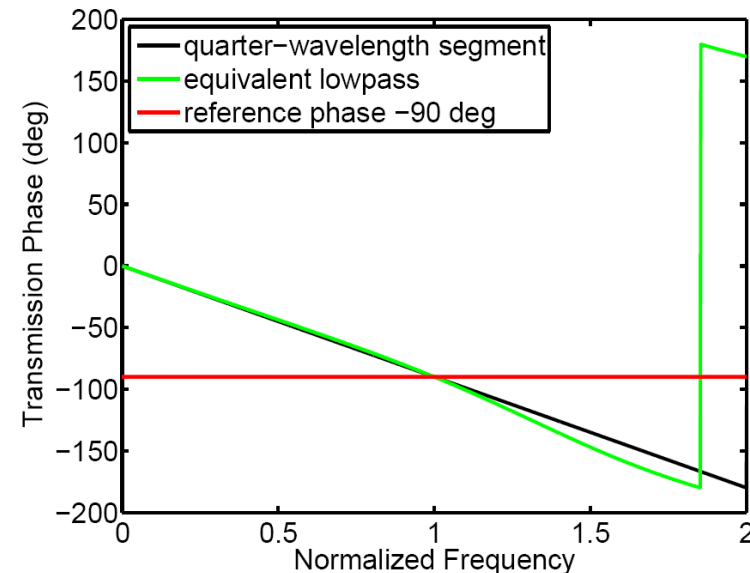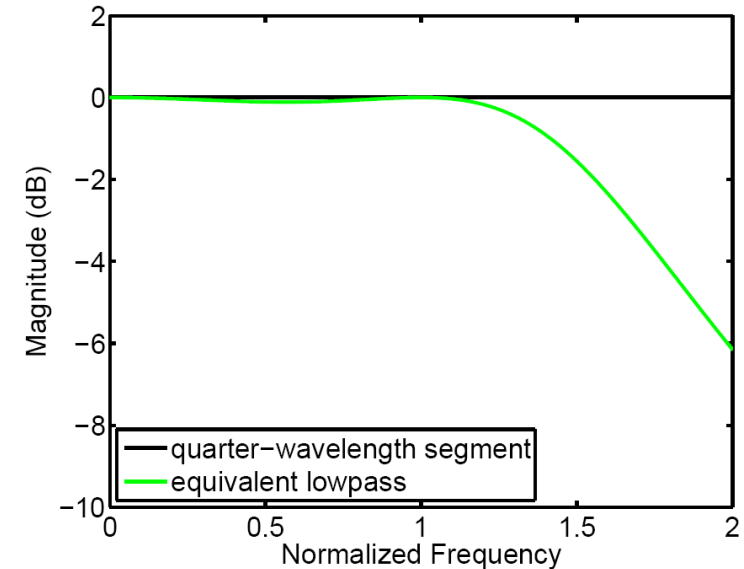- Scalable equivalent circuit
- Significant size reduction





Frequency Agile $\lambda/4$ Segments



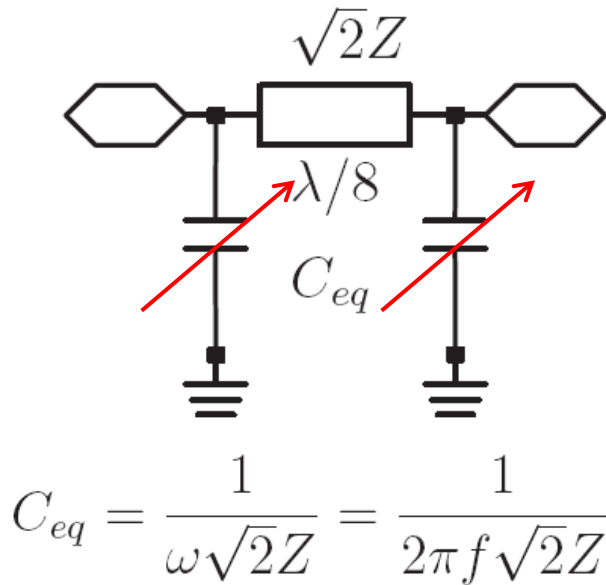


Tuning of $C_{eq} \rightarrow$
shifts resonance

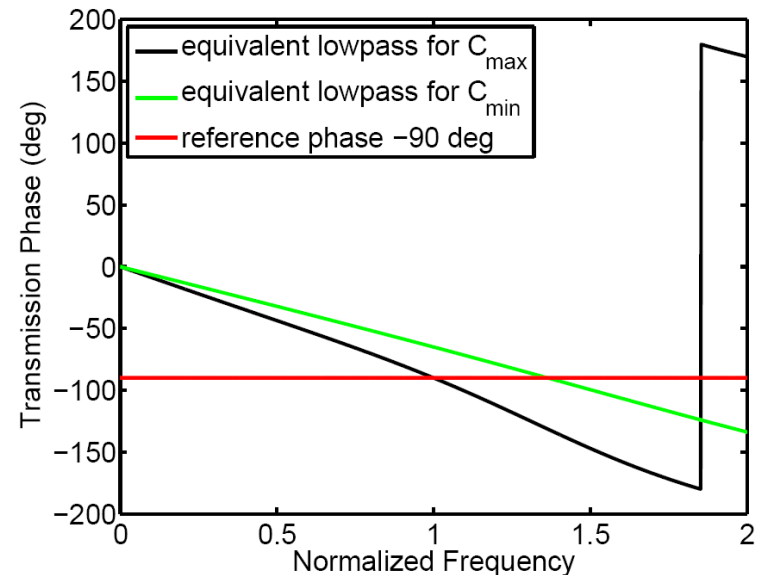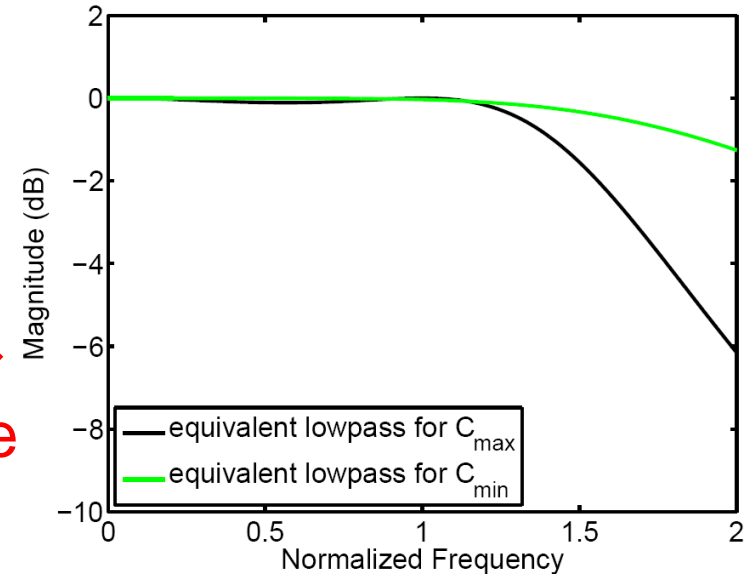- Scalable network
- Slightly detuned Z
- Perfect phase shift
- Multiband function
- Assumed tunability of 60%






Reduced Size Tunable Wilkinson Divider

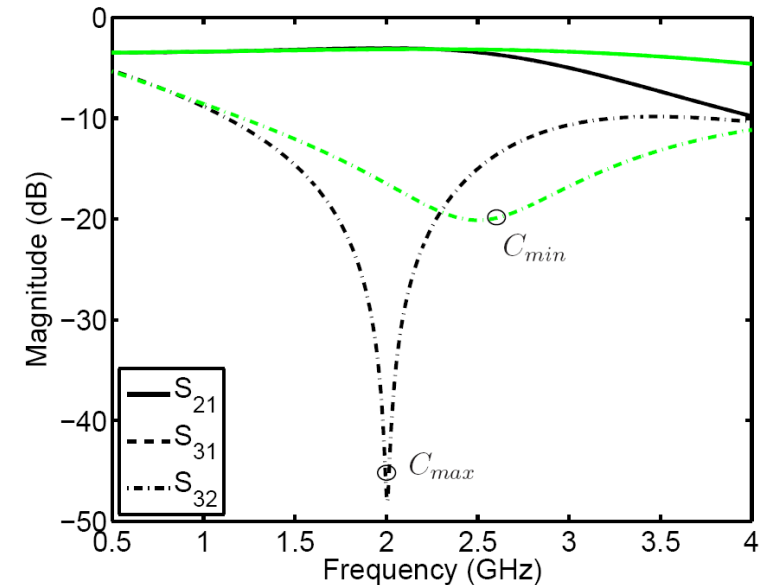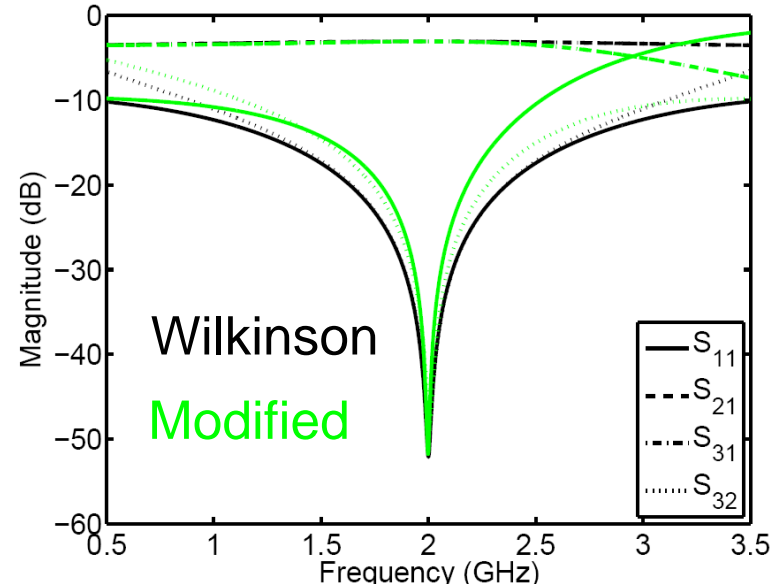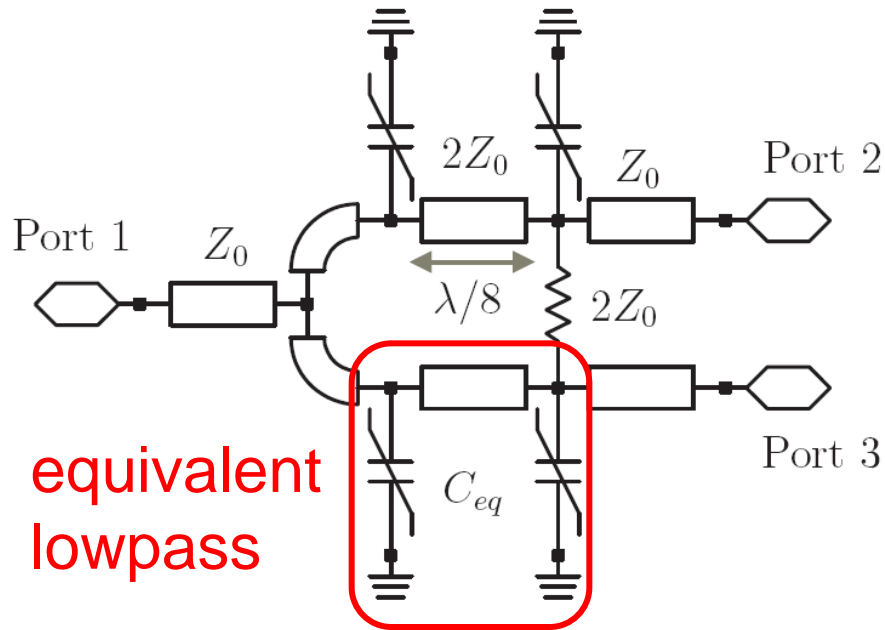

- Size reduction 50%
- Multiband tuning
- Assumed tunability 60%


Reduced Size Branch-Line Coupler

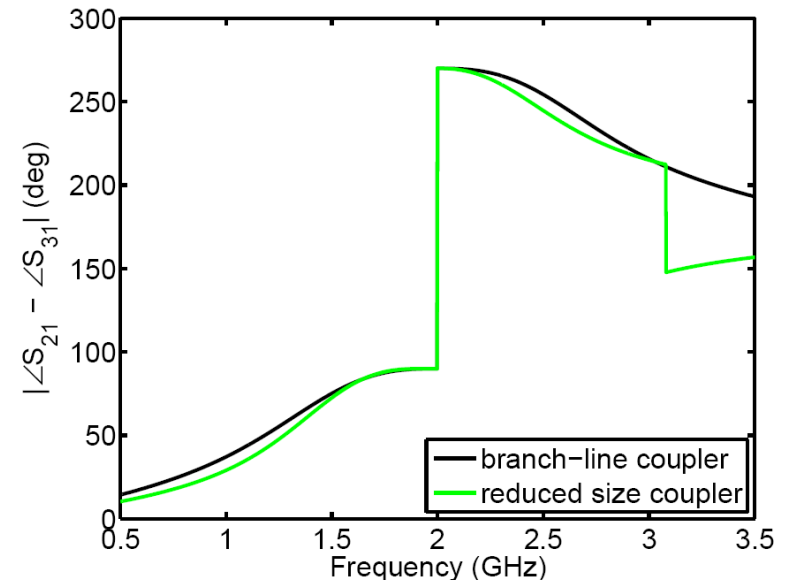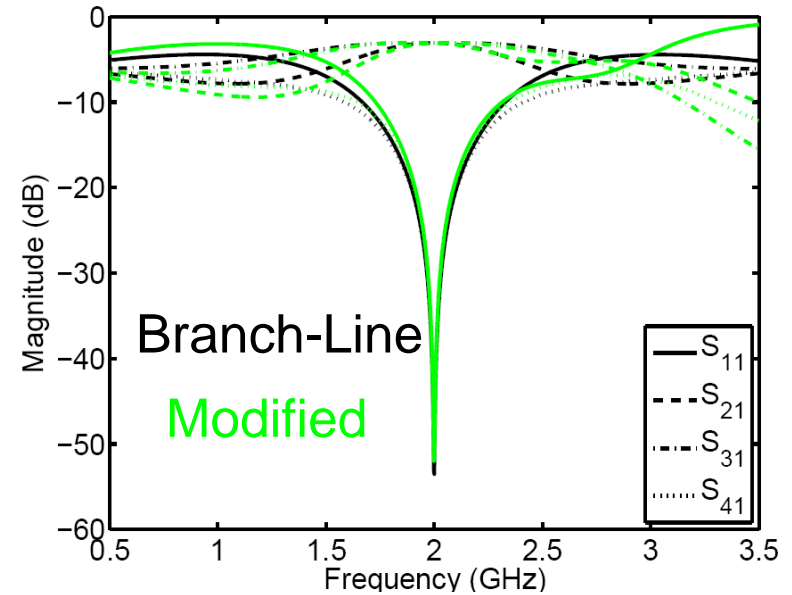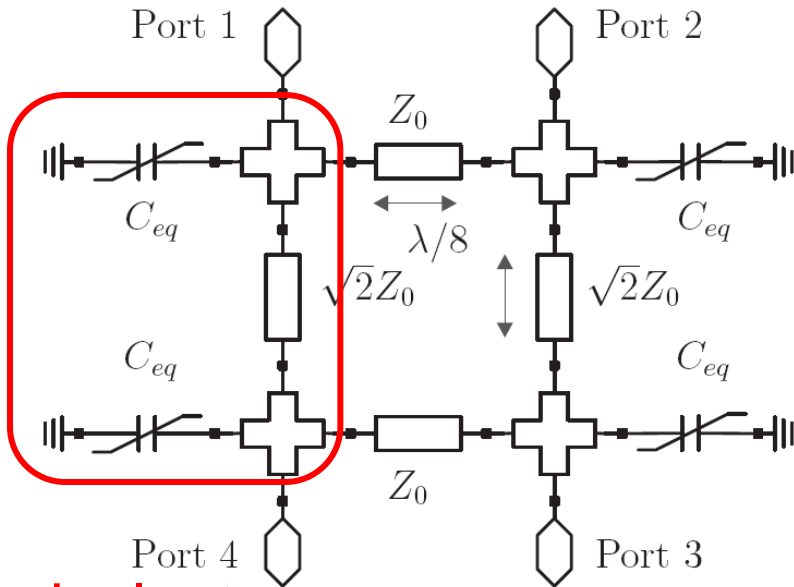

equivalent
lowpass



- Size reduction 50%
- Perfect phase match
- C_{eq} serves as shunt element for both segments

Reduced Size Tunable Branch-Line Coupler


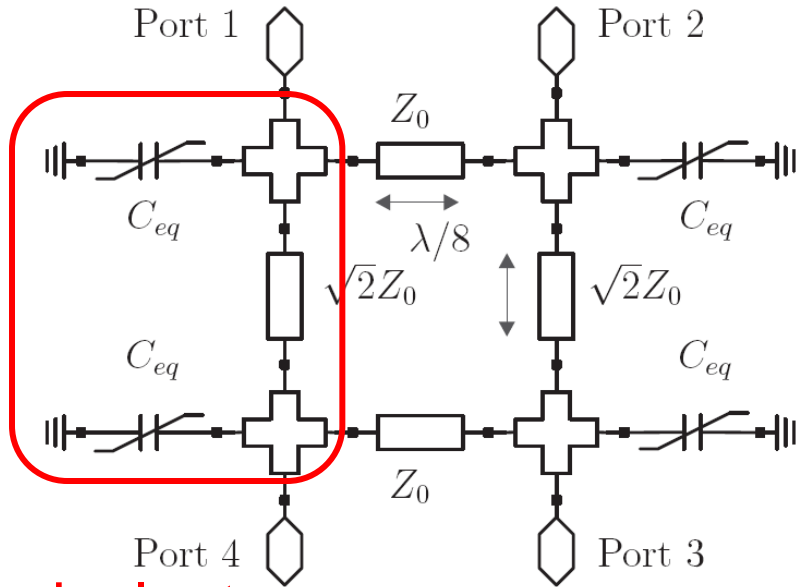


equivalent
lowpass

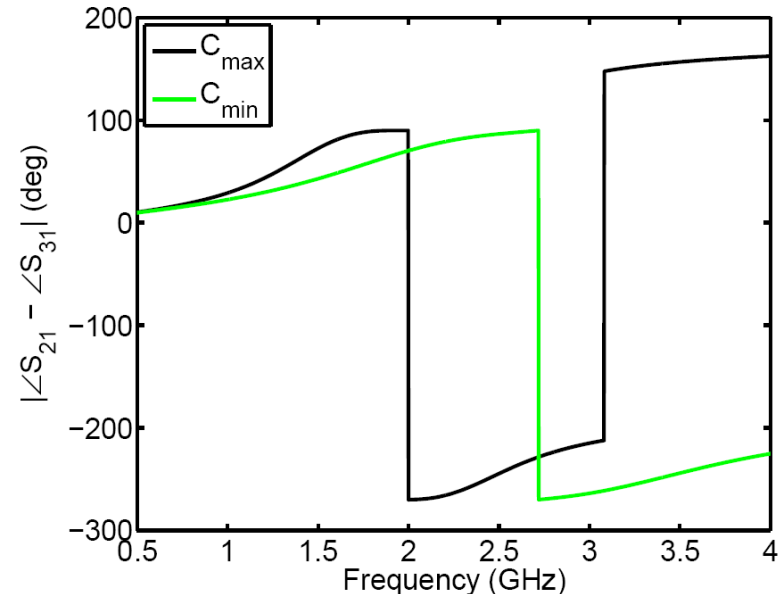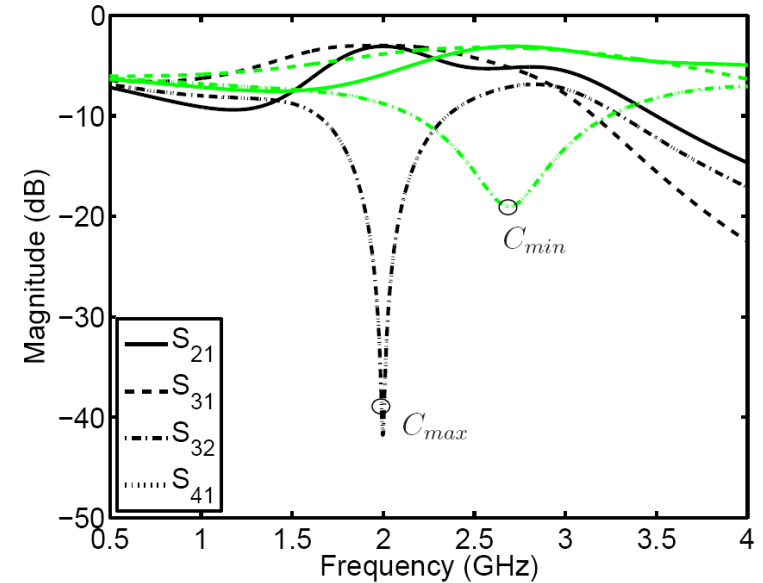- Size reduction 50%
- Perfect phase shift
- Multiband operation with tunability of 60% for C_{eq}




Prototype Implementation & Assembly

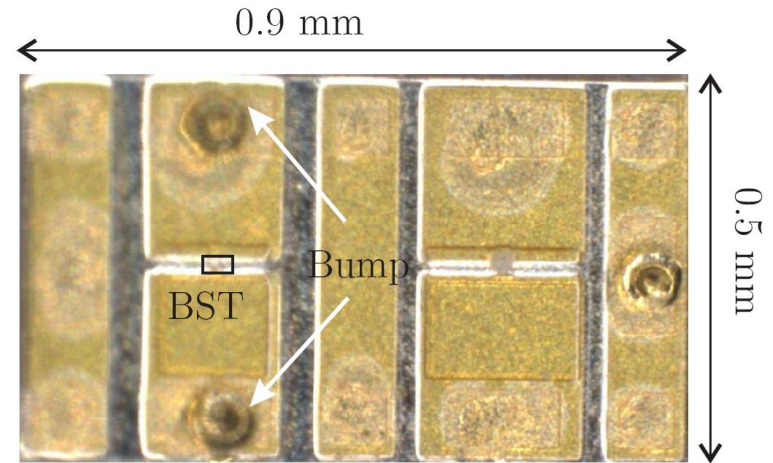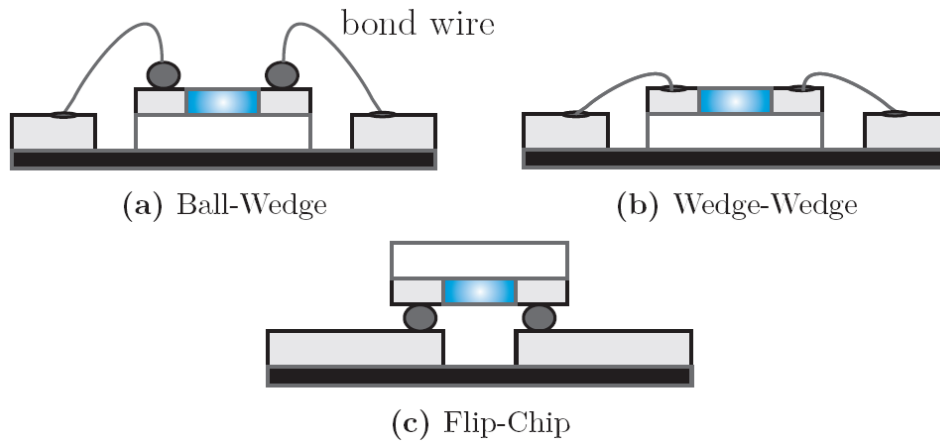



Wire inductance

$$L \approx \frac{\mu_0 l}{2\pi} \left[\ln \left(\frac{2l}{r} \right) - \frac{3}{4} \right]$$

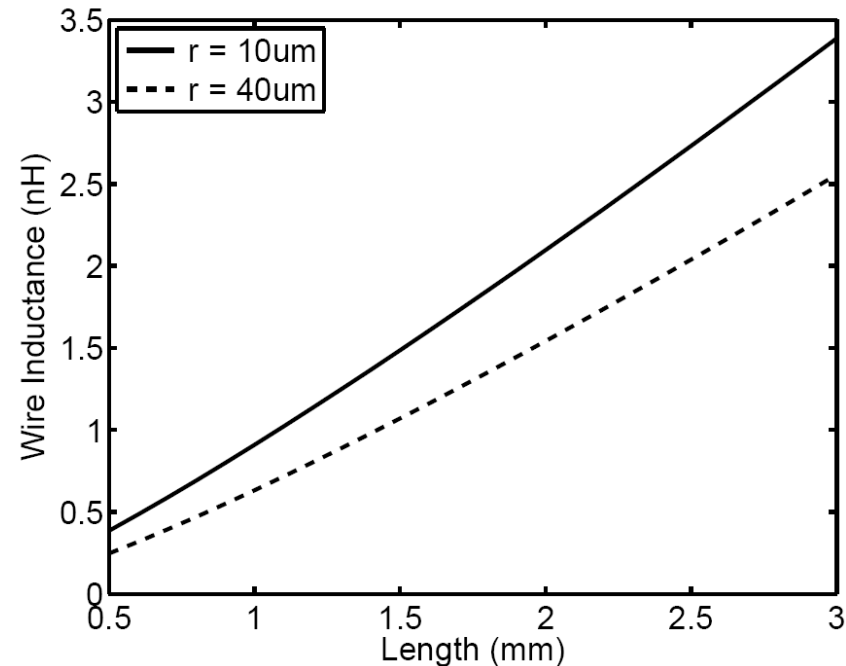
- Wire assemblies suffer from parasitics
- Flip-Chip is favorable
- Reduced footprint





Tunable Lowpass (1)

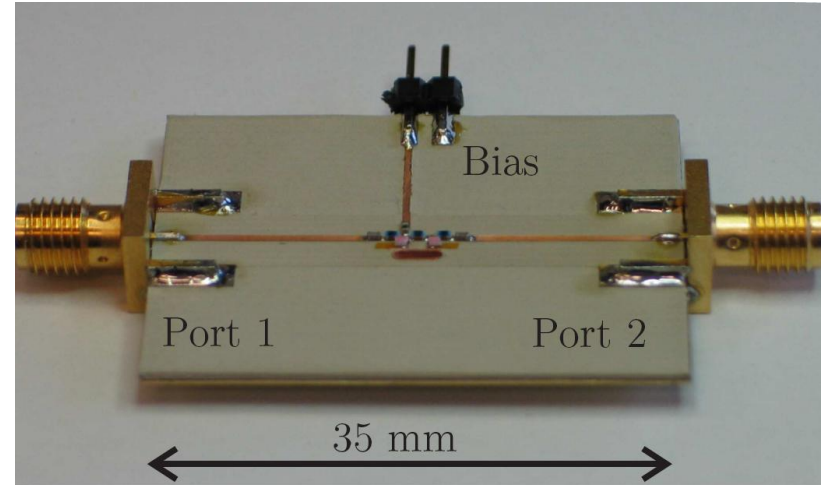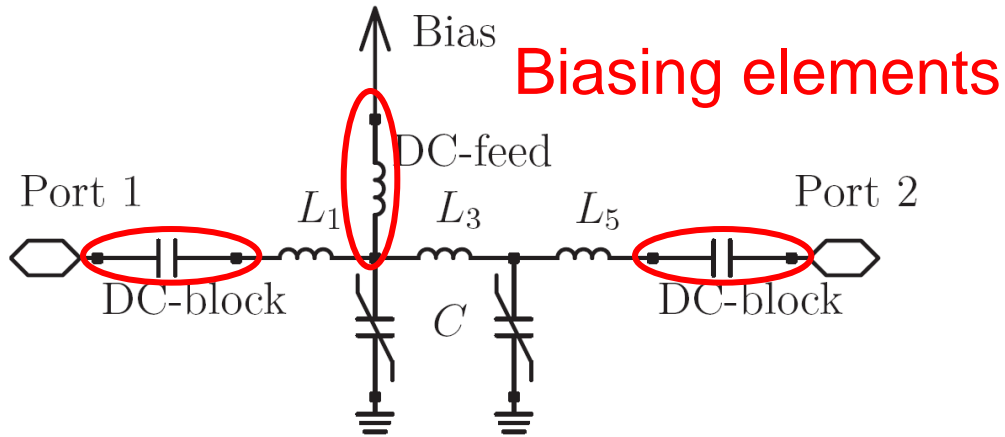

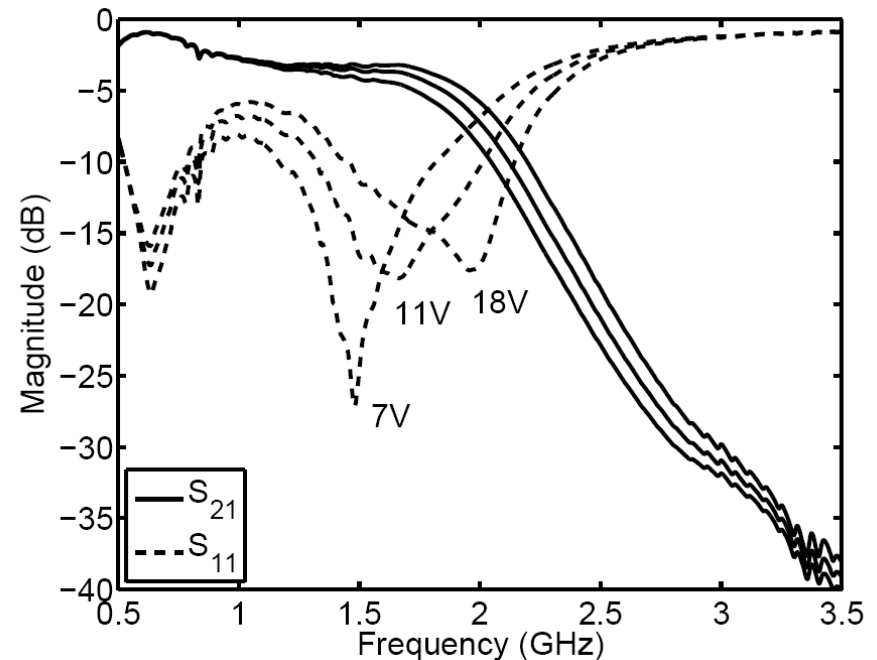
- Biasing components
- Compact dimensions
- Tuning range of 30%
- 1.5-2GHz multiband
- High losses due to moderate Q and RF isolation





Tunable Lowpass (2)

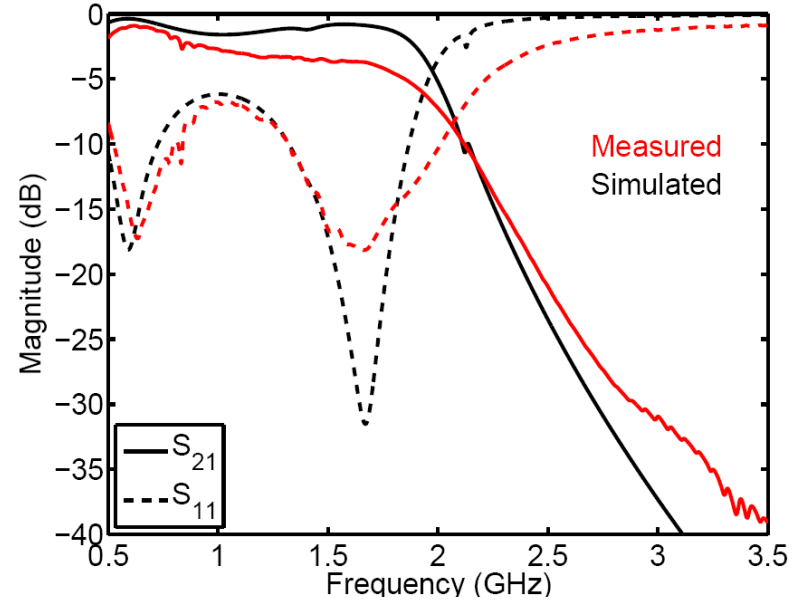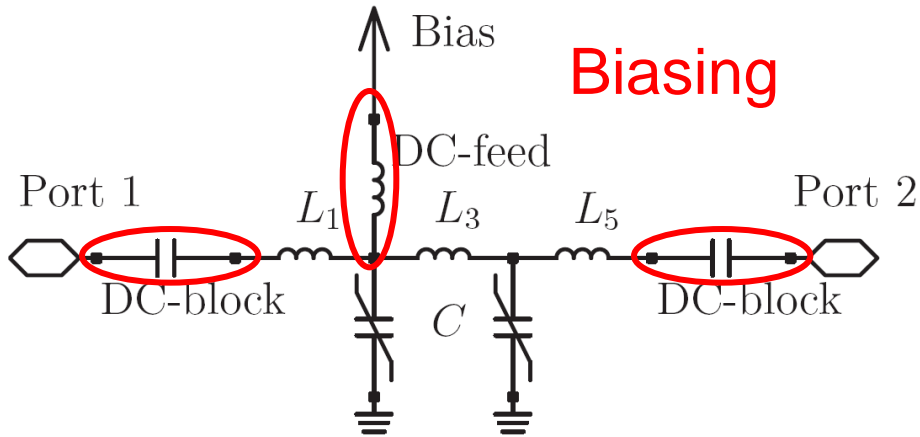

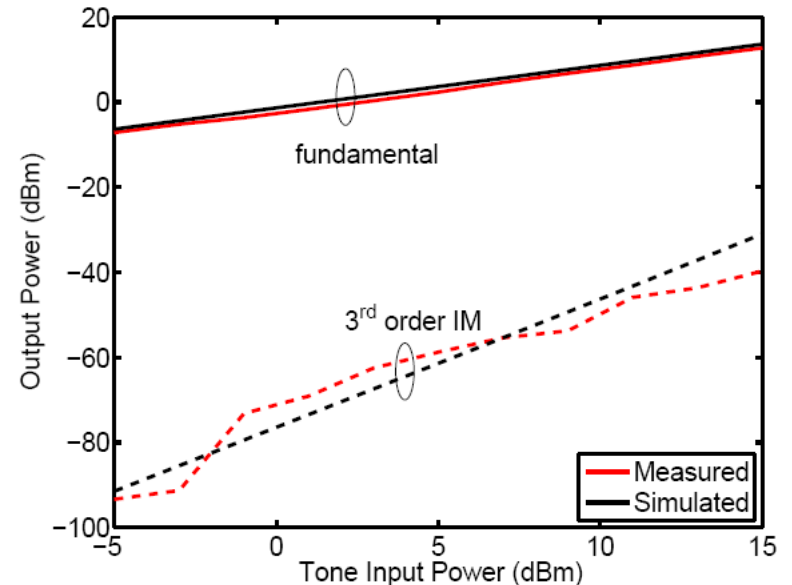
- Good agreement
- Increased loss due to varactor imbalances and prototype assembly
- Two-tone test @ 1.95GHz with $\Delta f=5\text{MHz}$ and Bias=20V




Tunable Notch Filter (1)

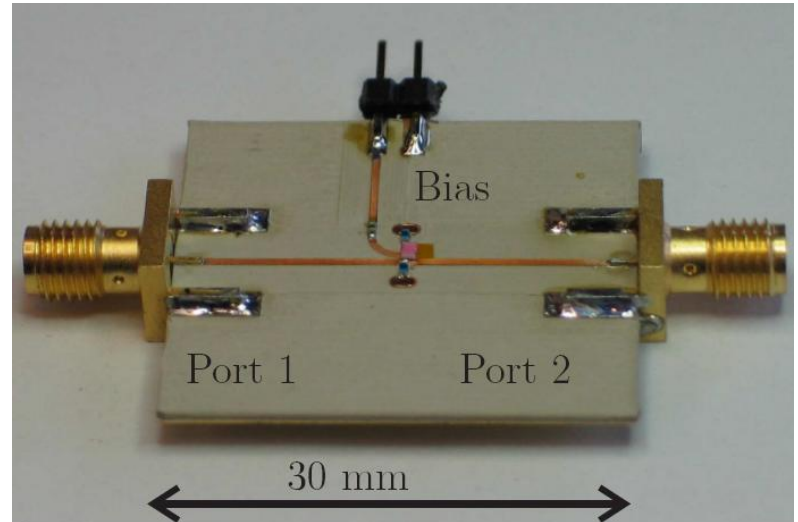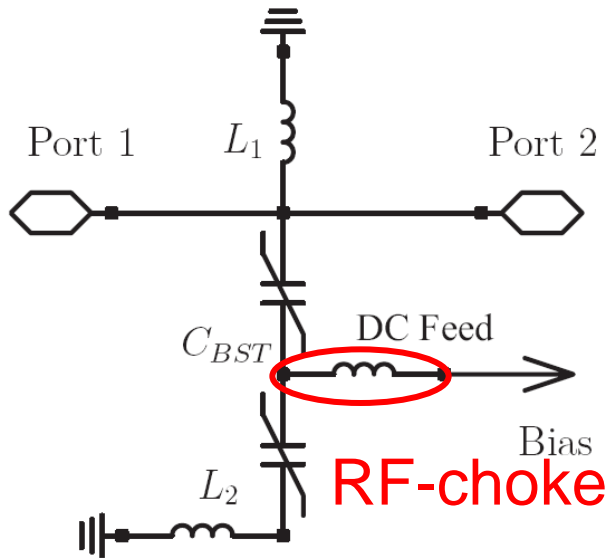


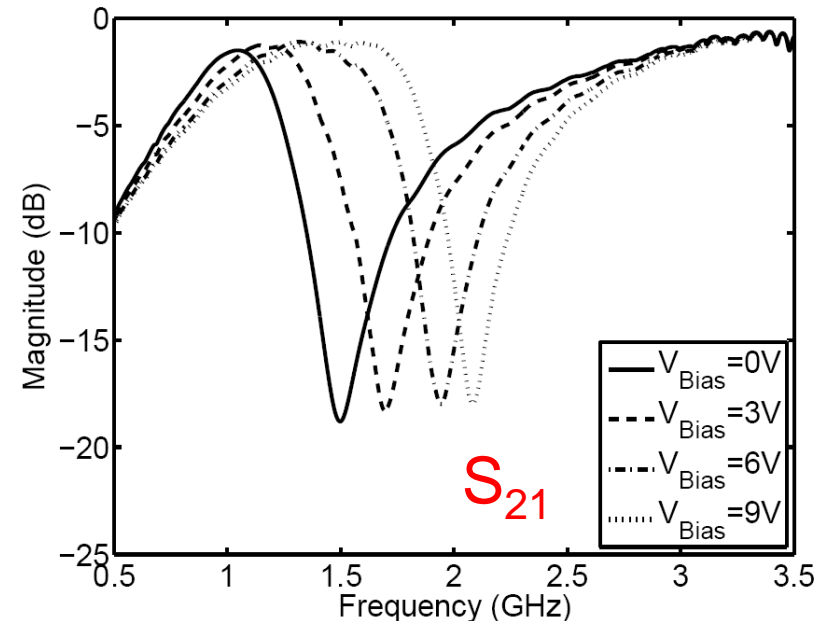
- Cascaded varactors simplify biasing
- Compact design
- Tuning 1.5-2.1GHz
- Multiband operation
- Low losses







Tunable Notch Filter (2)

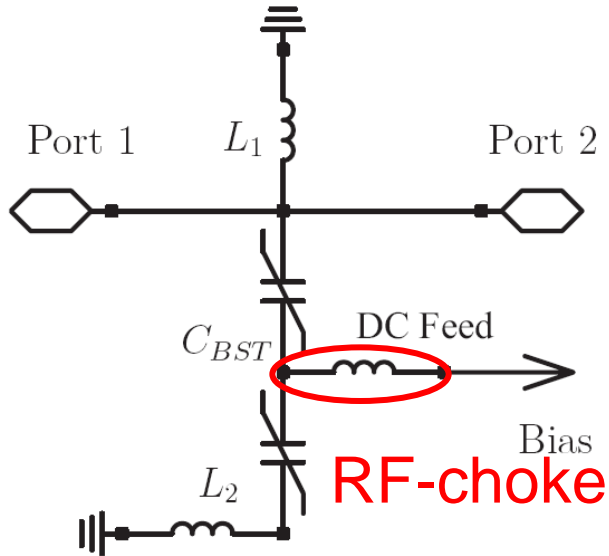

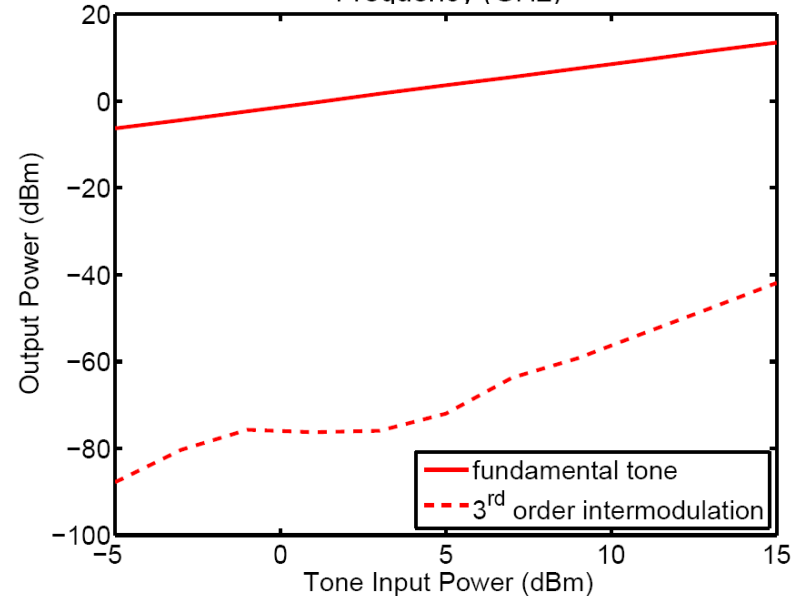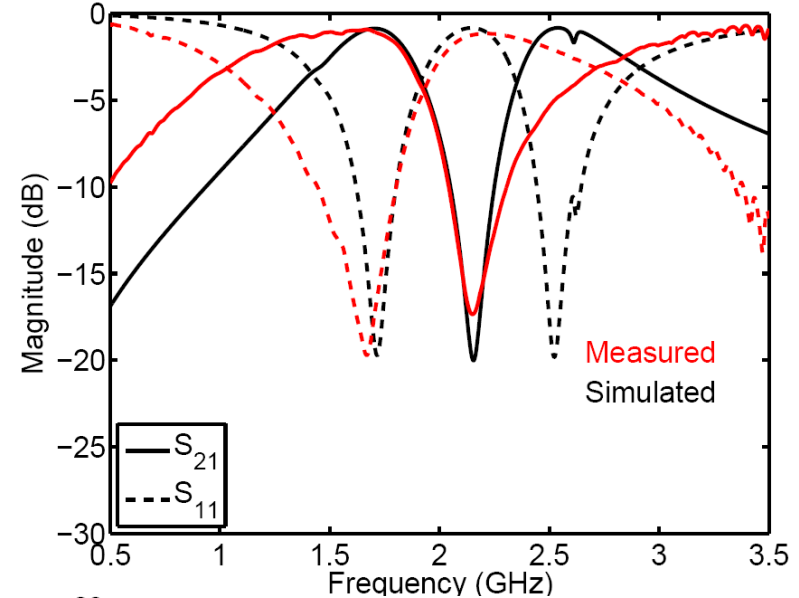- Good agreement between simulation and measurement
- Two-tone test @ 1.95GHz with $\Delta f=5\text{MHz}$ and Bias=20V





Tunable Comblines Filter (1)

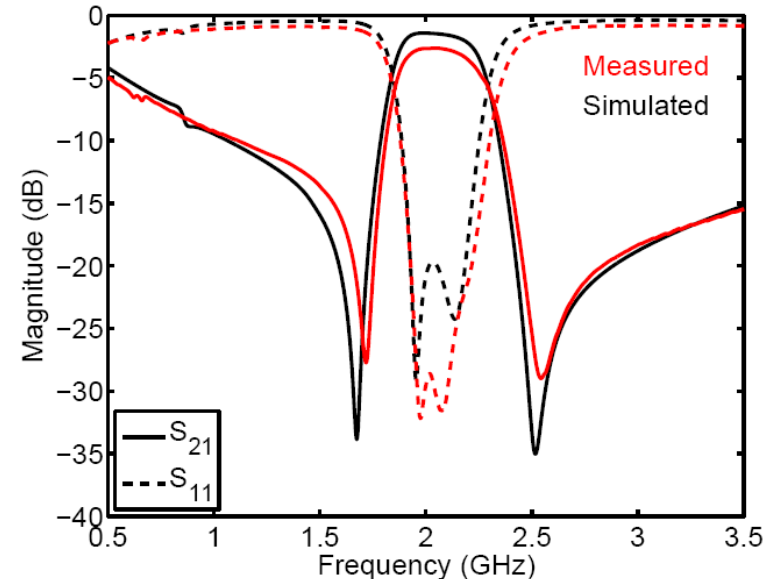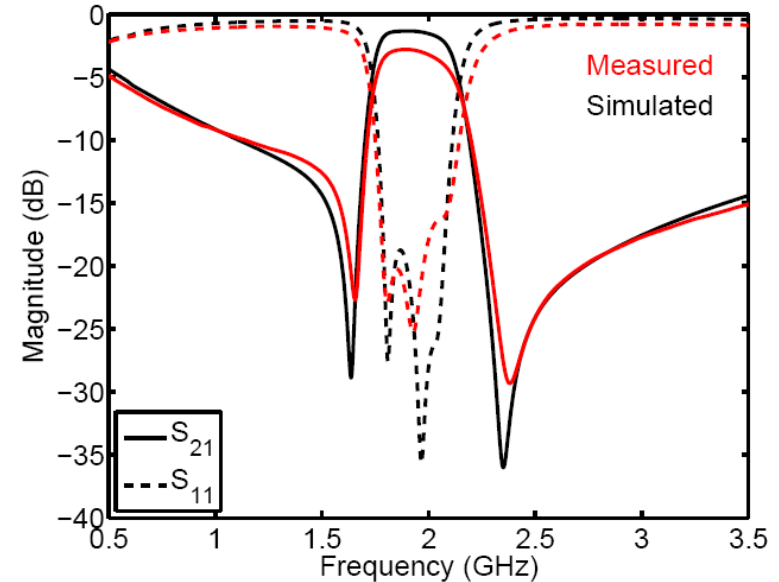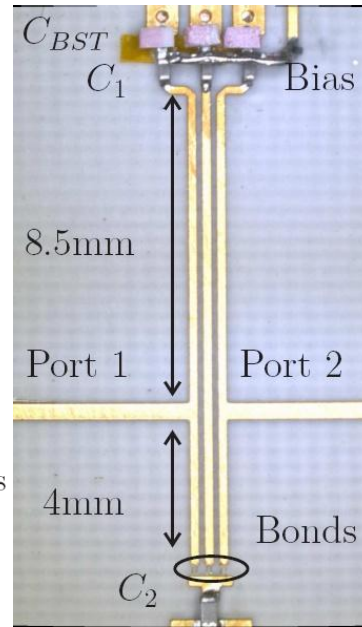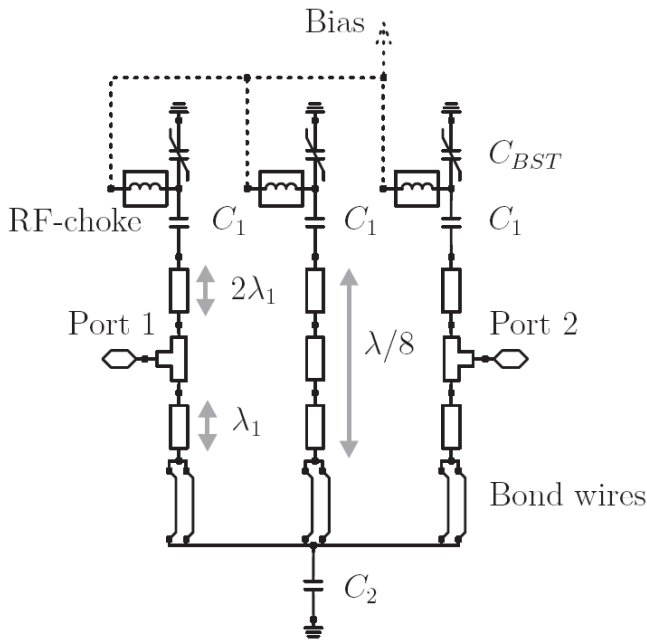


- Good agreement
- Compact dimensions
- $IL < 3\text{dB}$ and $RL > 20\text{dB}$
- Tuning 1.8-2GHz

Tunable Comblines Filter (2)




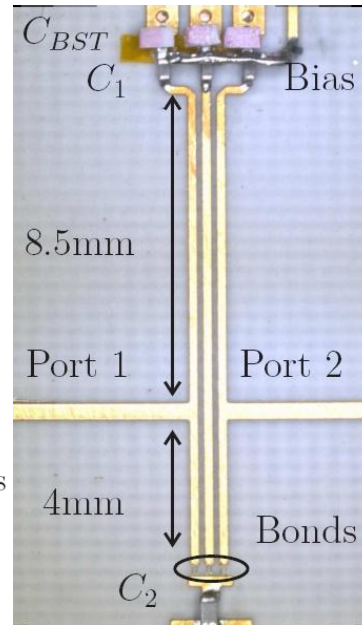
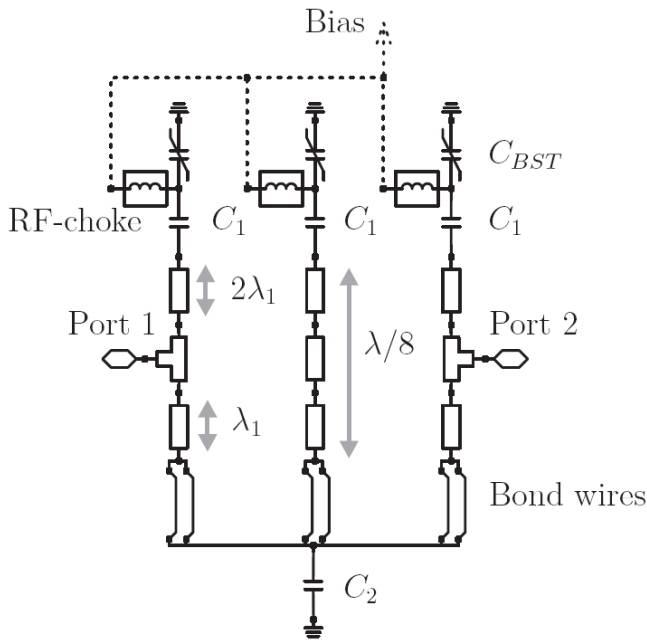


Bias (V)	f_0 (GHz)	IL (dB)	RL (dB)
0	1.85	2.8	20
5	1.90	2.7	22
10	1.97	2.6	26
15	2.02	2.6	28



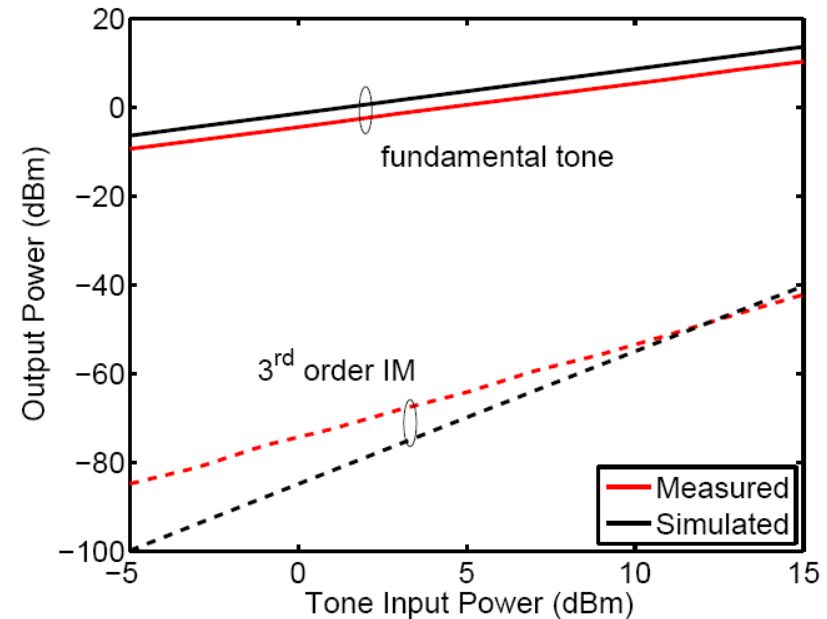


- Two-tone test @ 1.95GHz with $\Delta f=5\text{MHz}$ and Bias=5V
- Output 3rd order intercept point $\text{OIP3}=36.5\text{dBm}$

Tunable Wilkinson Divider (1)

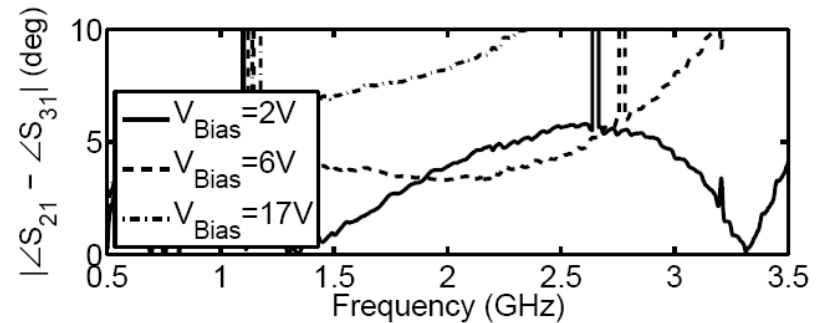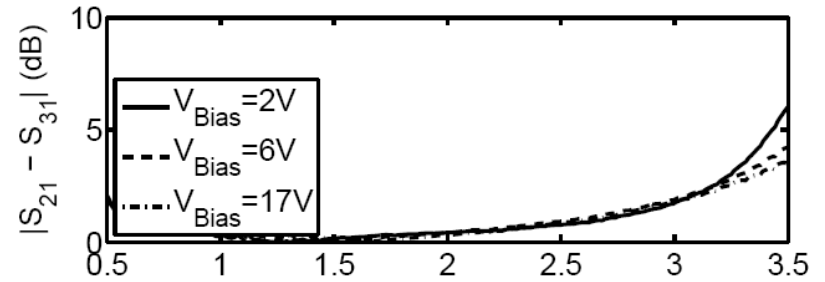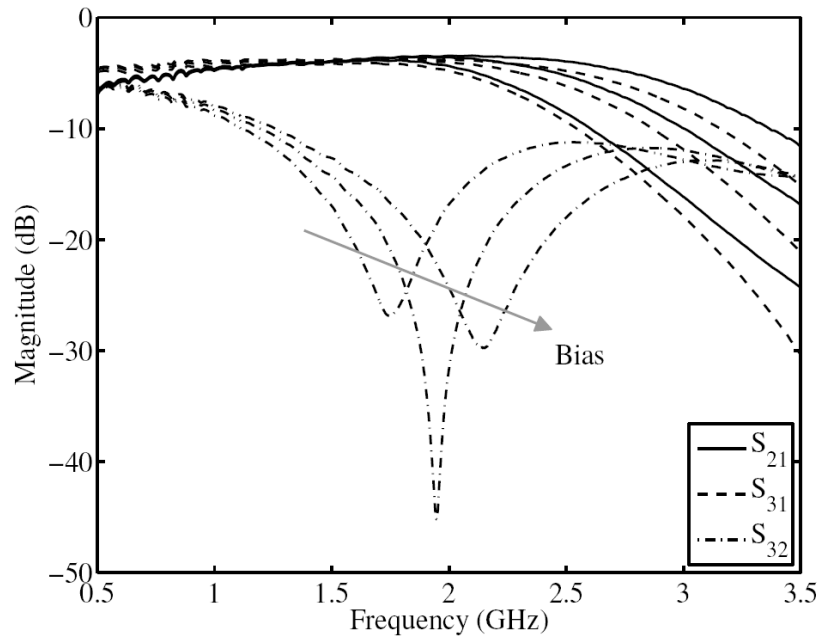
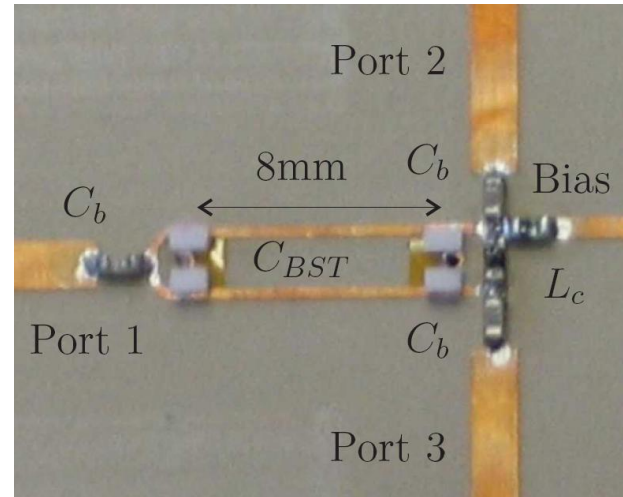
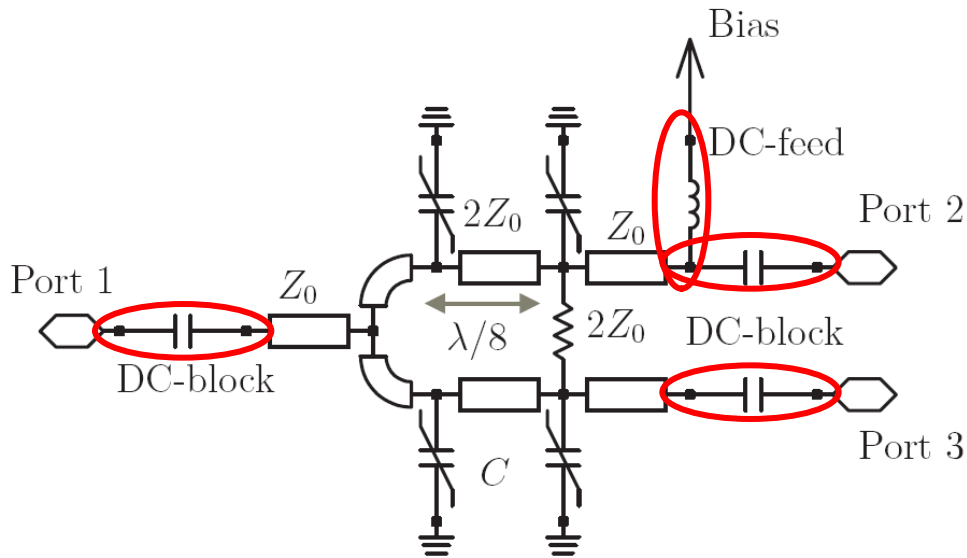


Tunable Wilkinson Divider (2)

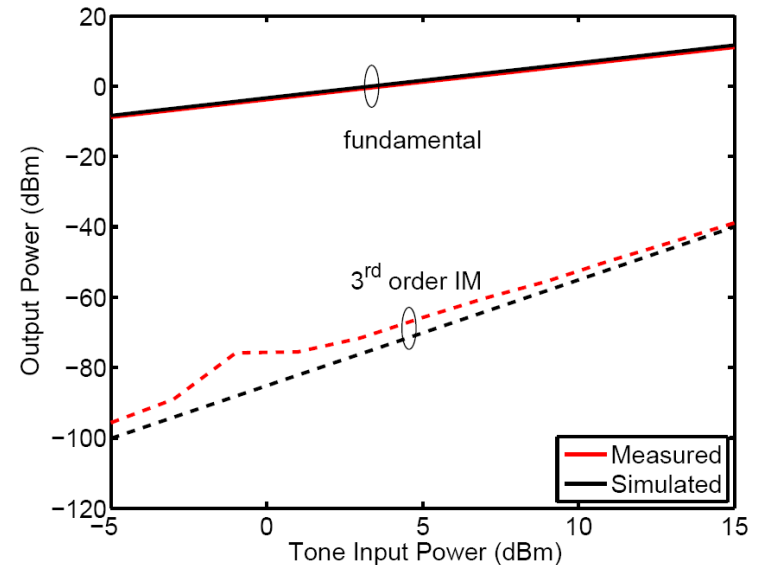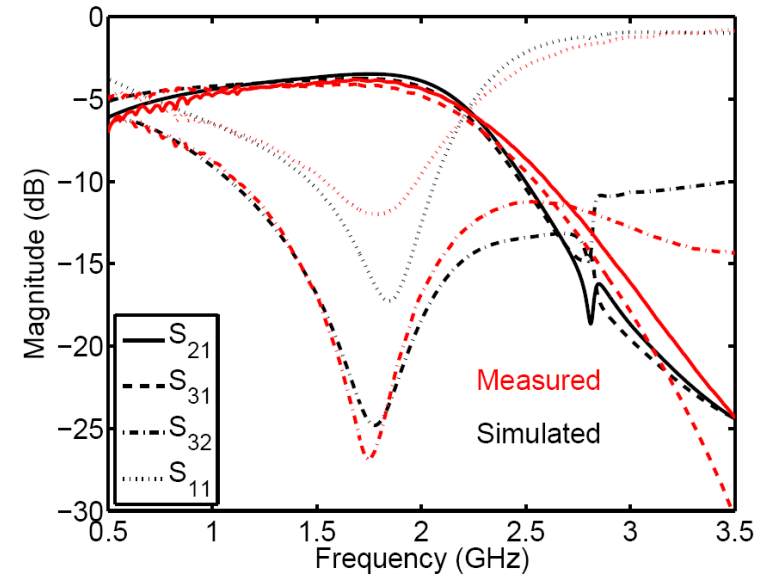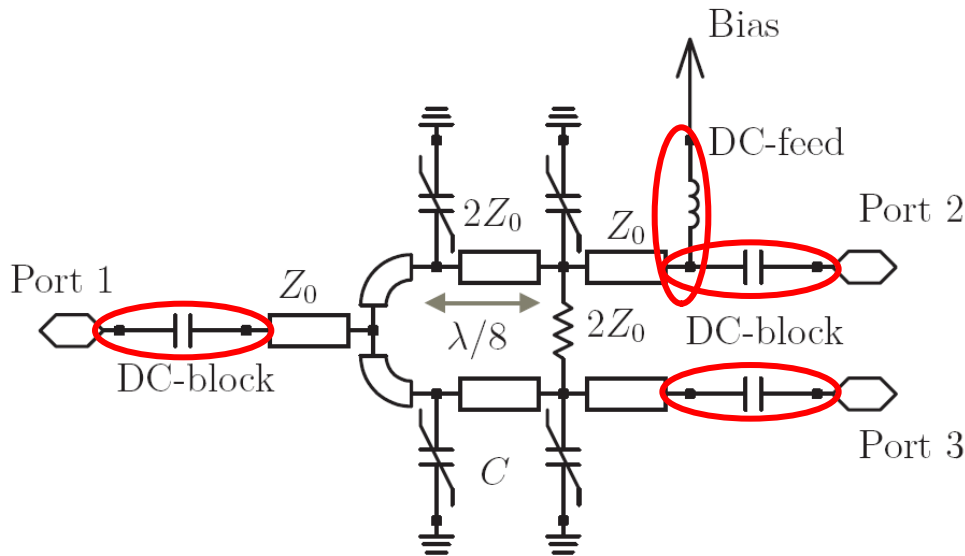






- IL < 1.2dB, Isolation > 25dB
- Size reduction 50%
- Lowpass filtering S_{21}, S_{31}
- Attenuation > 20dB at $2f_0$
- Tuning range 1.7-2.1GHz

Tunable Branch-Line Coupler (1)

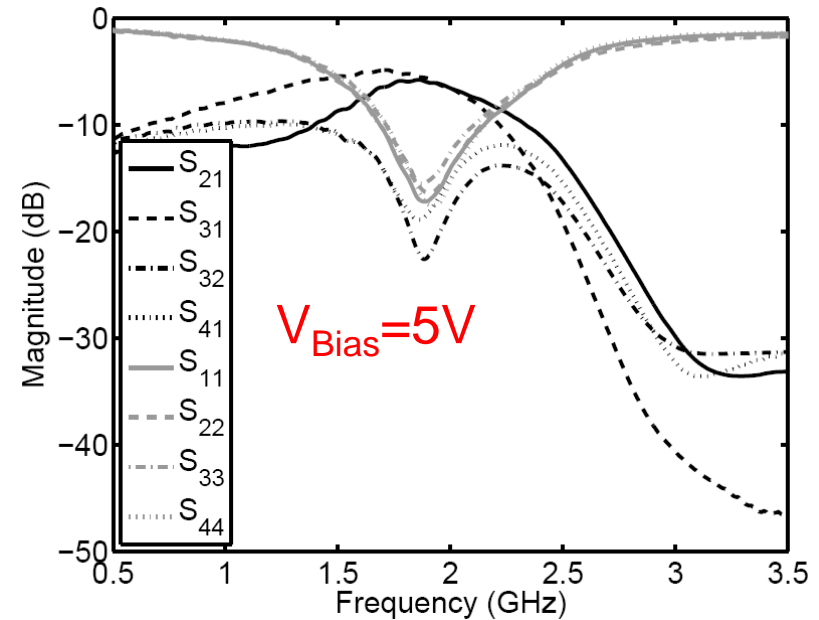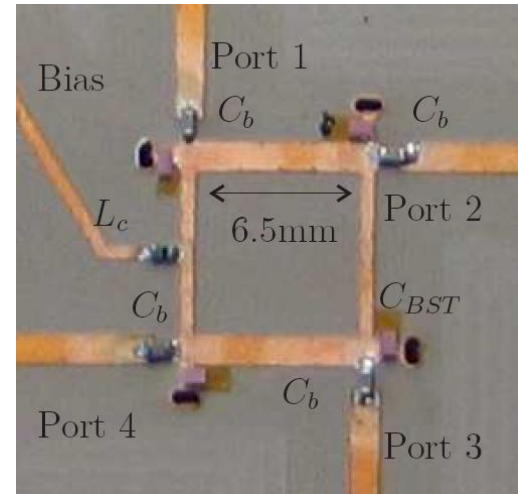
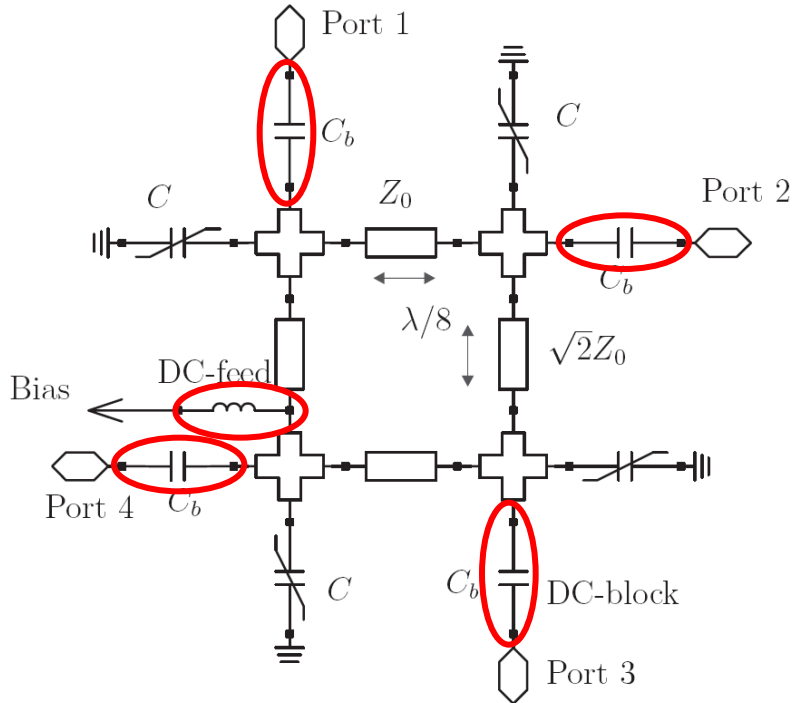


- Size reduction 50%
- Lowpass filtering at all transmission paths
- Attenuation $> 30\text{dB}$ at second harmonic


Tunable Branch-Line Coupler (2)

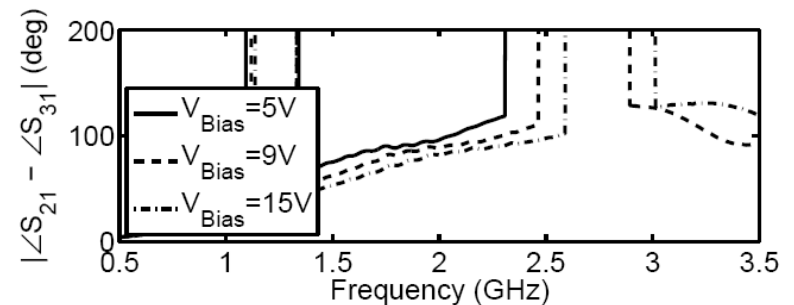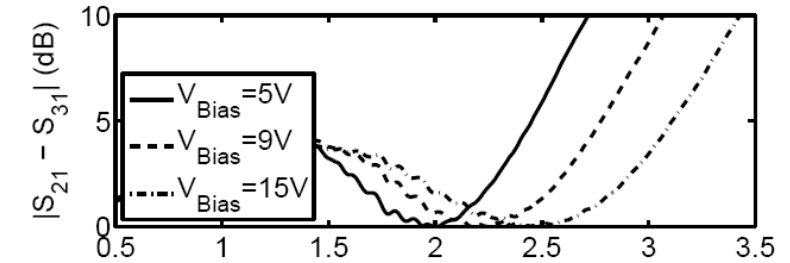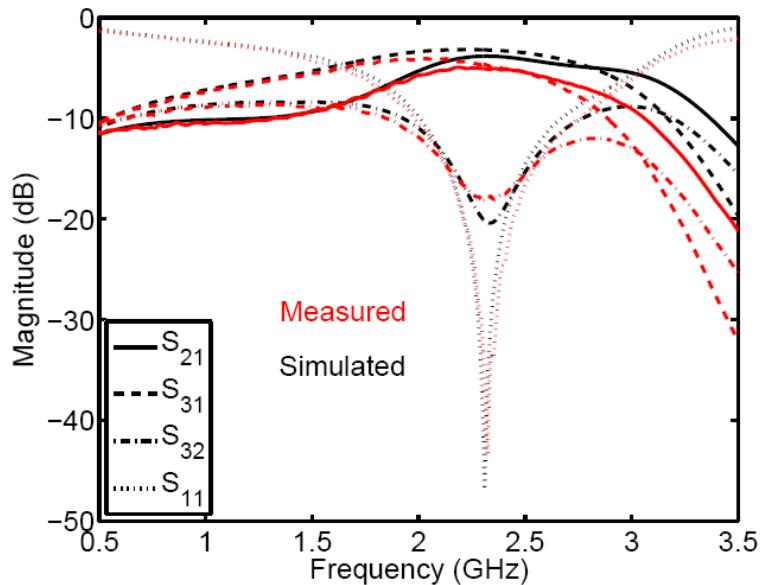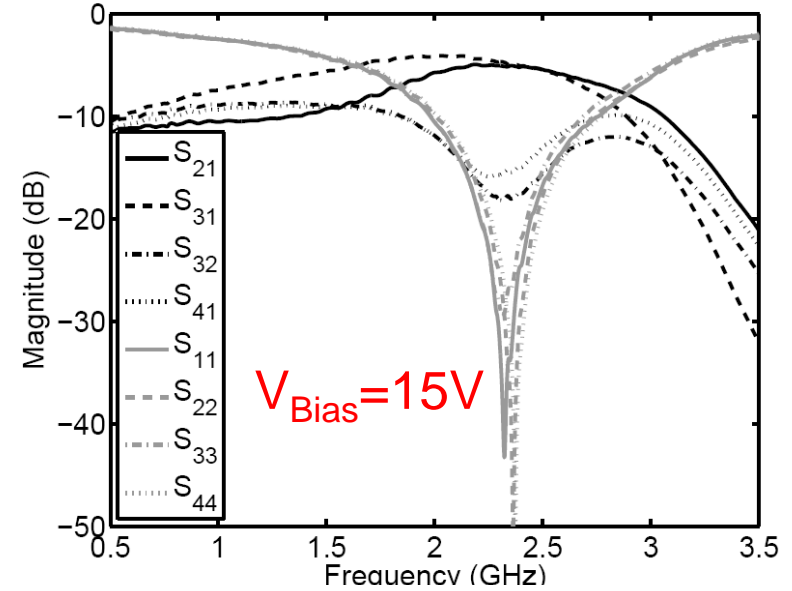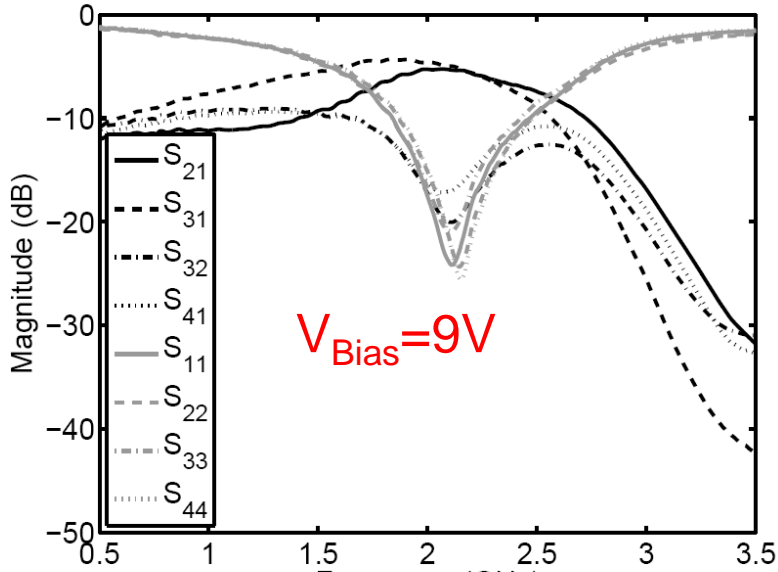

Tunable Branch-Line Coupler (3)

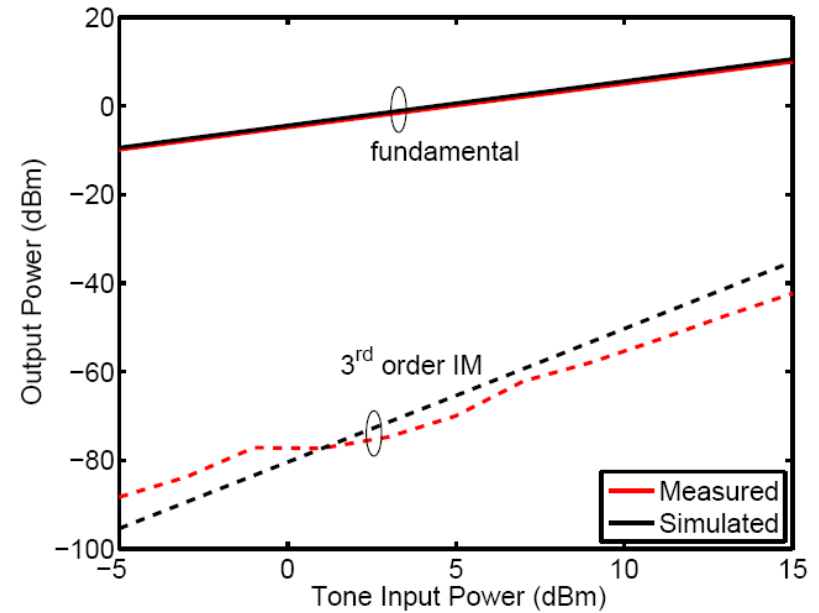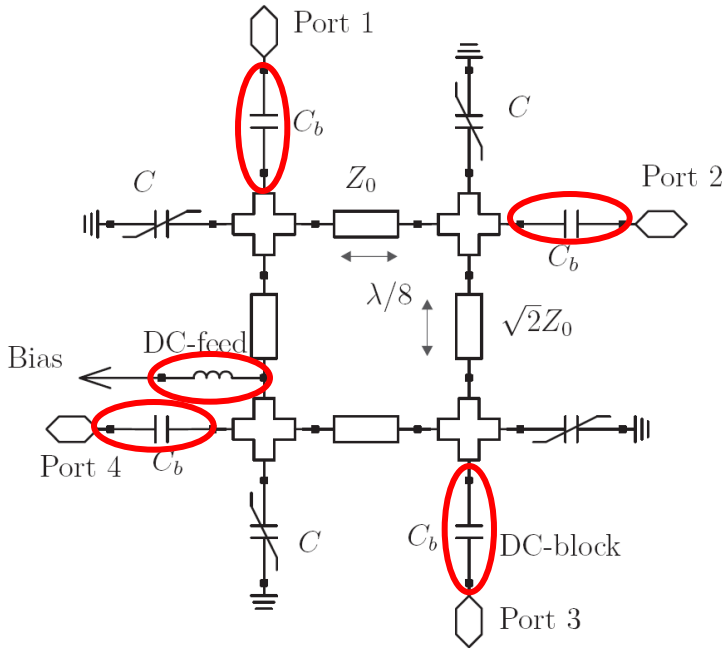

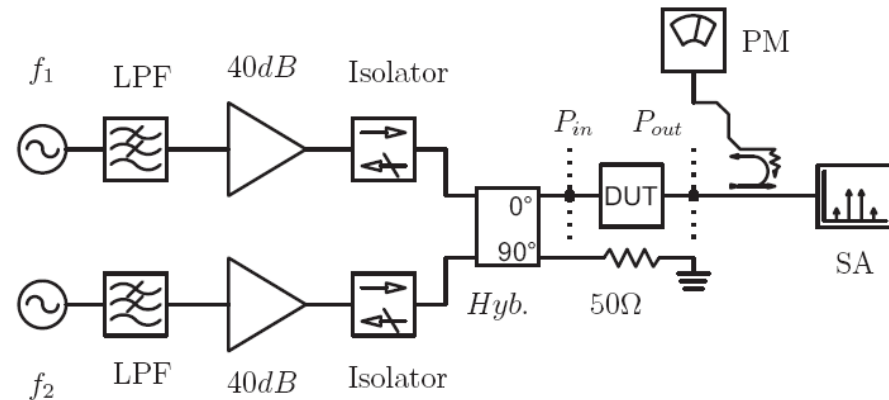- Tuning range 1.8-2.3GHz
- IL < 2.7dB, RL > 15dB
- Amplitude error < 0.4dB
- Phase error < 5deg




System Considerations – Modulated Signals


Arbitrary Modulated Signal

$$\begin{aligned} s(t) &= A \cos(\phi) \cos(2\pi ft) - A \sin(\phi) \sin(2\pi ft) \\ &= I \cos(2\pi ft) + Q \sin(2\pi ft). \end{aligned}$$


Baseband

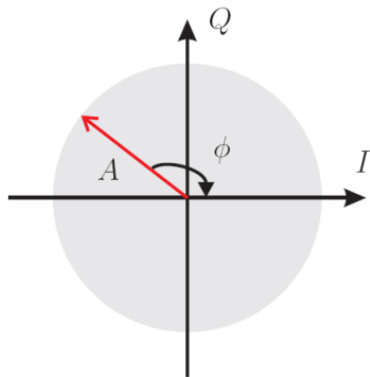


EVM

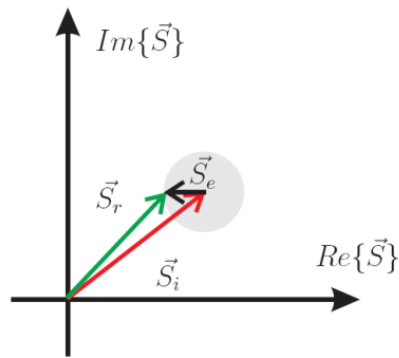

Measured QPSK Trajectory

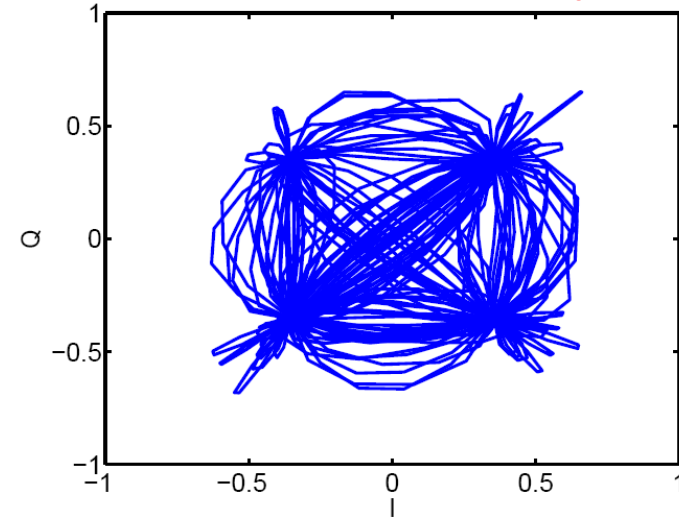



Measured WCDMA Channel

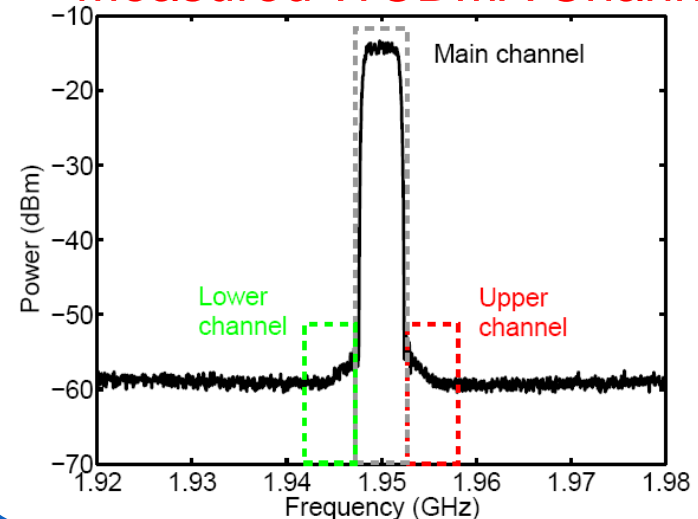



- 3GPP WCDMA signal
- Specified EVM 17,5%
- Specified ACLR 33dB

System – Balanced Amplifier

Operating at transmit band $f=1.95$ GHz

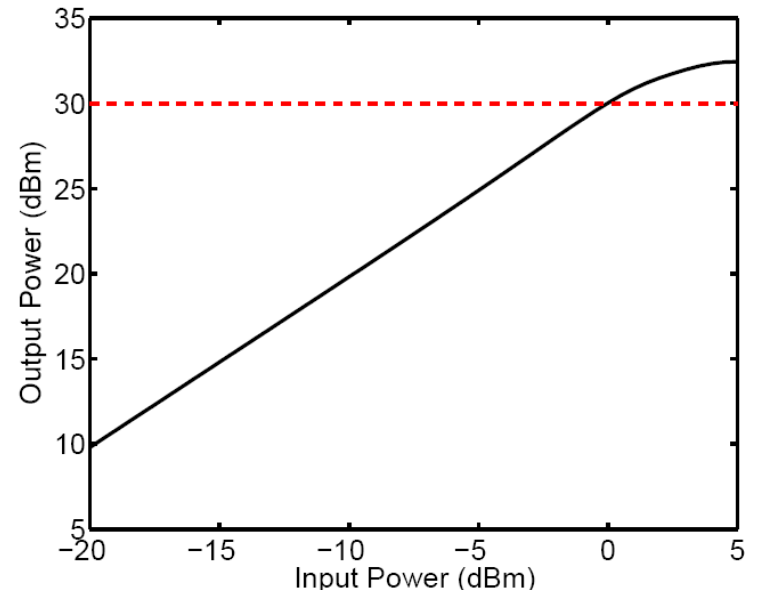
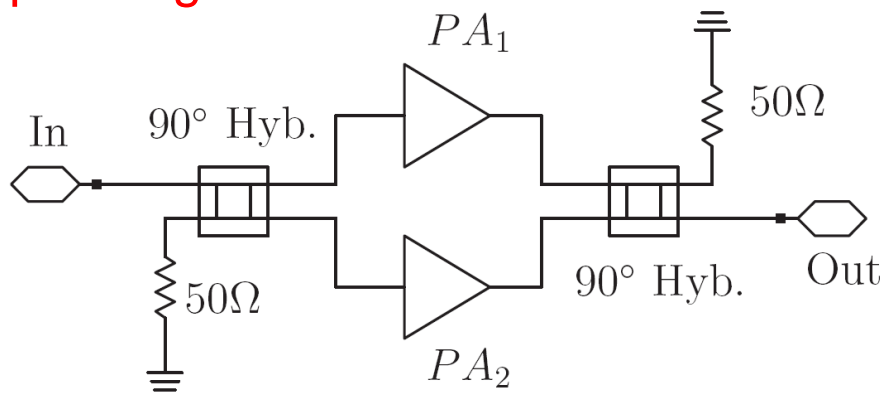


Voltage waveforms at $P_{in}=0$ dBm

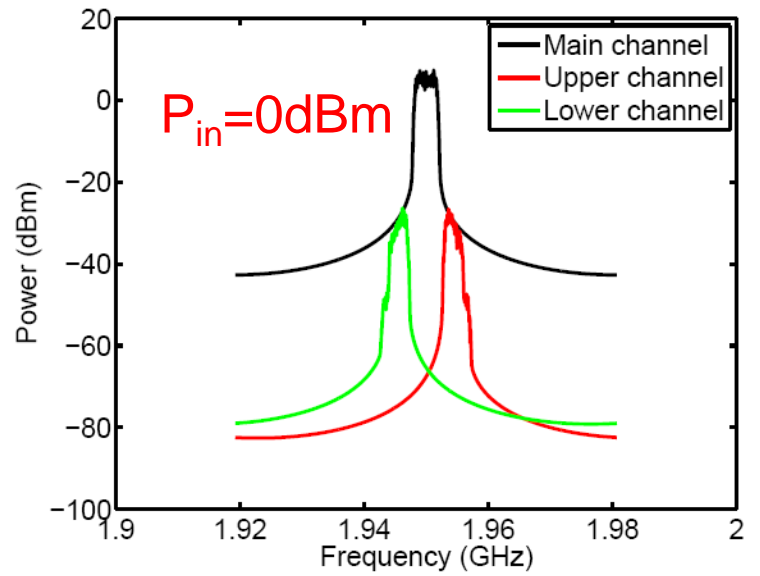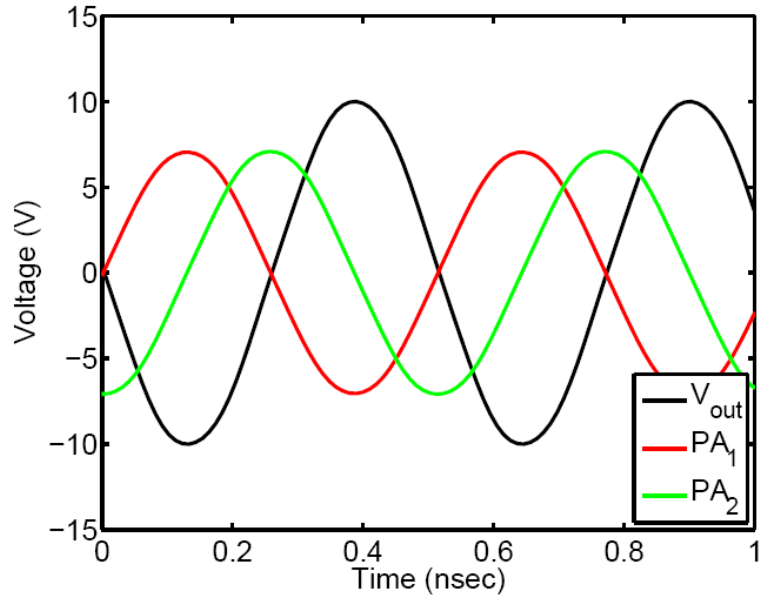


System – Reconfigurable Balanced Amplifier (1)

Operating at transmit band $f=1.95$ GHz

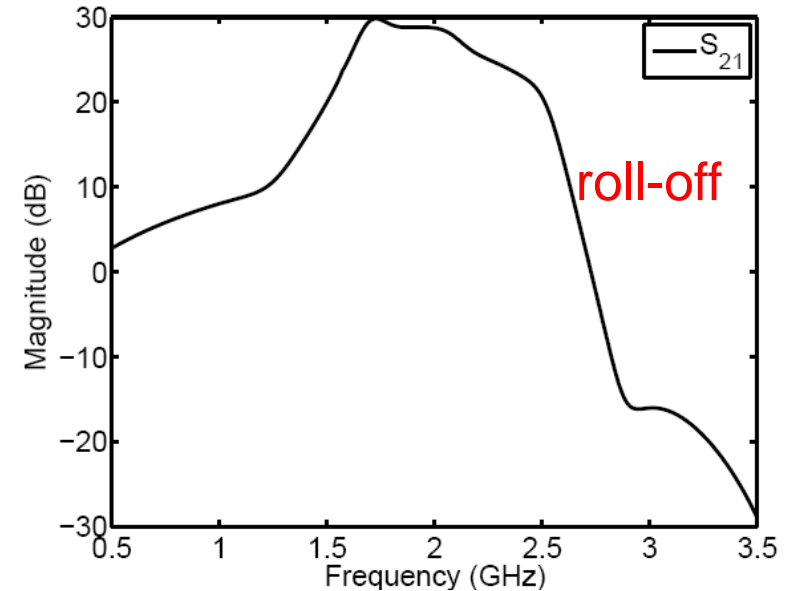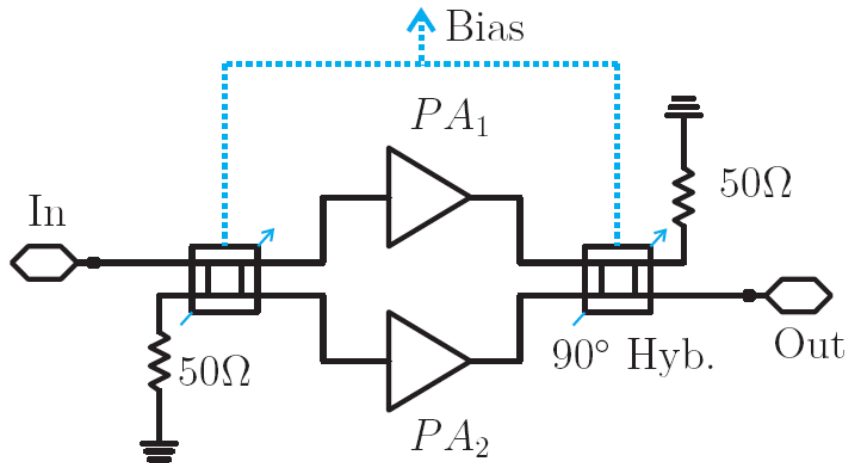


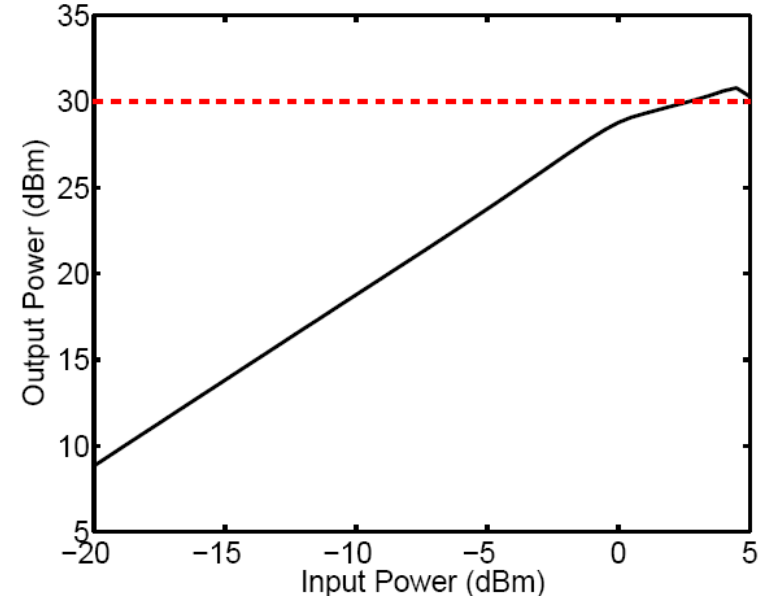- Size reduction 50%
- Lowpass filtering
- Increased loss
- Bias voltage 5V
- Strong nonlinearities due to BST-varactors





System – Reconfigurable Balanced Amplifier (2)

Operating at transmit band $f=1.95$ GHz




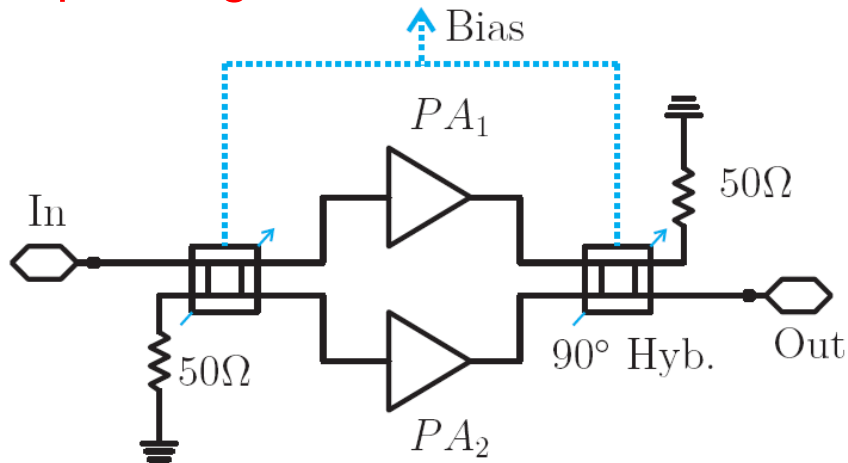


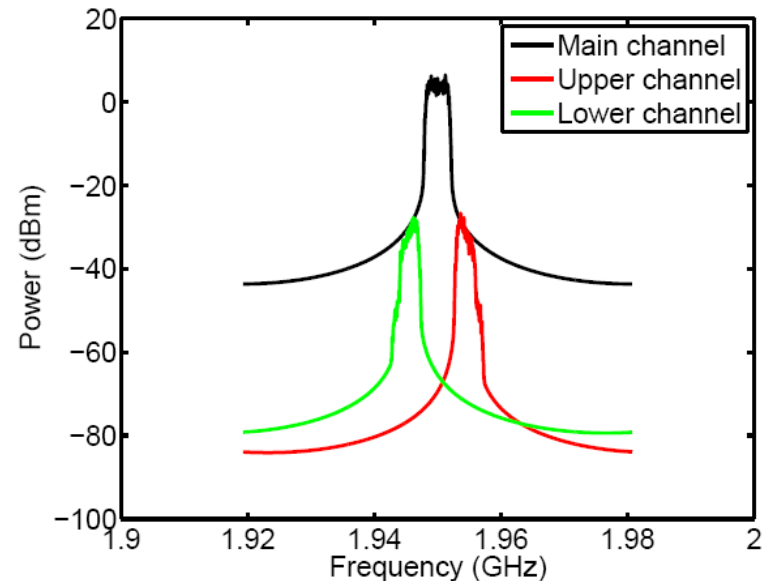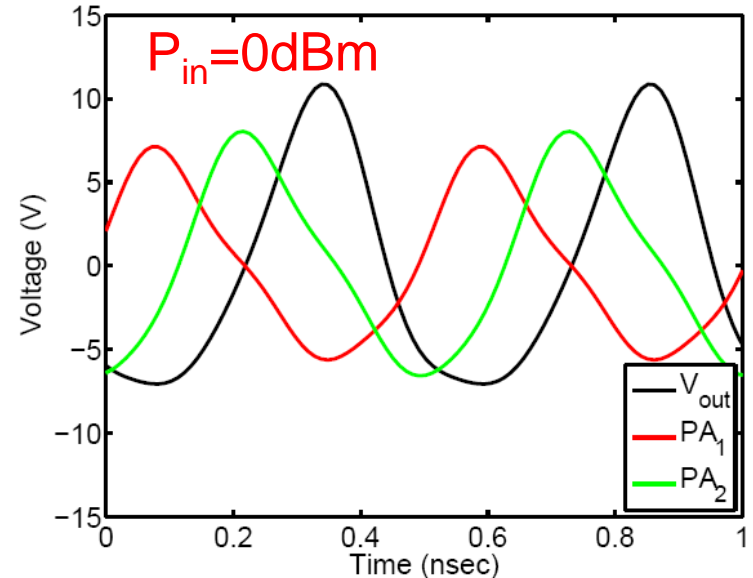- Distortion at voltage waveforms
- Performance still within specification
- Simulated EVM < 10%
- Simulated ACLR ~ 35dB







Tunable coupler with 3 cascaded varactors

Operating at transmit band $f=1.95$ GHz

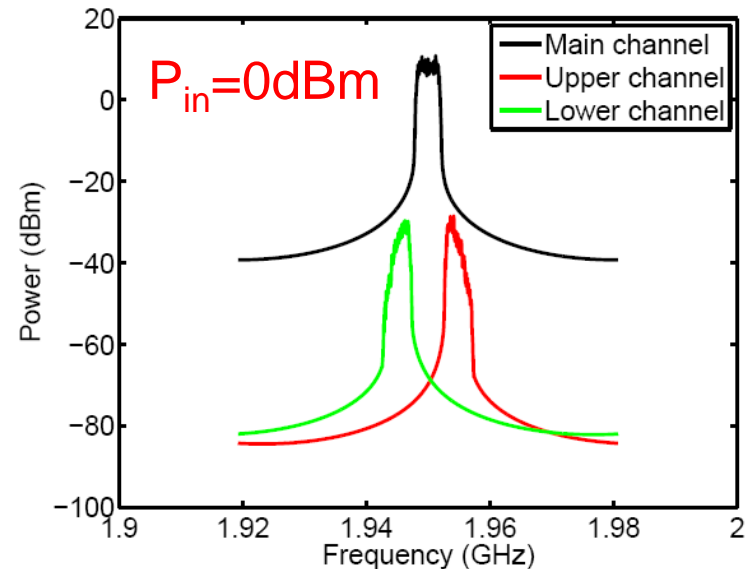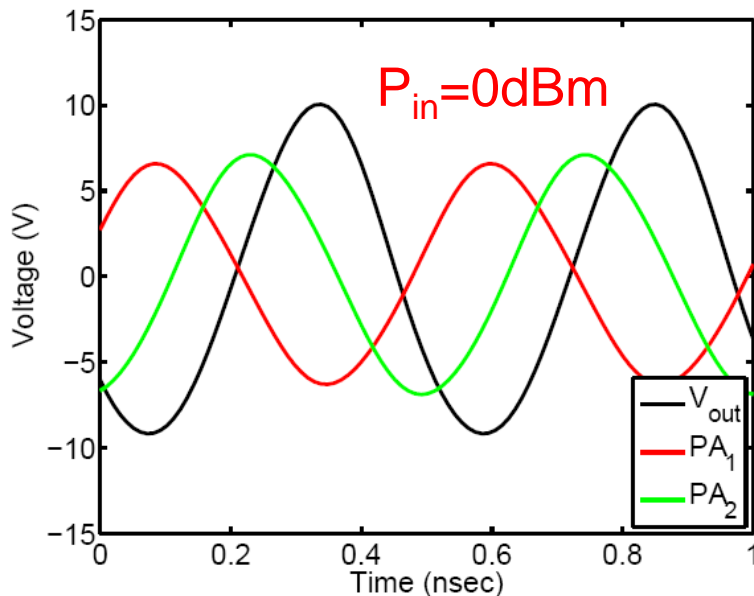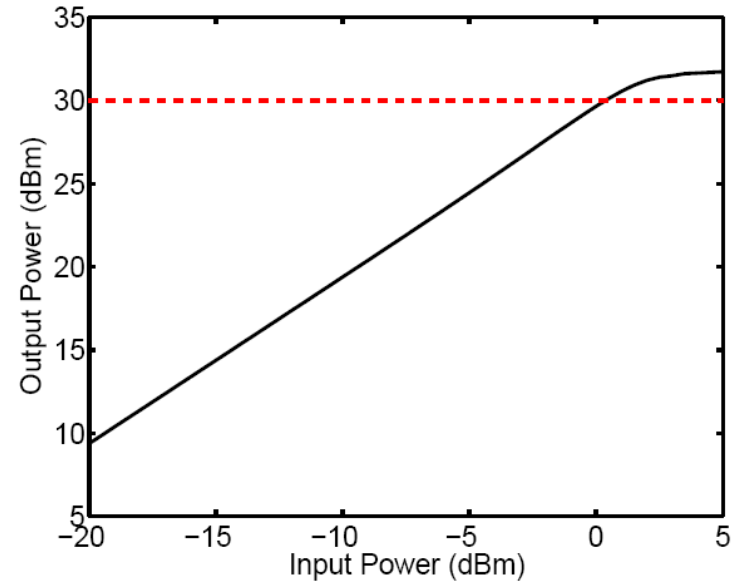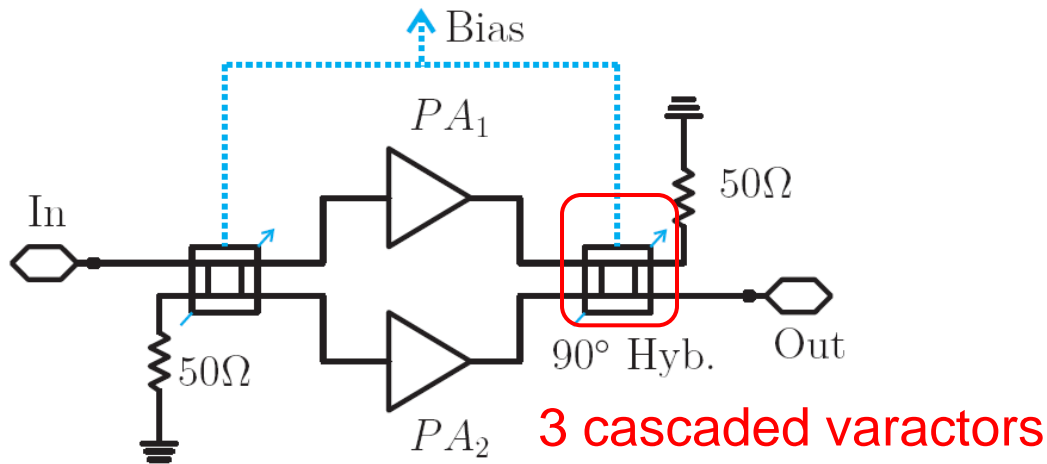

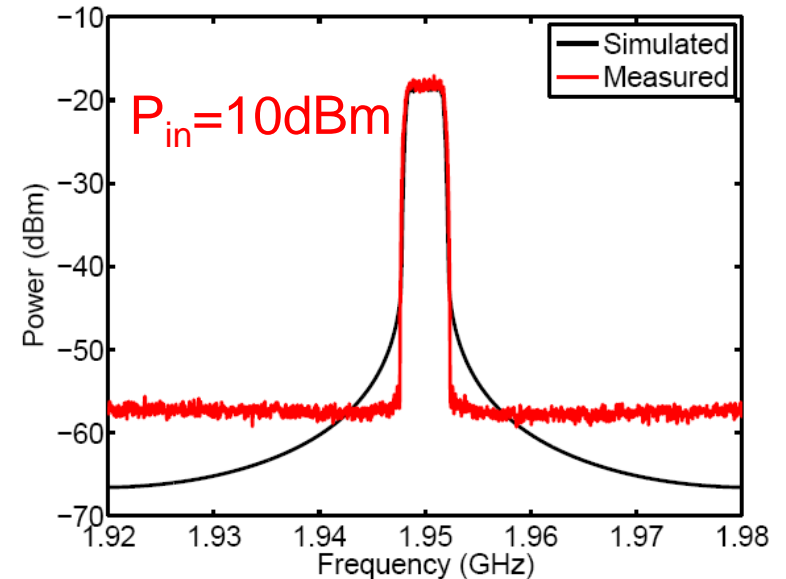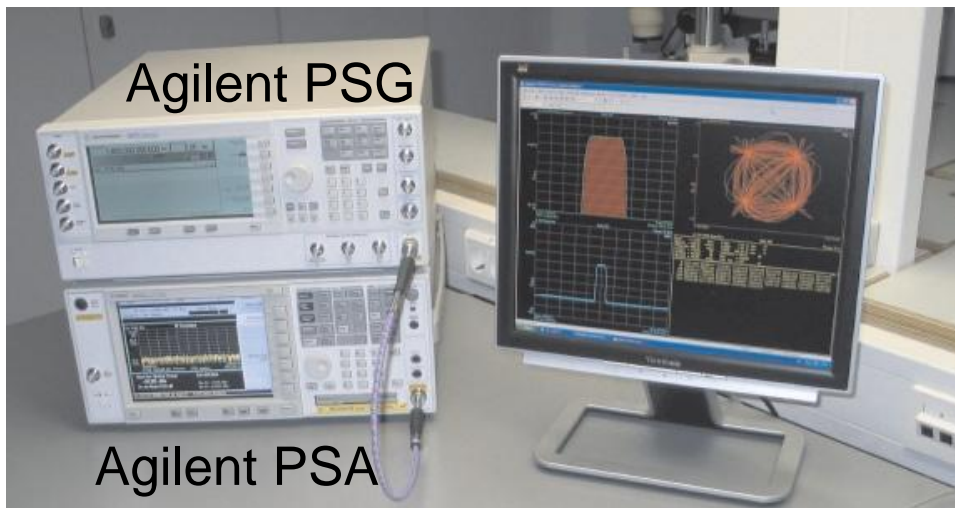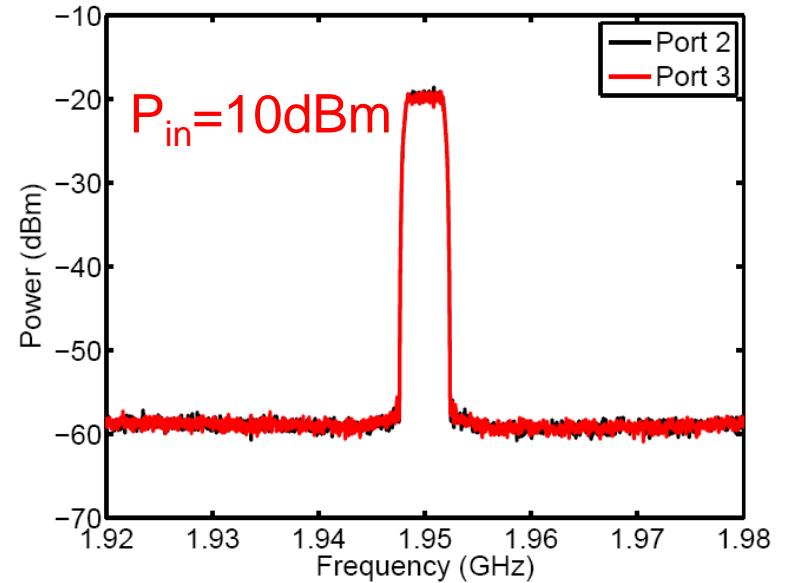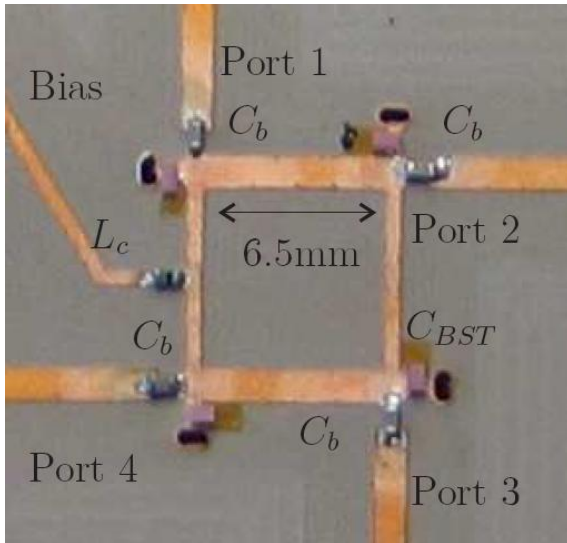Verification – Tunable Branch-Line Coupler



Conclusion & Outlook

Conclusion

- Potential of ferroelectrics in tunable front-end
- Reliable modeling and characterization
- Candidates for tunable microwave circuits
 - Frequency agile filters
 - Reduced size tunable dividers and couplers
- Prototype implementation & results
- Overall good agreement to simulation

Outlook

- Integration of tunable subsystems into front-end