

Reconfigurable Front-End Modules Based on Ferroelectric Varactors


R. Weigel and E. Lourandakis

Institute for Electronics Engineering, University Erlangen-Nuremberg
Cauerstraße 9, 91058 Erlangen, Germany

weigel@lfe.de




Outline

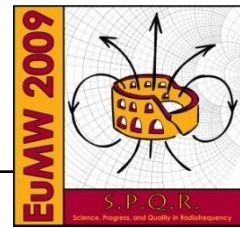



- Motivation
- Tunable Passive Components
- Part 1
 - Frequency Agile Filters
 - Frequency Agile Power Dividers & Couplers
 - Prototype Implementation & Results
- Part 2
 - Impedance Matching Networks
 - L, Pi, T, and reflection type
 - Prototype Implementation & Results
- Conclusion

Motivation

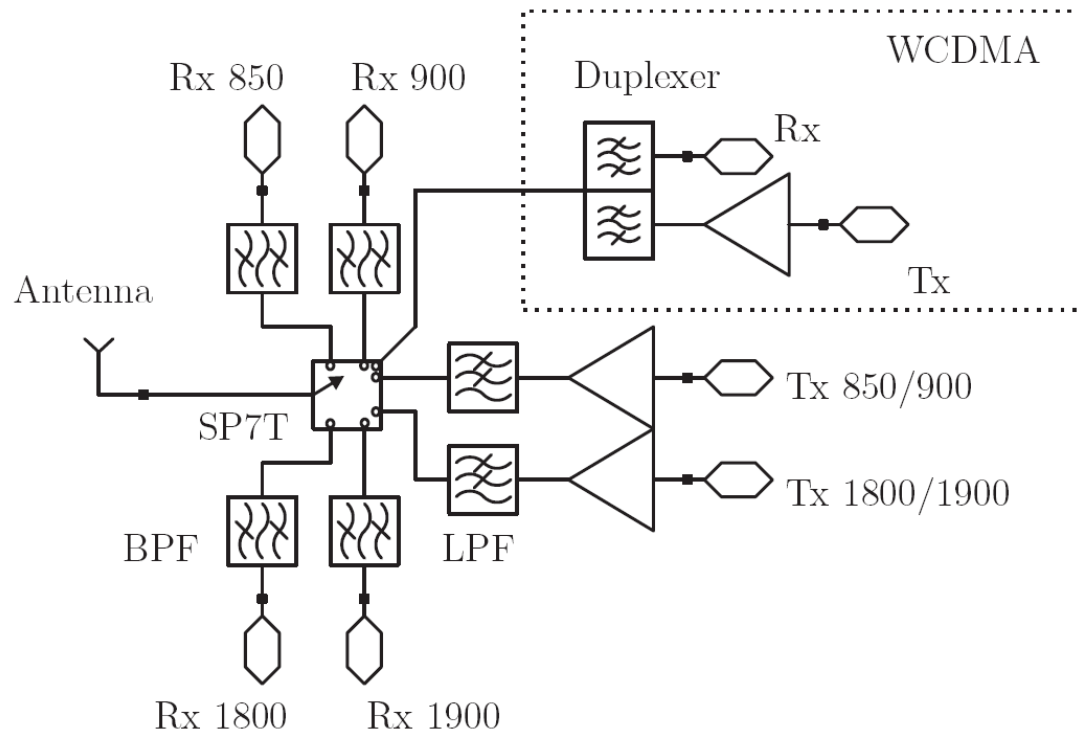






- Increasing number of communication bands
- Additional wireless services, e.g. GPS, WiMAX
- Demand for reconfigurable front-end solutions

Ferroelectric Thin-Film Varactors

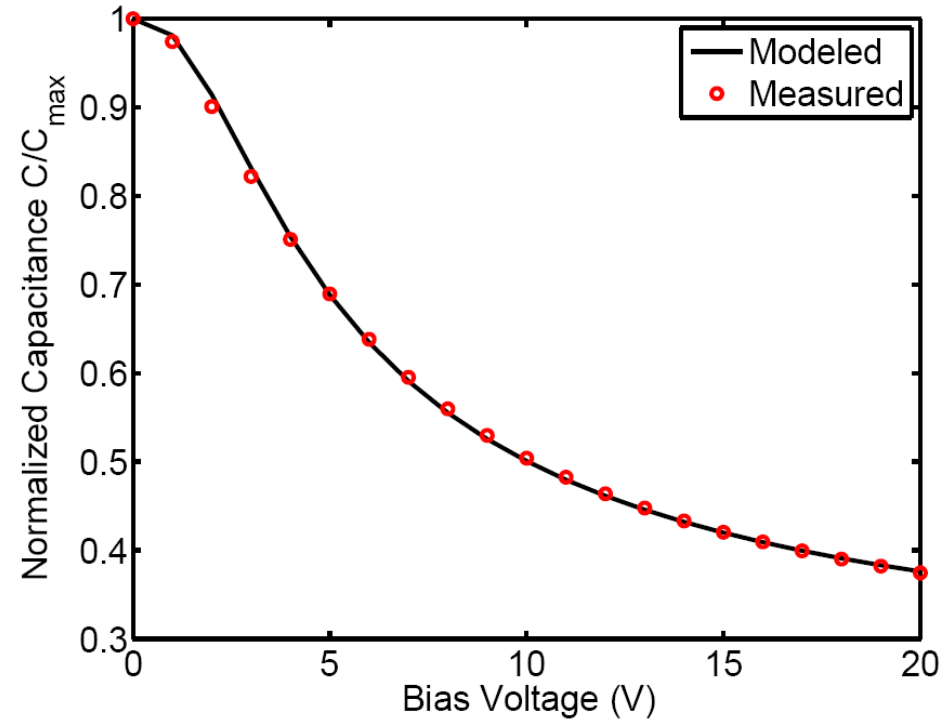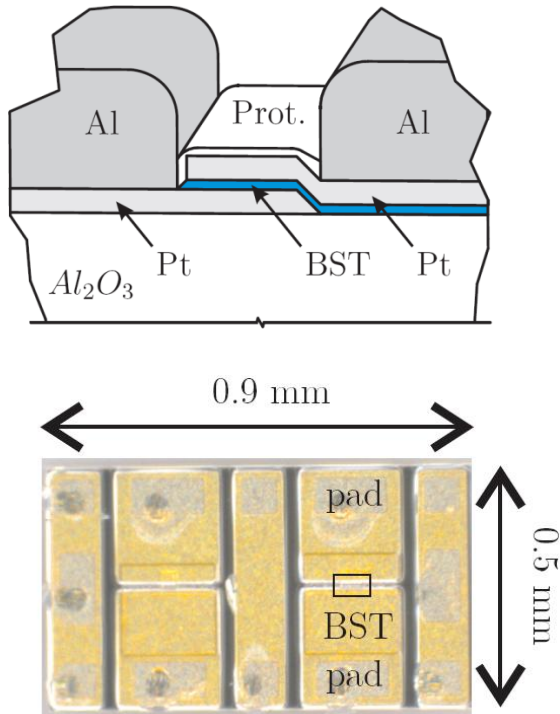



- Nonlinear component
- Compact dimensions
- Induced acoustic resonance

Ferroelectric Thin-Film Varactors

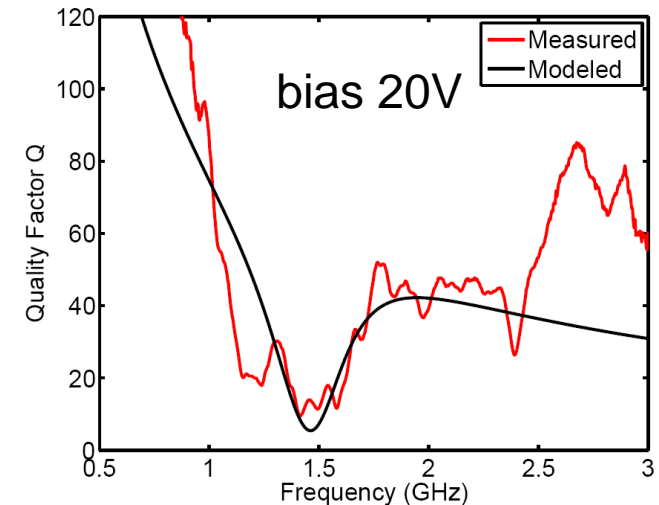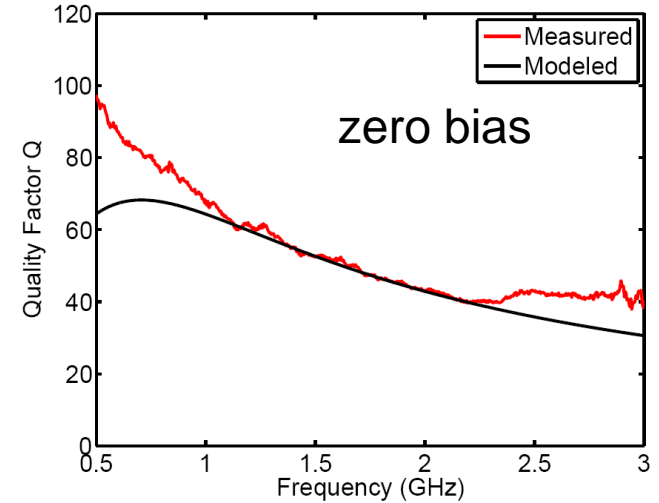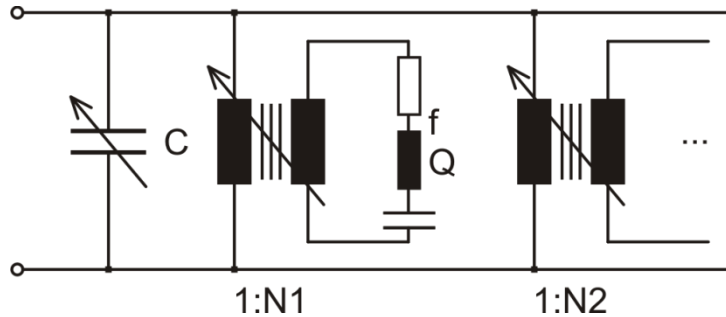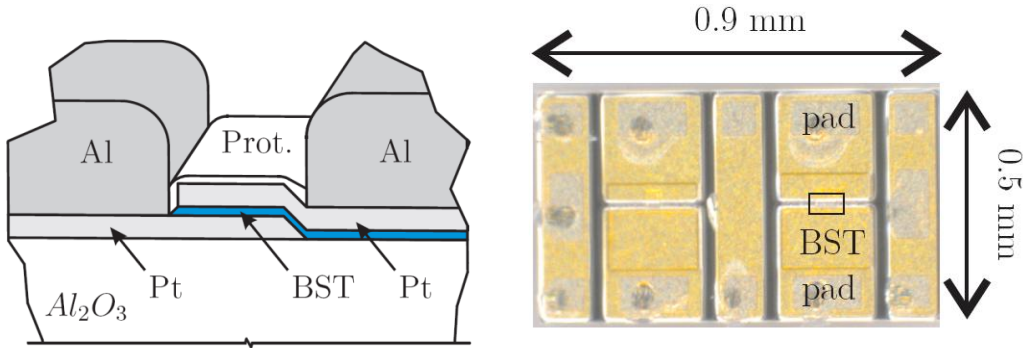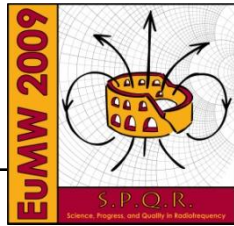

- Metal-Insulator-Metal (MIM)
- Compact dimensions
- Q around 40 @ 2 GHz
- ADS model available

Filter Design – Lowpass

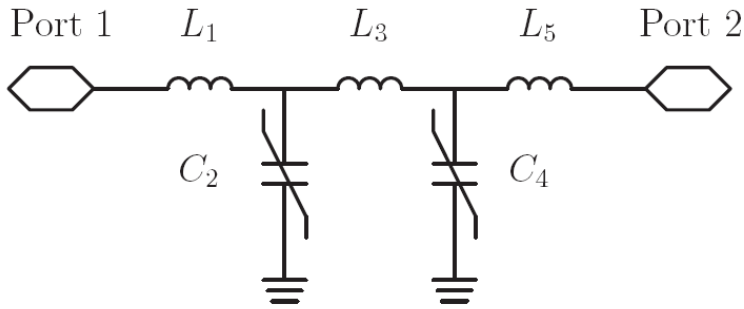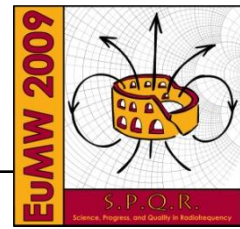


$$M_{i=1,3,5} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_i \\ 0 & 1 \end{bmatrix}$$

$$M_{j=2,4} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_j & 1 \end{bmatrix}$$

$$M_{total} = M_1 \cdot M_2 \cdot M_3 \cdot M_4 \cdot M_5$$

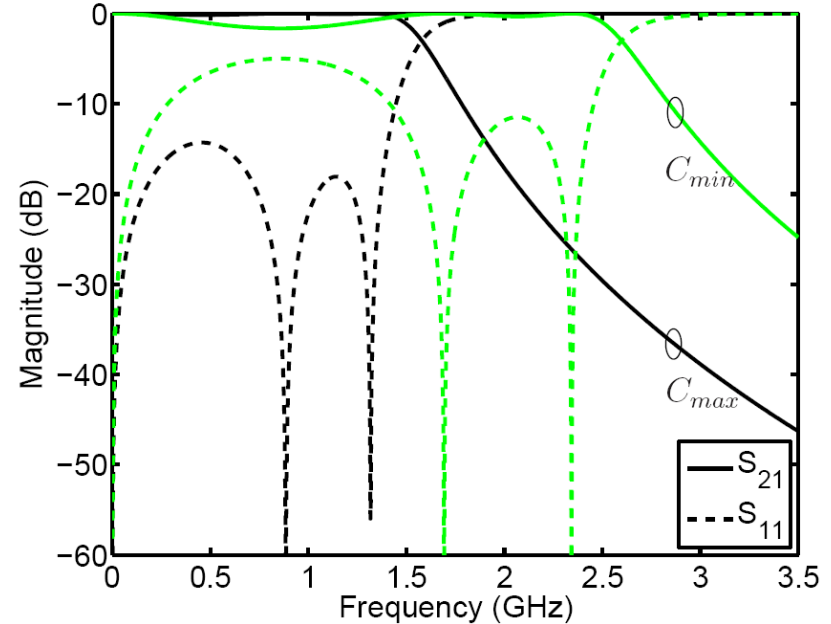- Chebyshev lowpass filter
- Analytical formulas for zero locations





$$z_2 = j\omega_2 = \pm \frac{\sqrt{2CL_3(-2L_1L_3 - 2L_1^2 + Z_0^2CL_3 + \alpha)}}{2CL_1L_3}$$

$$z_3 = j\omega_3 = \pm \frac{\sqrt{2CL_3(-2L_1L_3 - 2L_1^2 + Z_0^2CL_3 - \alpha)}}{2CL_1L_3}$$

$$\alpha = \sqrt{-4L_1L_3^2Z_0^2C + 4L_1^4 + 4L_1^2L_3Z_0^2C + L_3^2Z_0^4C^2}$$

Filter Design – Notch Filter

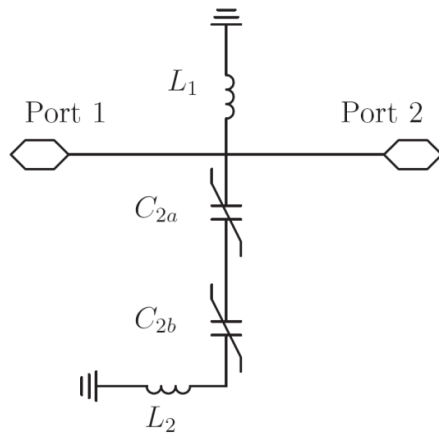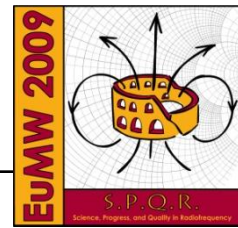


$$M_1 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix}$$

$$M_2 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix}$$

$$Y_2 = 1 / [2 / (pC) + pL_2]$$


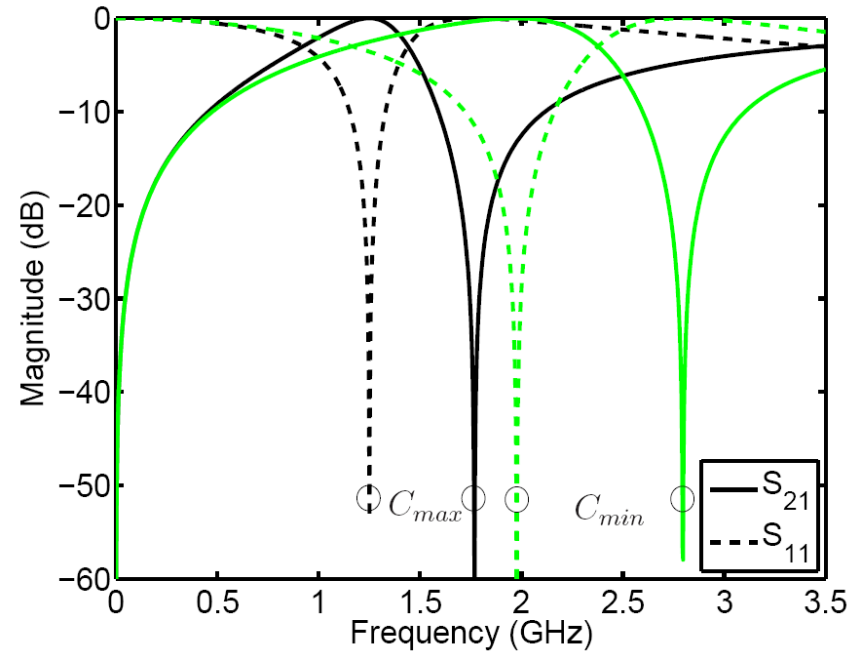
- Notch filter
- Analytical formulas for zero and pole locations



zero $z_1 = j\omega_1 = \pm \sqrt{-2 / [(L_1 + L_2)C]}$

pole $p_2 = j\omega_2 = \pm \sqrt{-2 / (L_2C)}$



Modified Comblin Filter

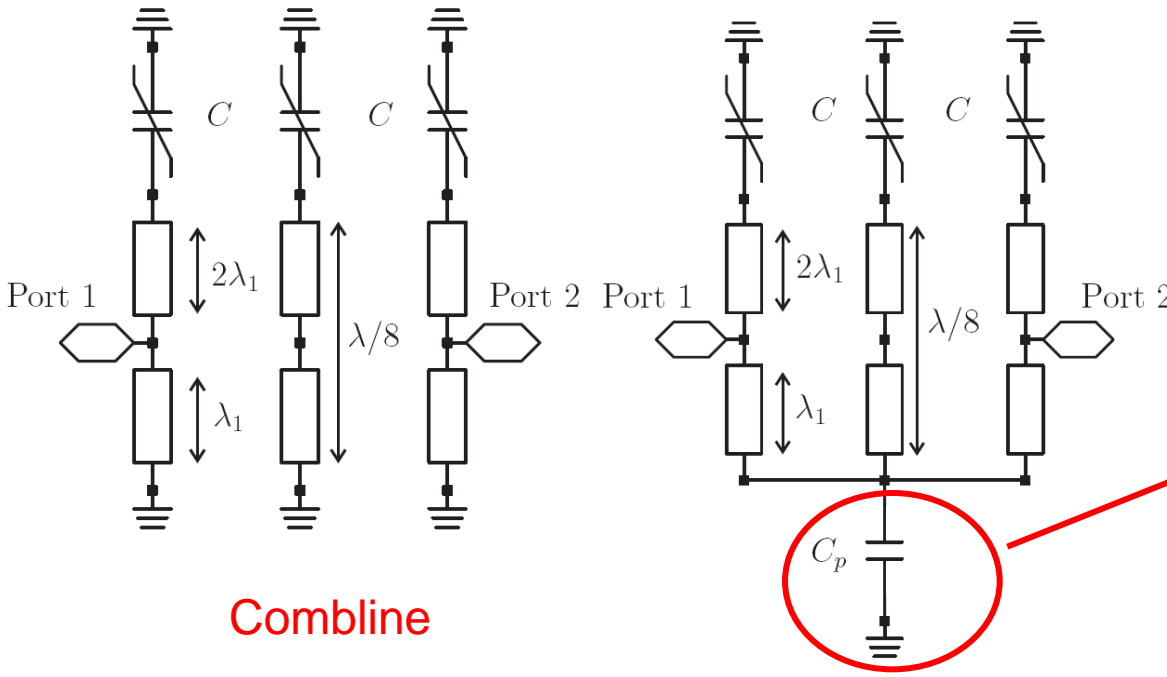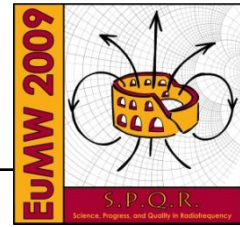

Comblin



Modified

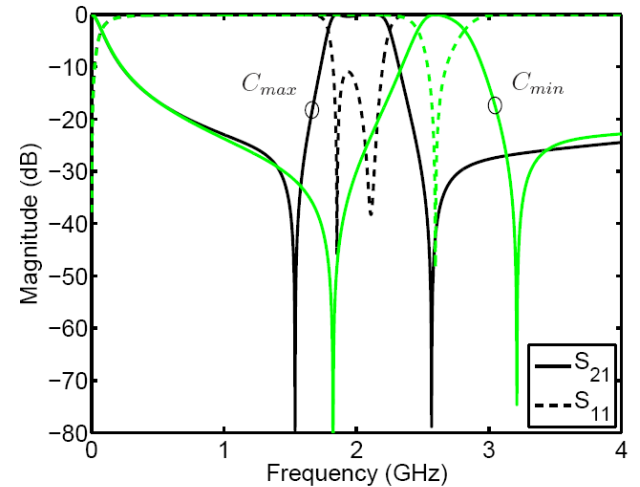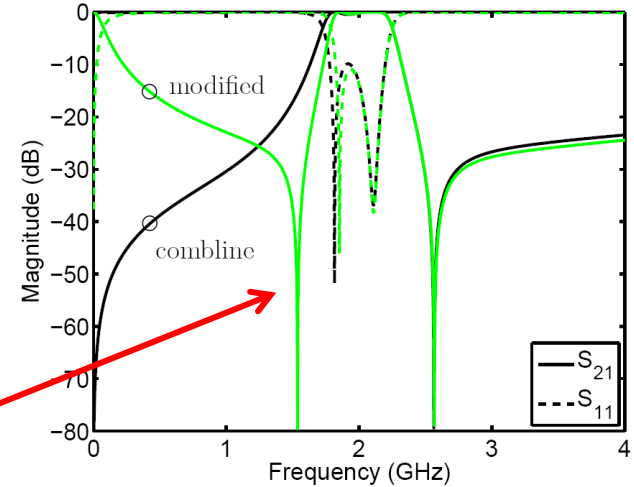- Second attenuation pole is shifted from DC to lower stopband







Frequency Agile $\lambda/4$ Segments

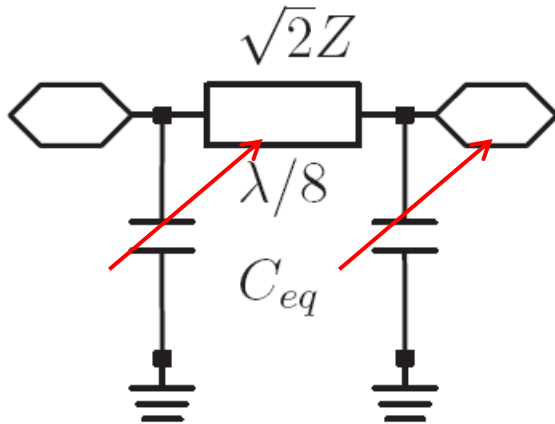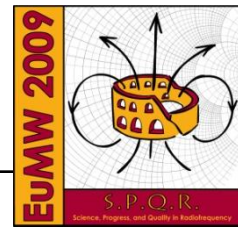



Tuning of $C_{eq} \rightarrow$
shifts resonance

$$C_{eq} = \frac{1}{\omega \sqrt{2}Z} = \frac{1}{2\pi f \sqrt{2}Z}$$

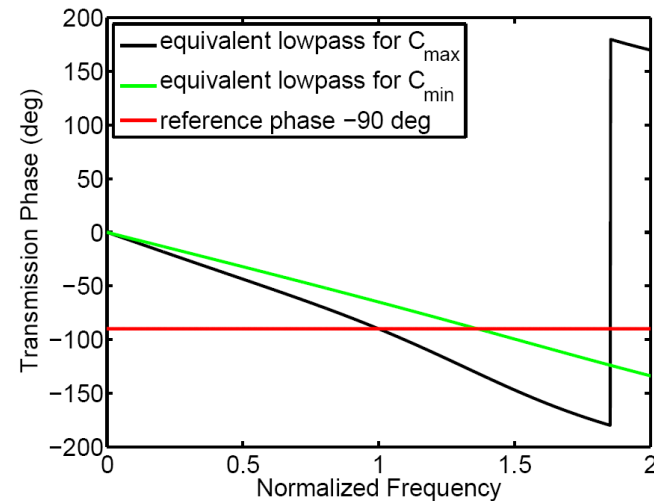
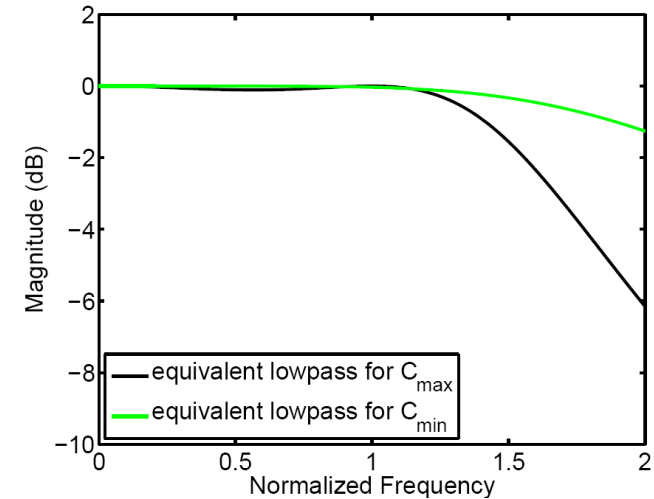
- Scalable network
- Slightly detuned Z
- Perfect phase shift





Tunable Wilkinson Divider

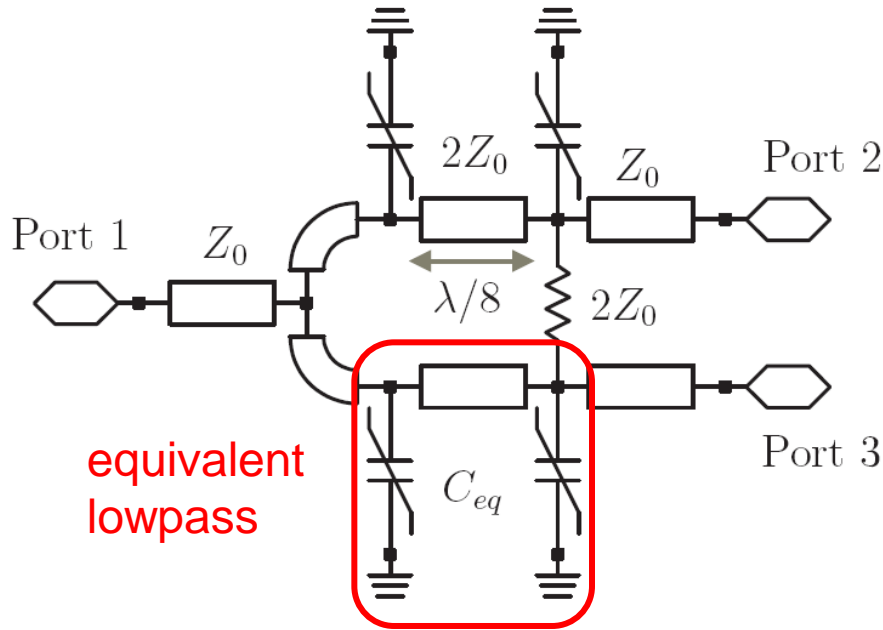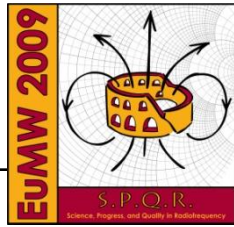

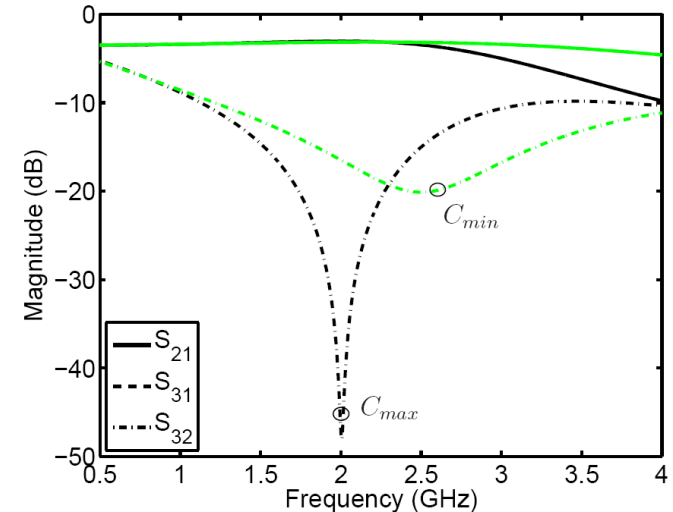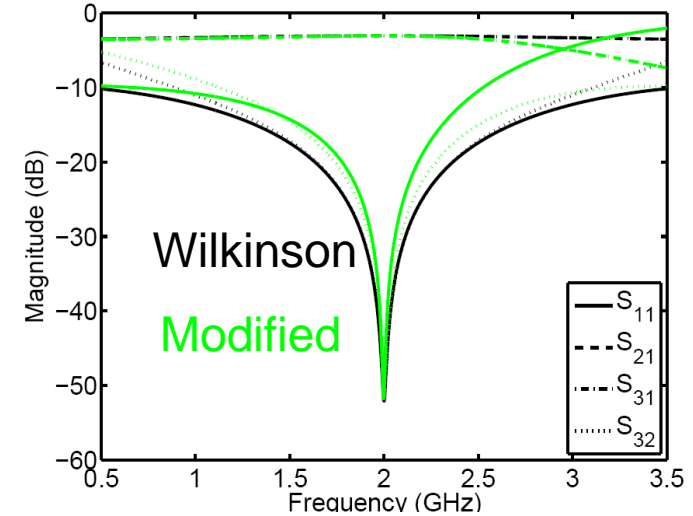- Size reduction 50%
- Multiband tuning
- Assumed tunability 60%





Tunable Branch-Line Coupler

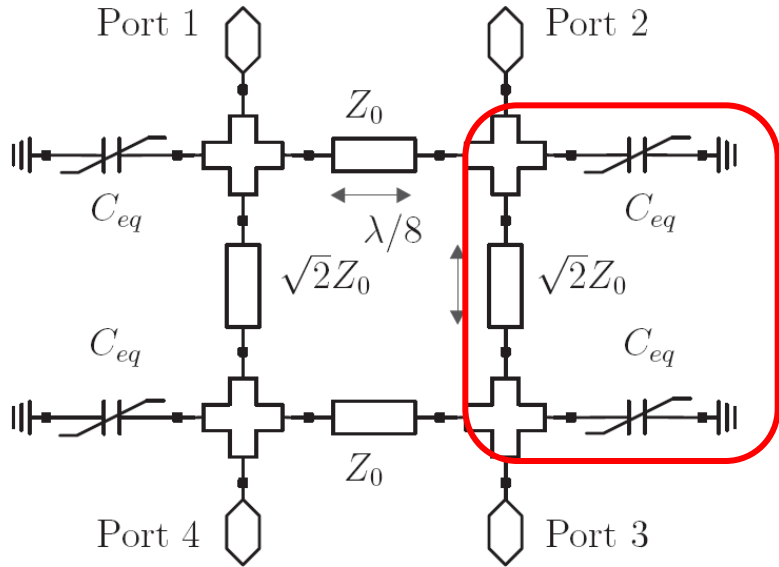
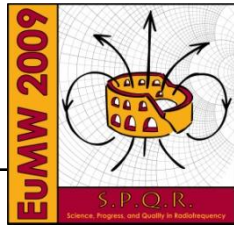


equivalent
lowpass

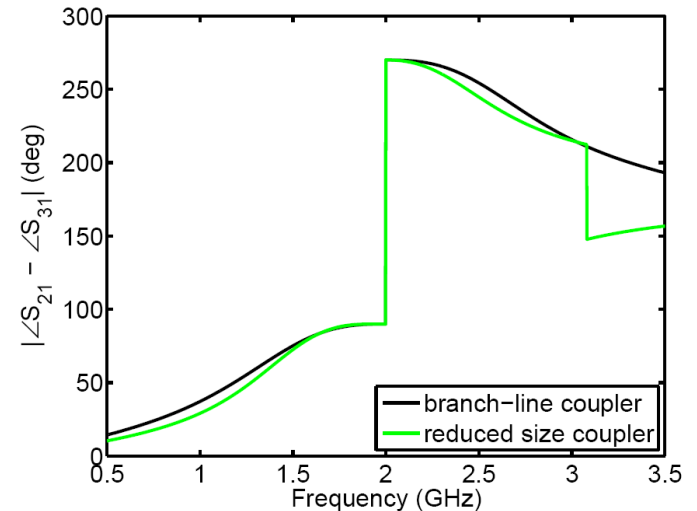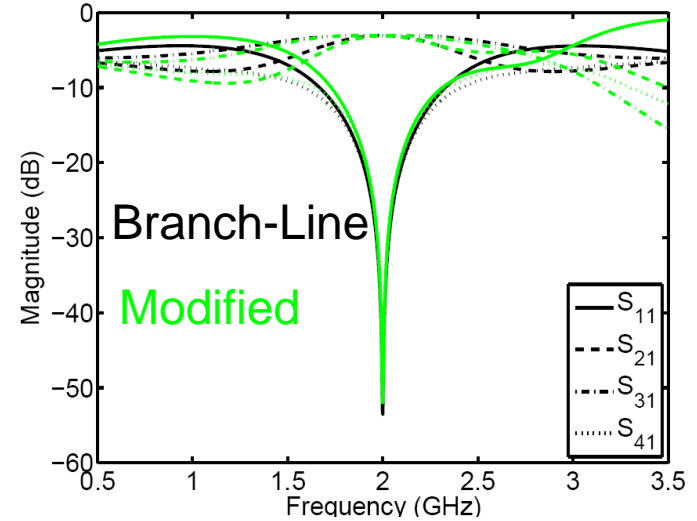- Size reduction 50%
- Perfect phase match
- C_{eq} serves as shunt element for both segments





Tunable Branch-Line Coupler


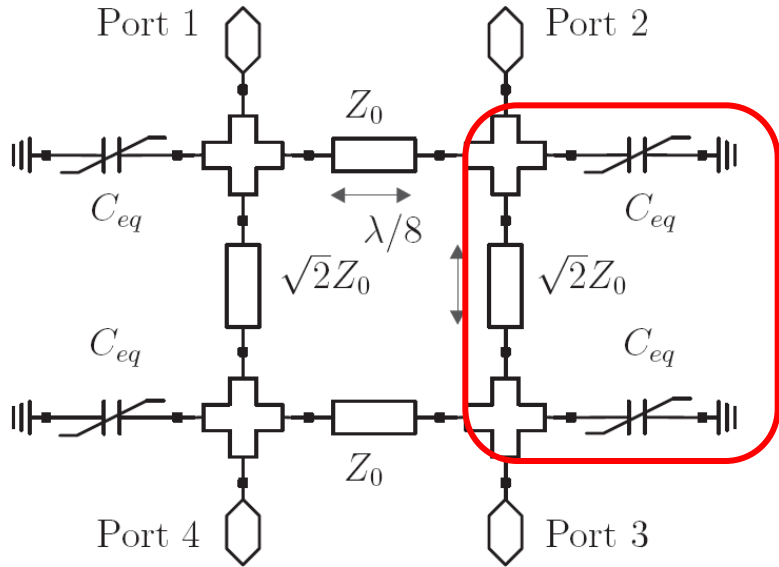
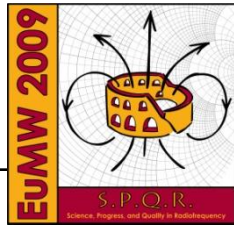


equivalent
lowpass

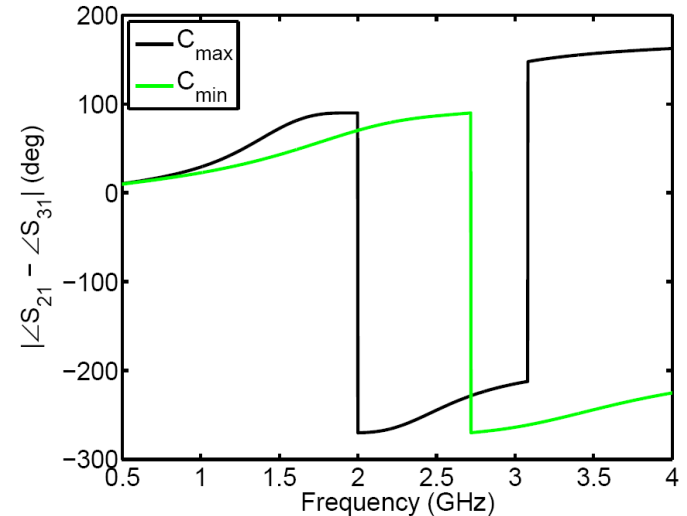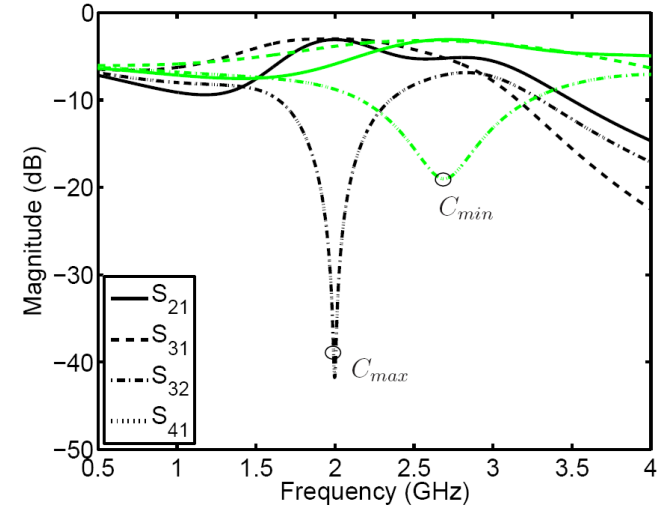
- Size reduction 50%
- Perfect phase shift
- Multiband operation with tunability of 60% for C_{eq}





Tunable Lowpass (1)

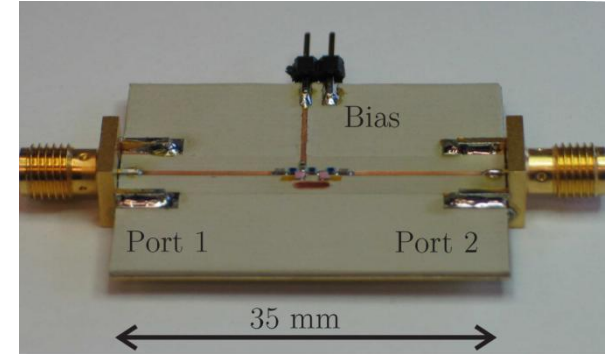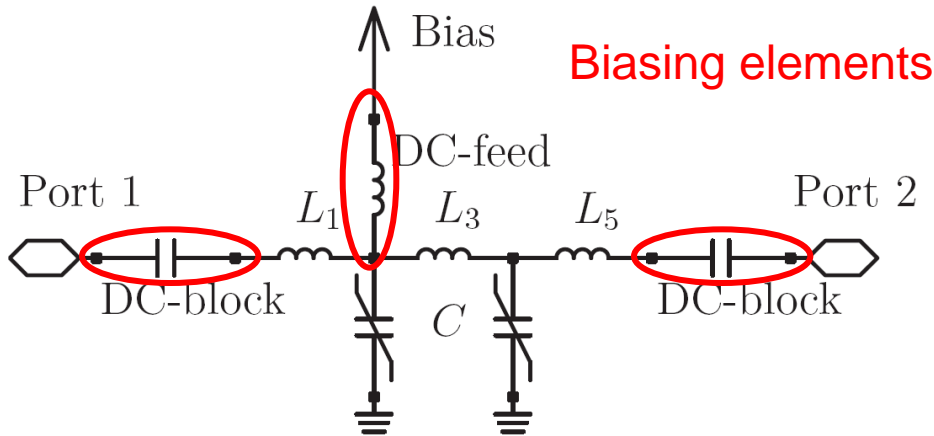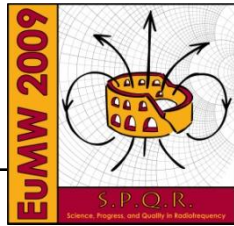


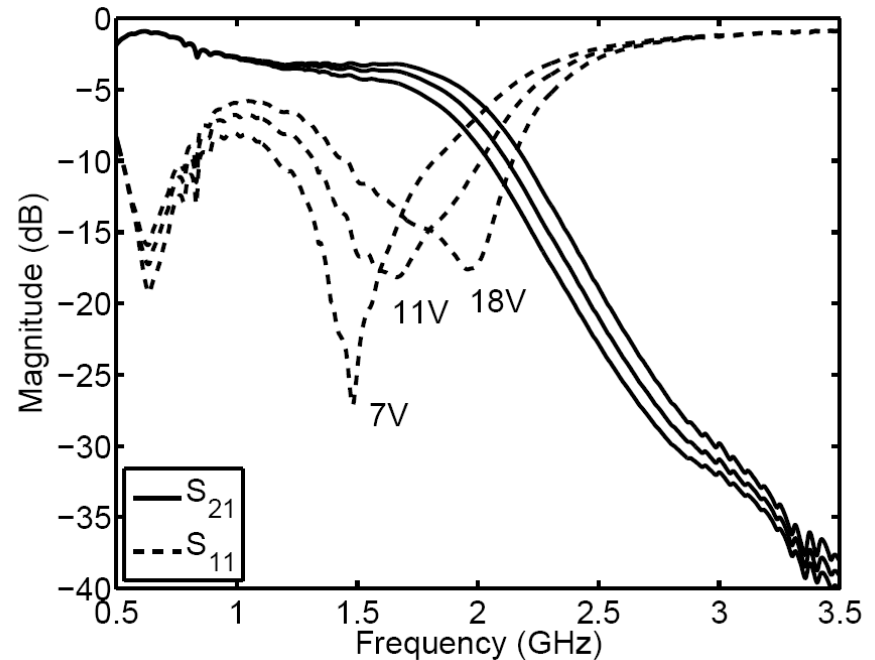
- Tuning range of 30%
- 1.5-2GHz multiband
- High losses due to moderate Q and RF isolation





Tunable Lowpass (2)

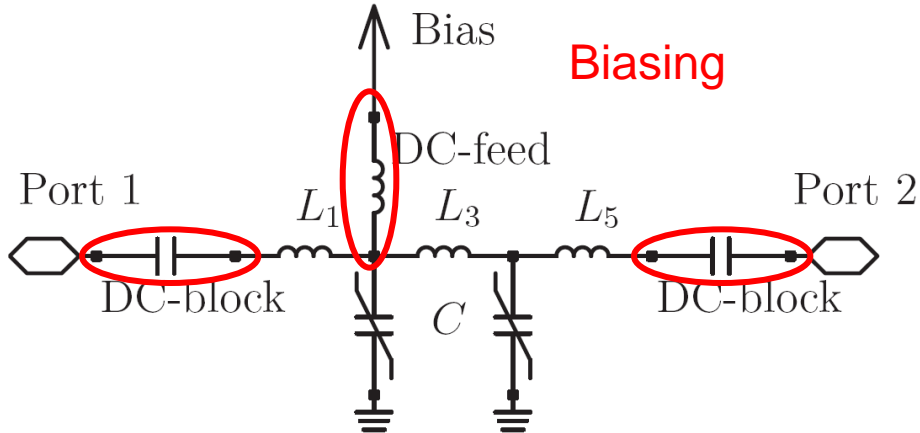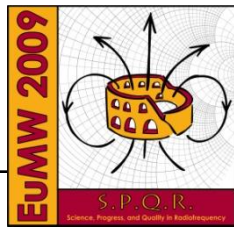

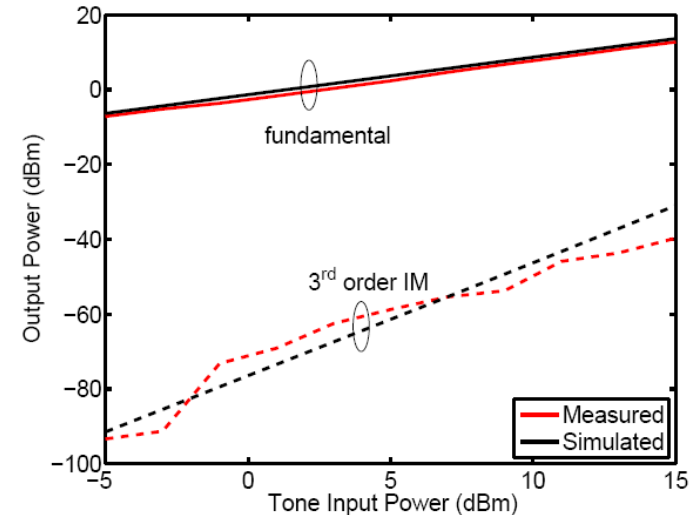
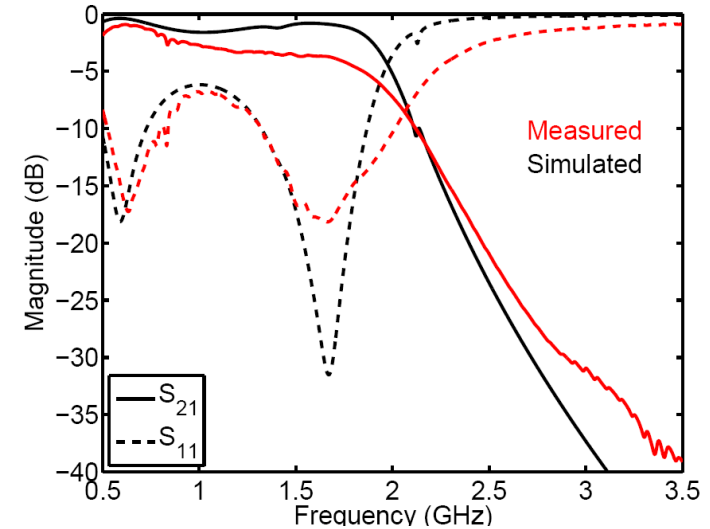
- Good agreement
- Loss due to varactor imbalances and prototype assembly
- Two-tone test @ 1.95GHz with $\Delta f=5\text{MHz}$ and Bias=20V





Tunable Notch Filter (1)

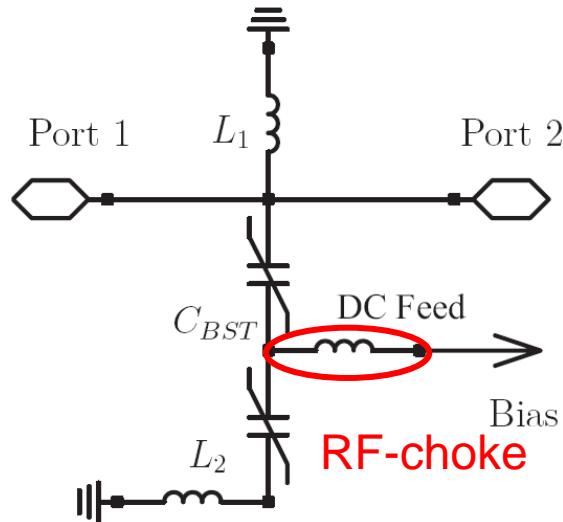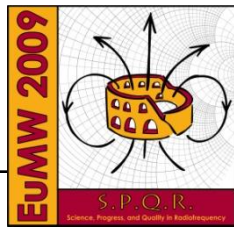

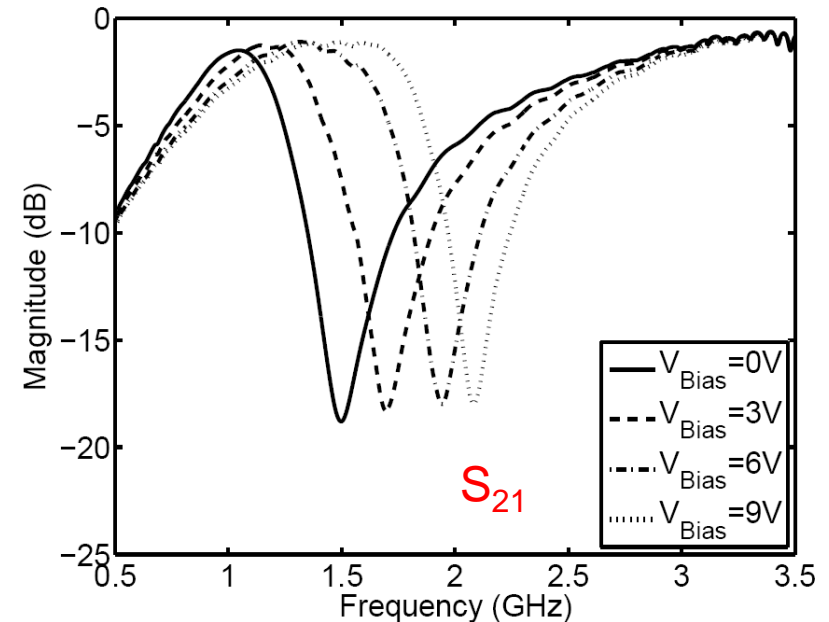
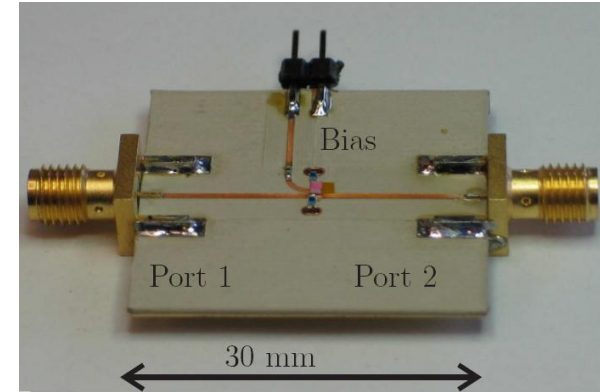
- Cascaded varactors simplify biasing
- Notch tuning 1.5-2.1GHz
- Multiband operation
- Low losses








Tunable Notch Filter (2)

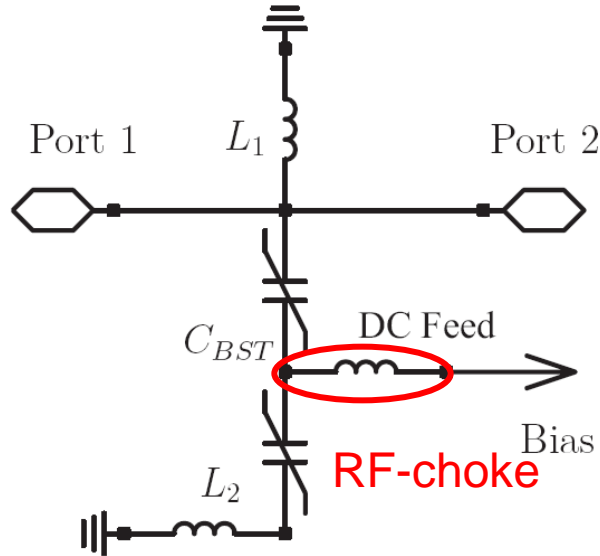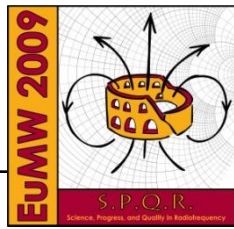

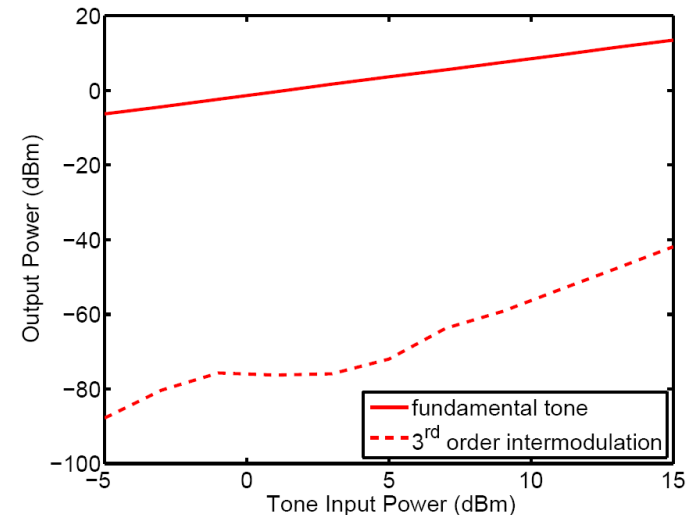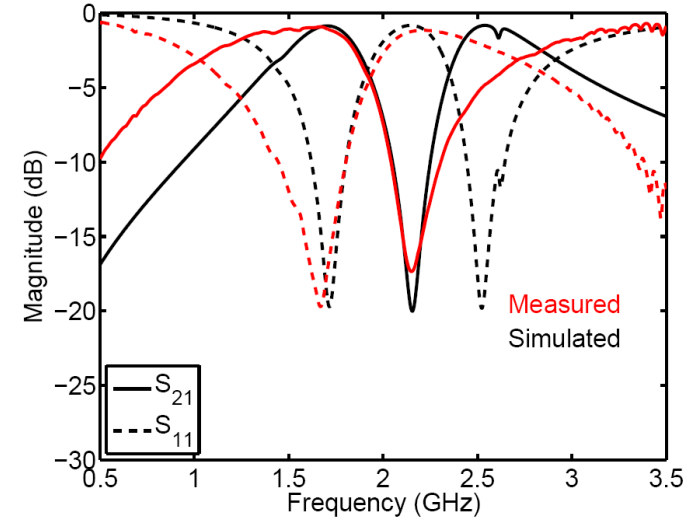- Good agreement between simulation and measurement
- Two-tone test @ 1.95GHz with $\Delta f=5\text{MHz}$ and Bias=20V





Tunable Comblines Filter (1)

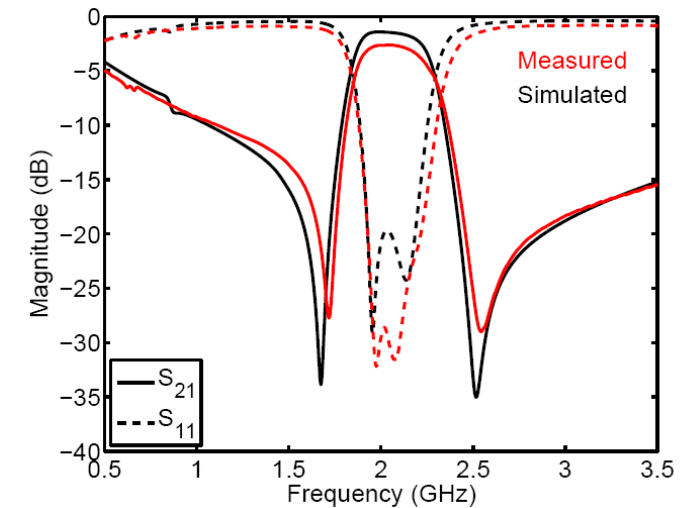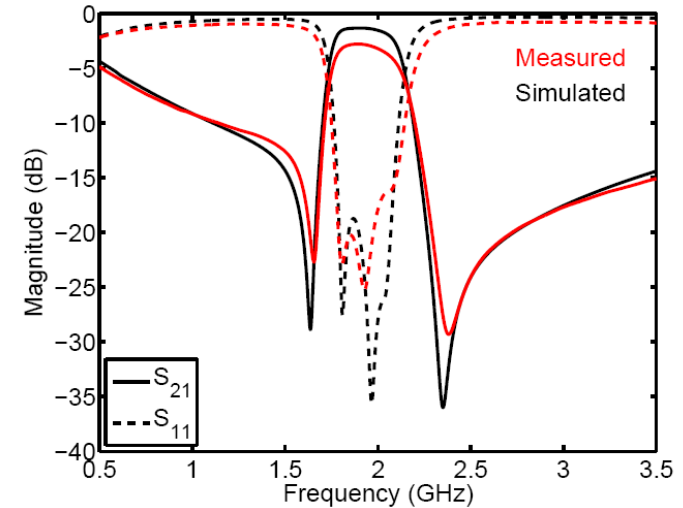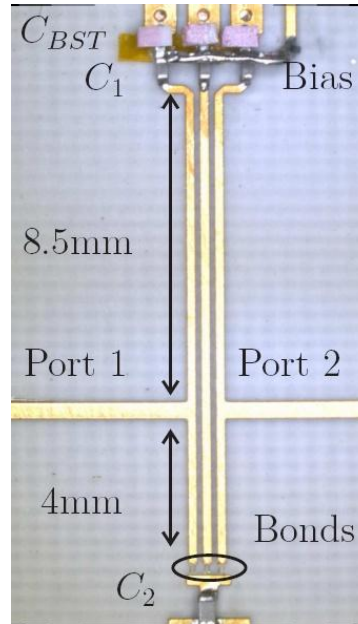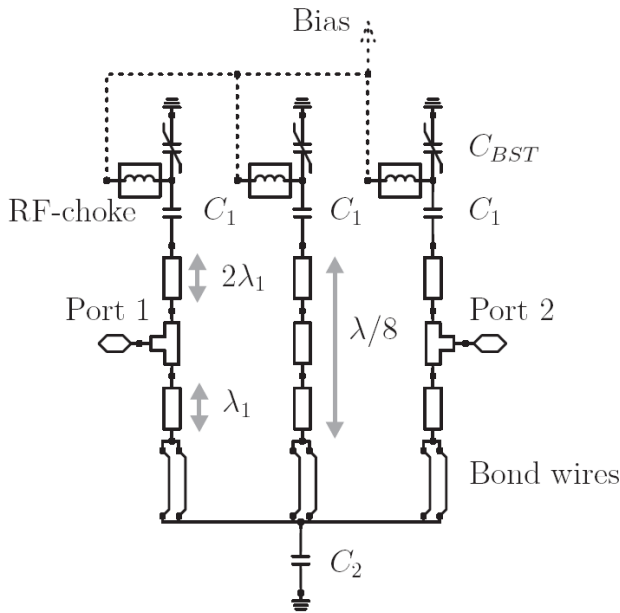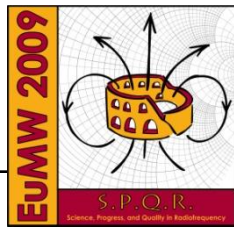


- Good agreement
- Compact dimensions
- $IL < 3\text{dB}$ and $RL > 20\text{dB}$
- Tuning 1.8-2GHz

Tunable Comblines Filter (2)

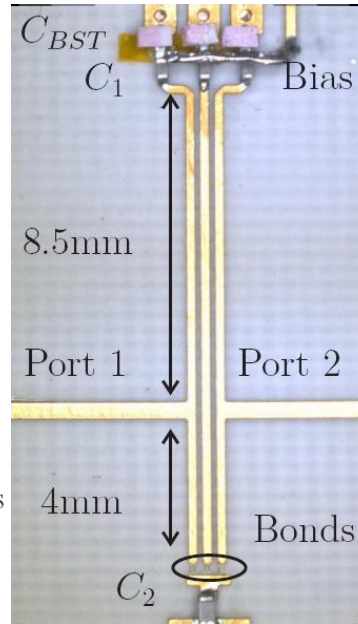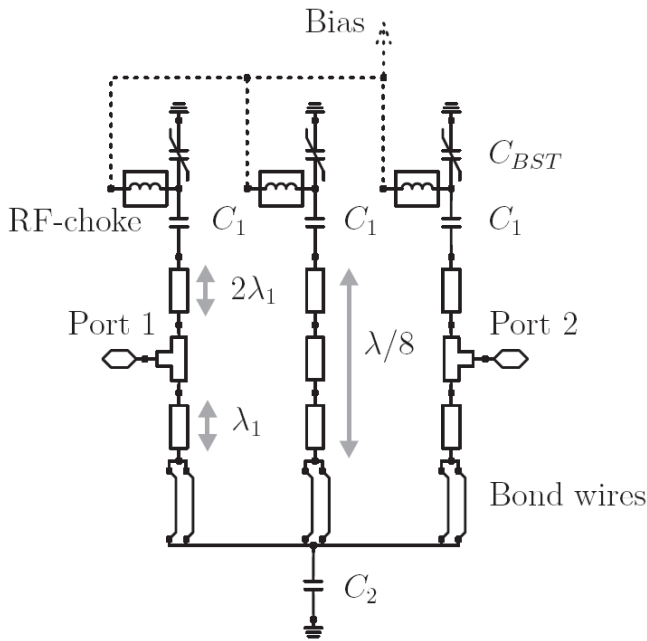






Bias (V)	f_0 (GHz)	IL (dB)	RL (dB)
0	1.85	2.8	20
5	1.90	2.7	22
10	1.97	2.6	26
15	2.02	2.6	28

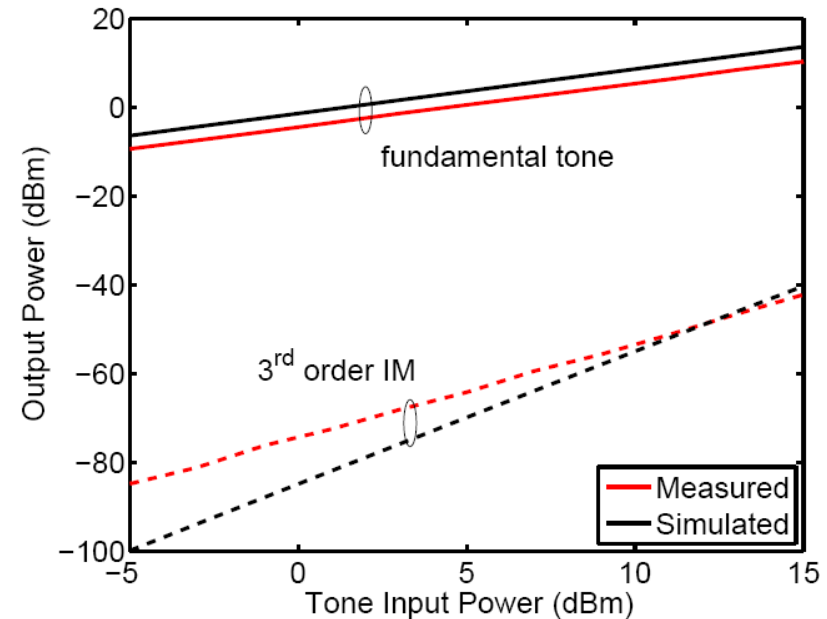




- Two-tone test @ 1.95GHz with $\Delta f=5\text{MHz}$ and Bias=5V
- OIP3=36.5dBm




Tunable Wilkinson Divider (1)

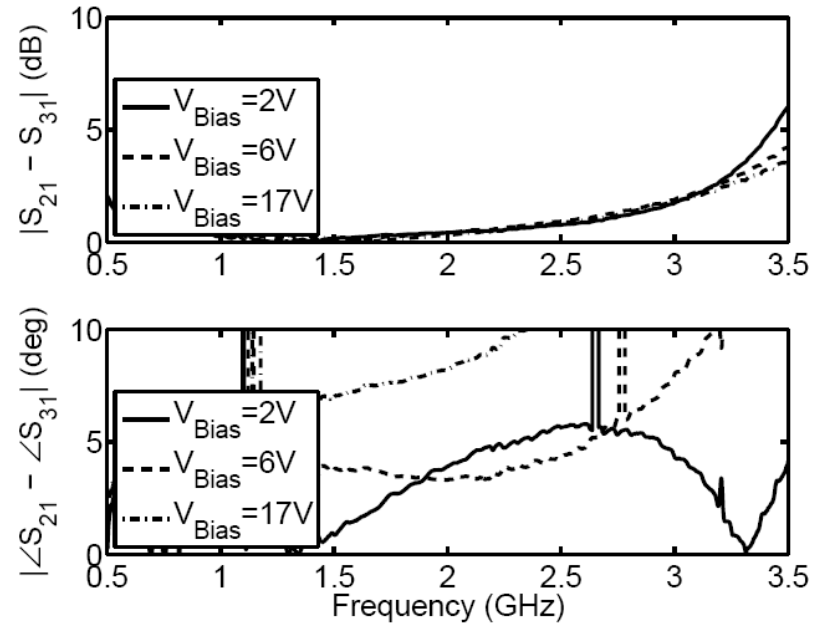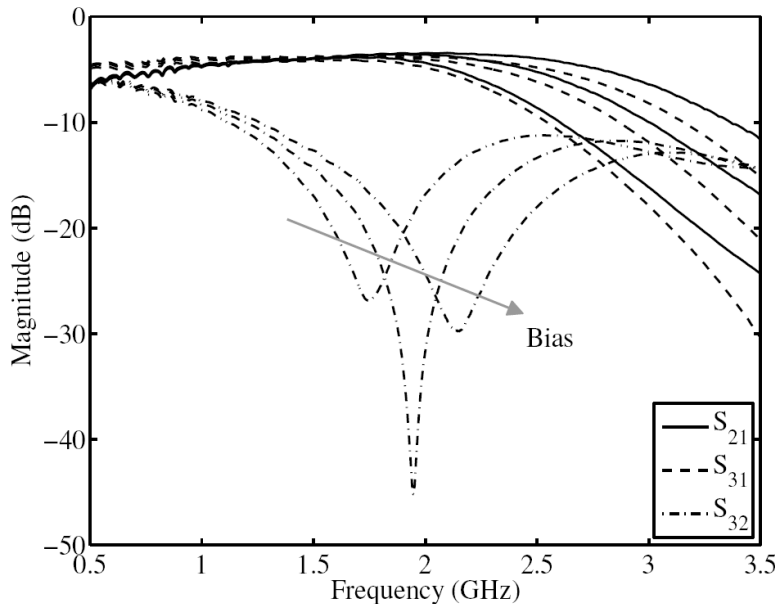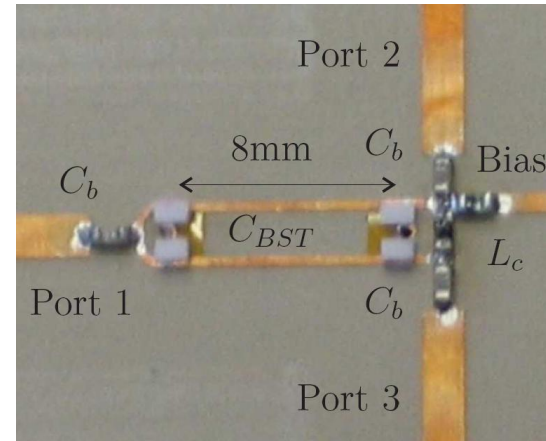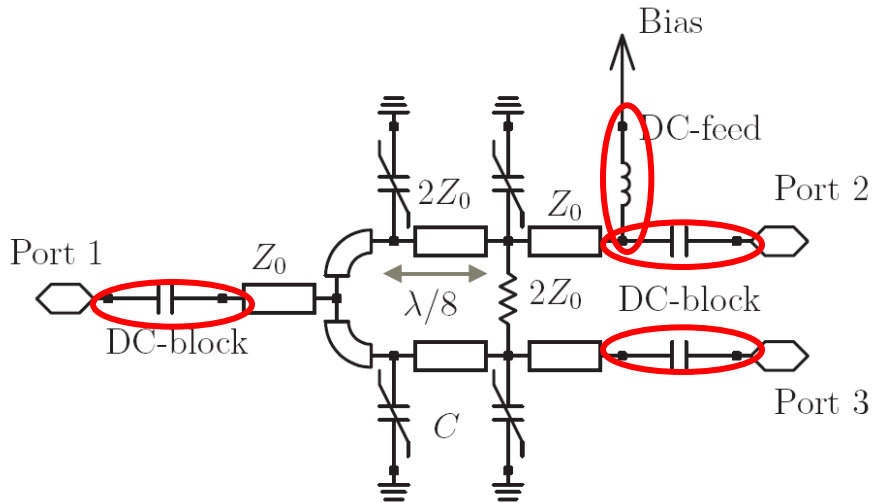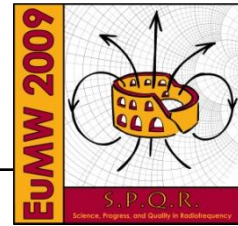





Tunable Wilkinson Divider (2)

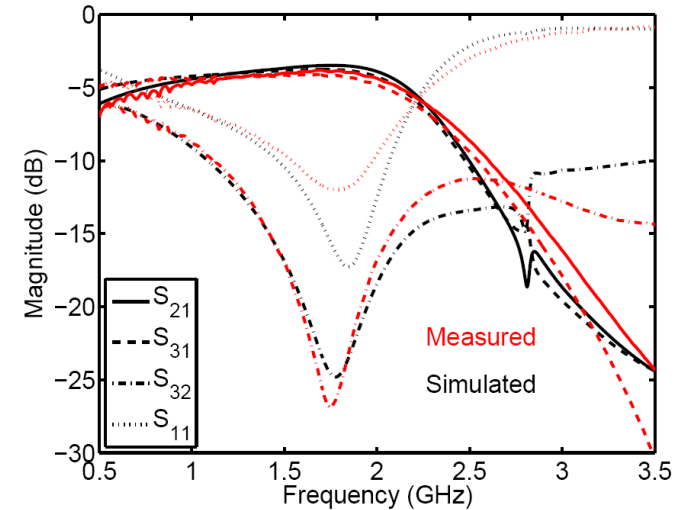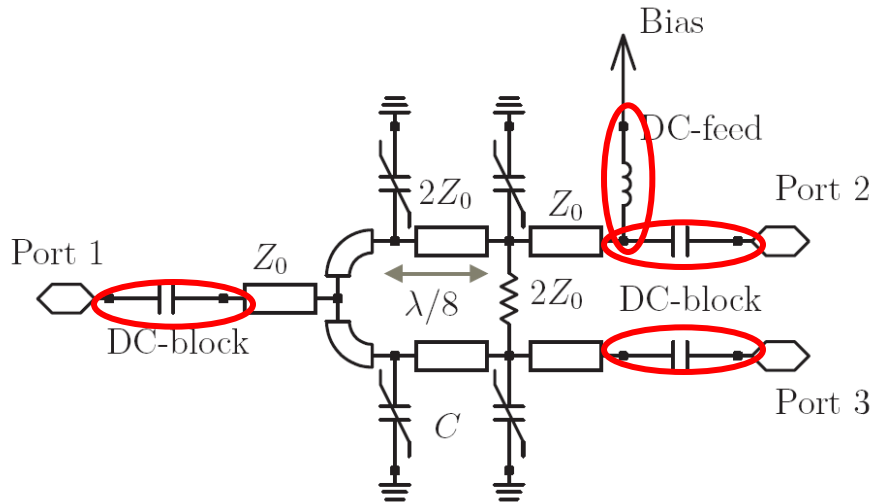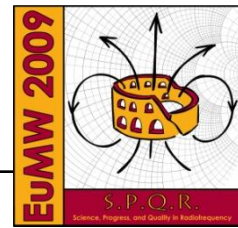

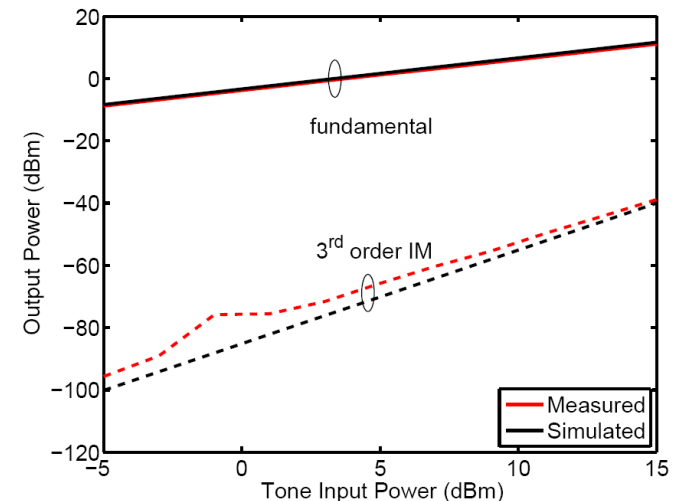- $IL < 1.2\text{dB}$, Isolation $> 25\text{dB}$
- Lowpass filtering S_{21}, S_{31}
- Attenuation $> 20\text{dB}$ at $2f_0$
- Tuning range 1.7-2.1GHz









Tunable Branch-Line (1)

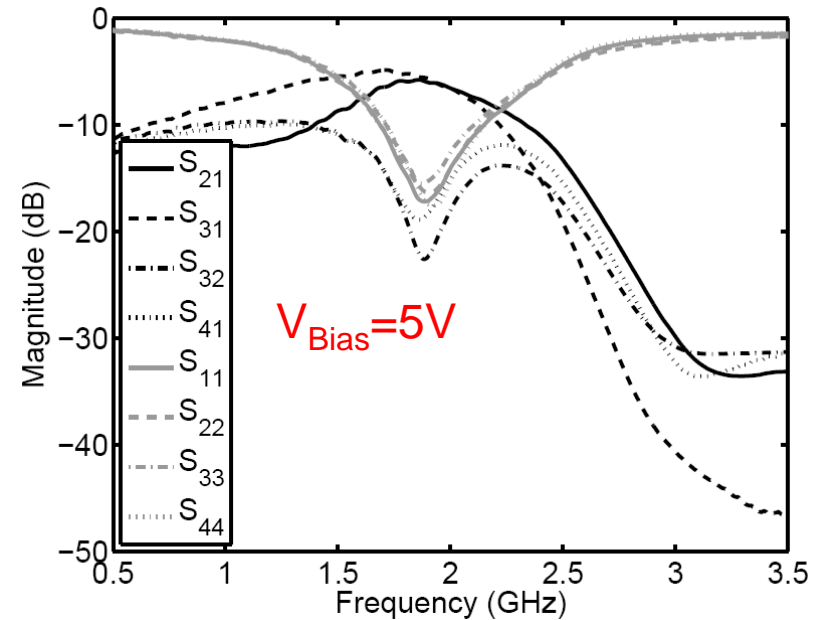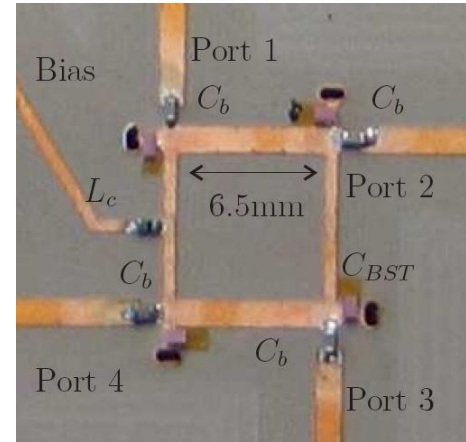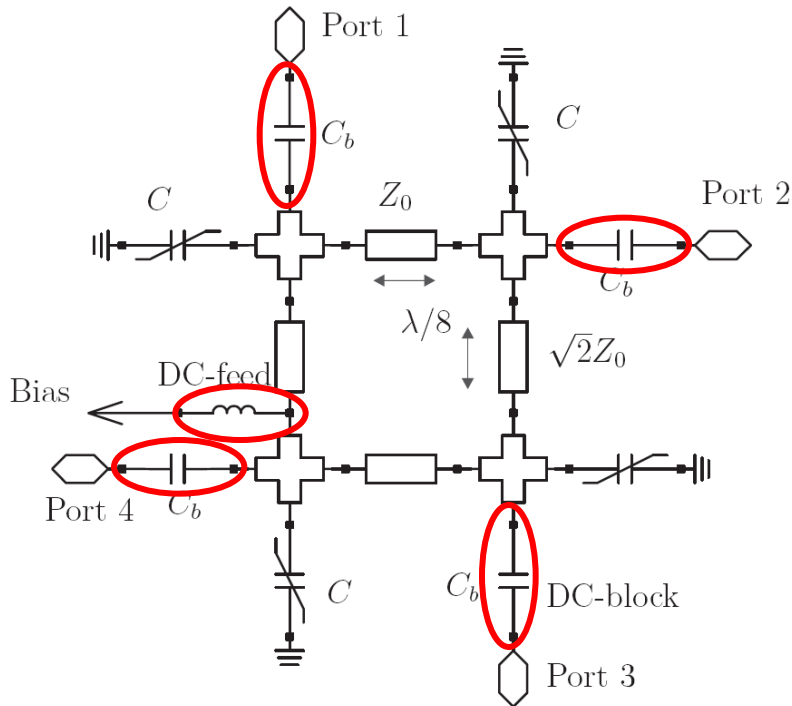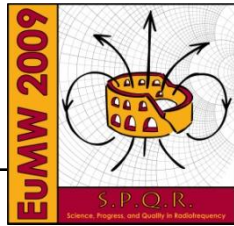




- Size reduction 50%
- Lowpass filtering
- Attenuation > 30dB at second harmonic



Tunable Branch-Line (2)

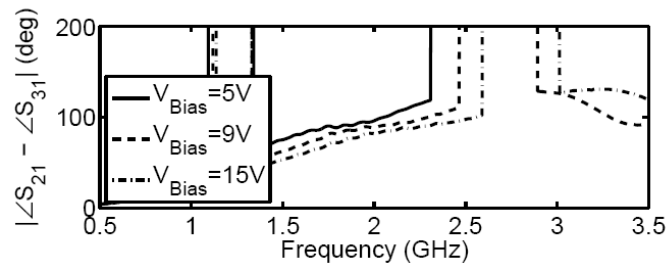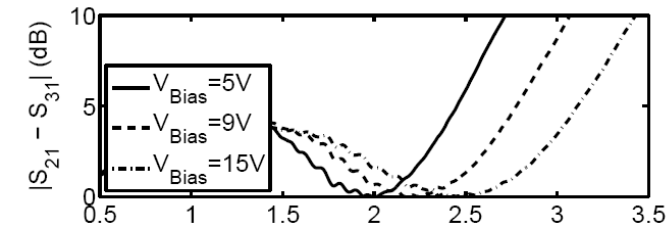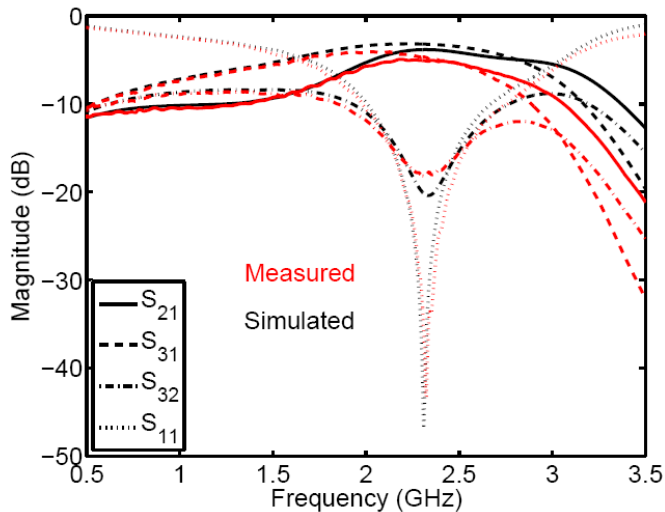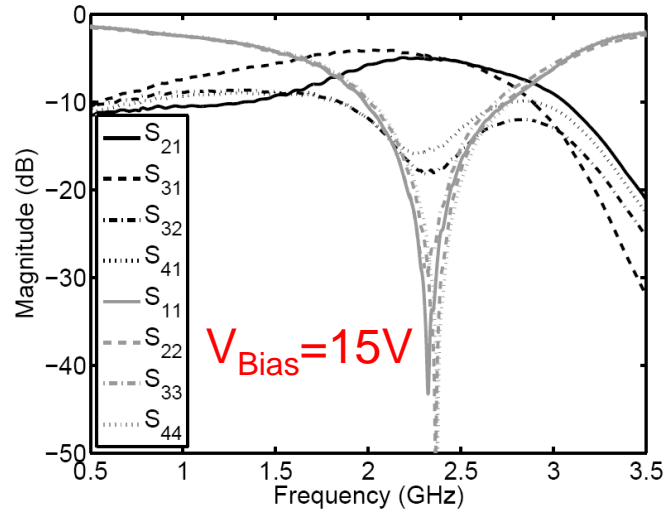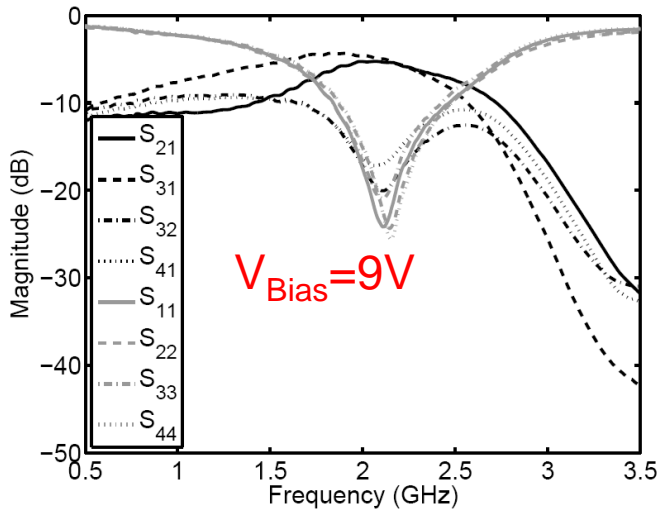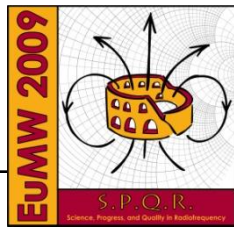


Tunable Branch-Line (3)

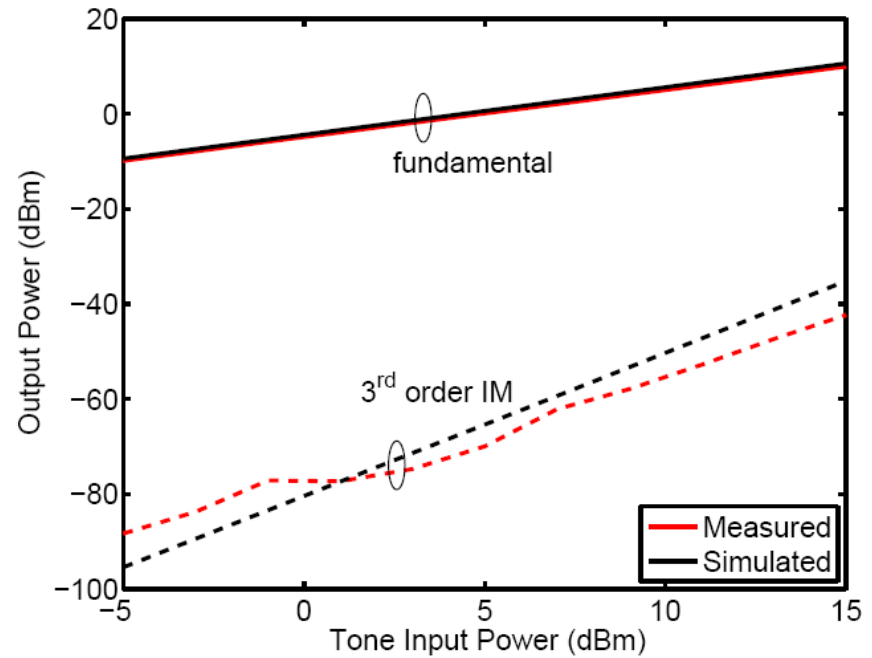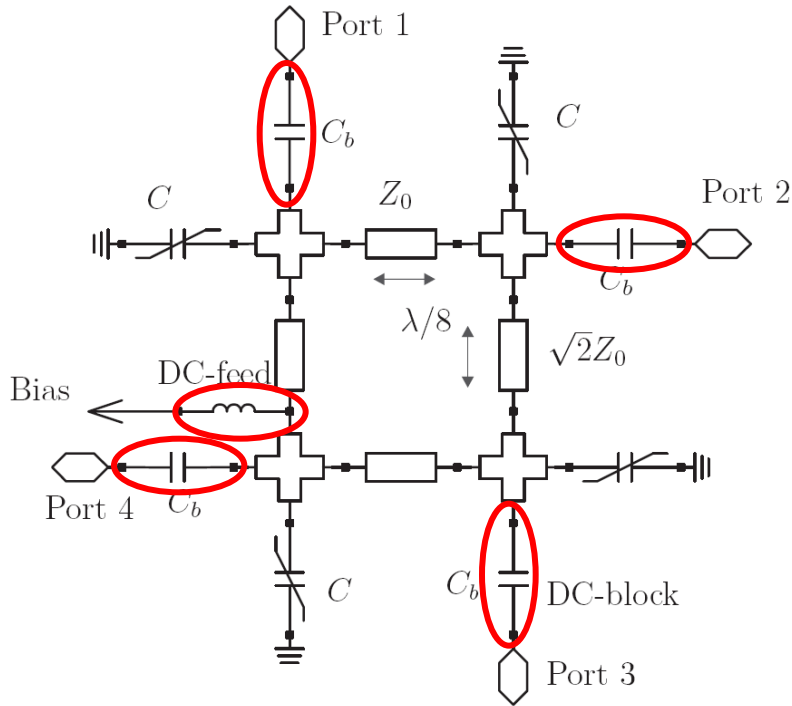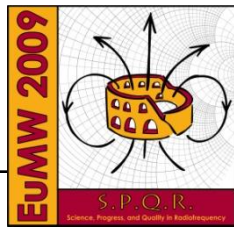

- Tuning range 1.8-2.3GHz
- IL < 2.7dB, RL > 15dB
- Amplitude error < 0.4dB, phase error < 5deg





Part 2 – Impedance Matching

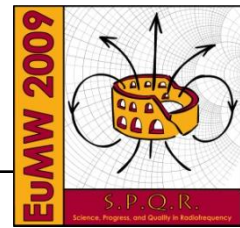



- Motivation - Mismatch Conditions
- L Matching Network
- Pi Matching Network
- T Matching Network
- Reflection Type Matching Network

Mismatch Conditions

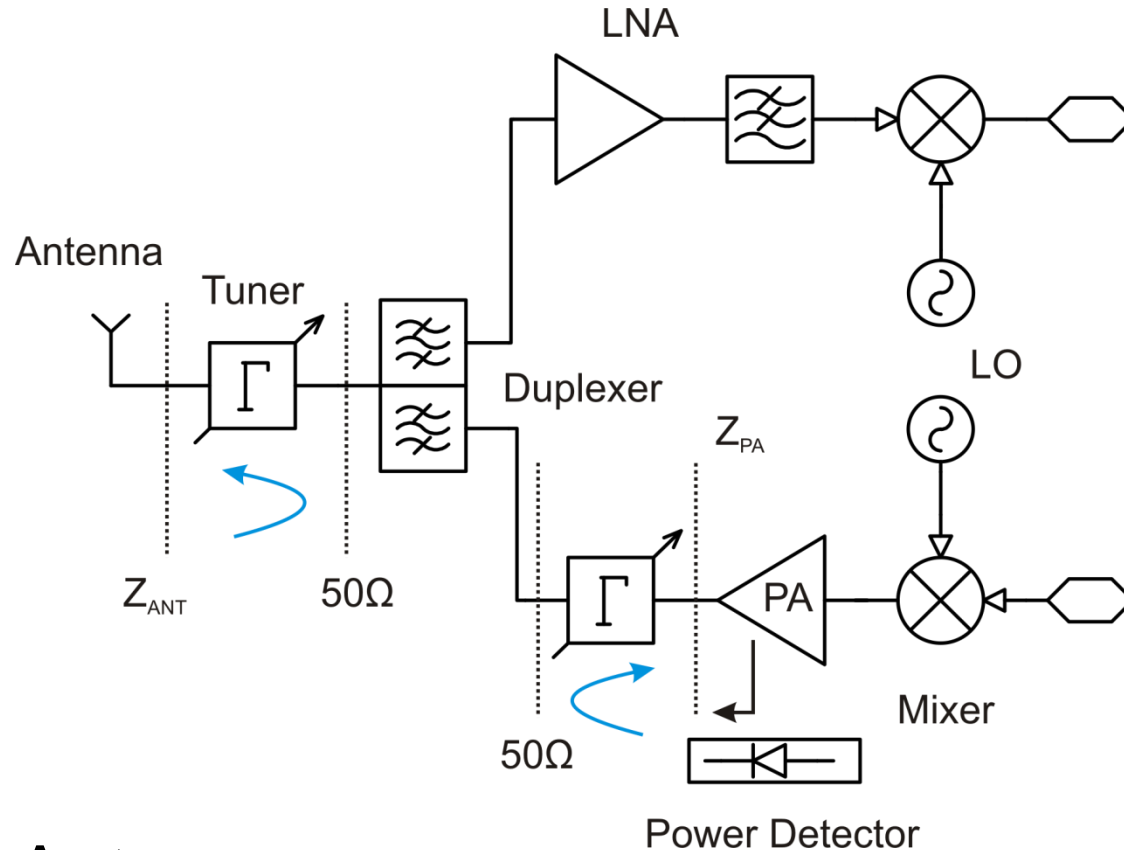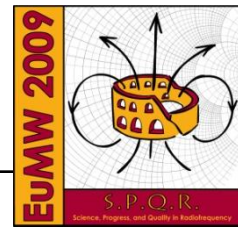


- Antenna
- Power amplifier


L - Matching Network

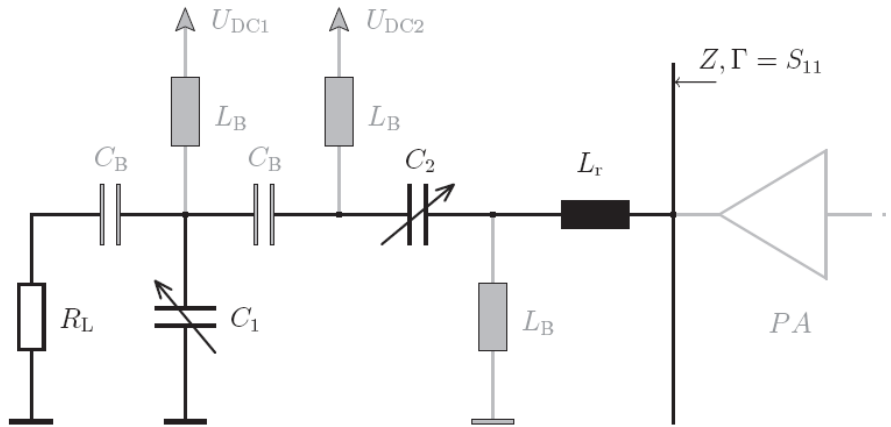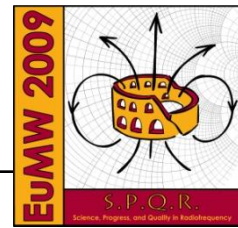

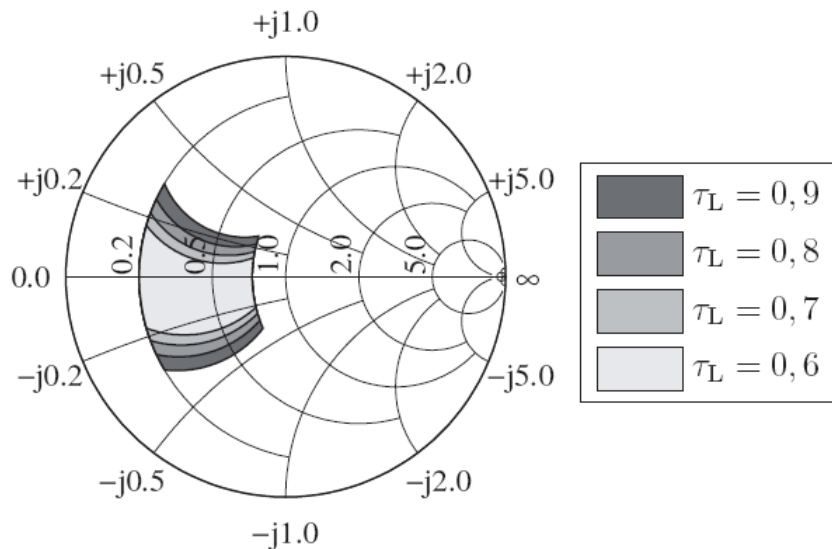- PA Matching
- Tunable L is series LC
- Small matching area




L - Network Gain

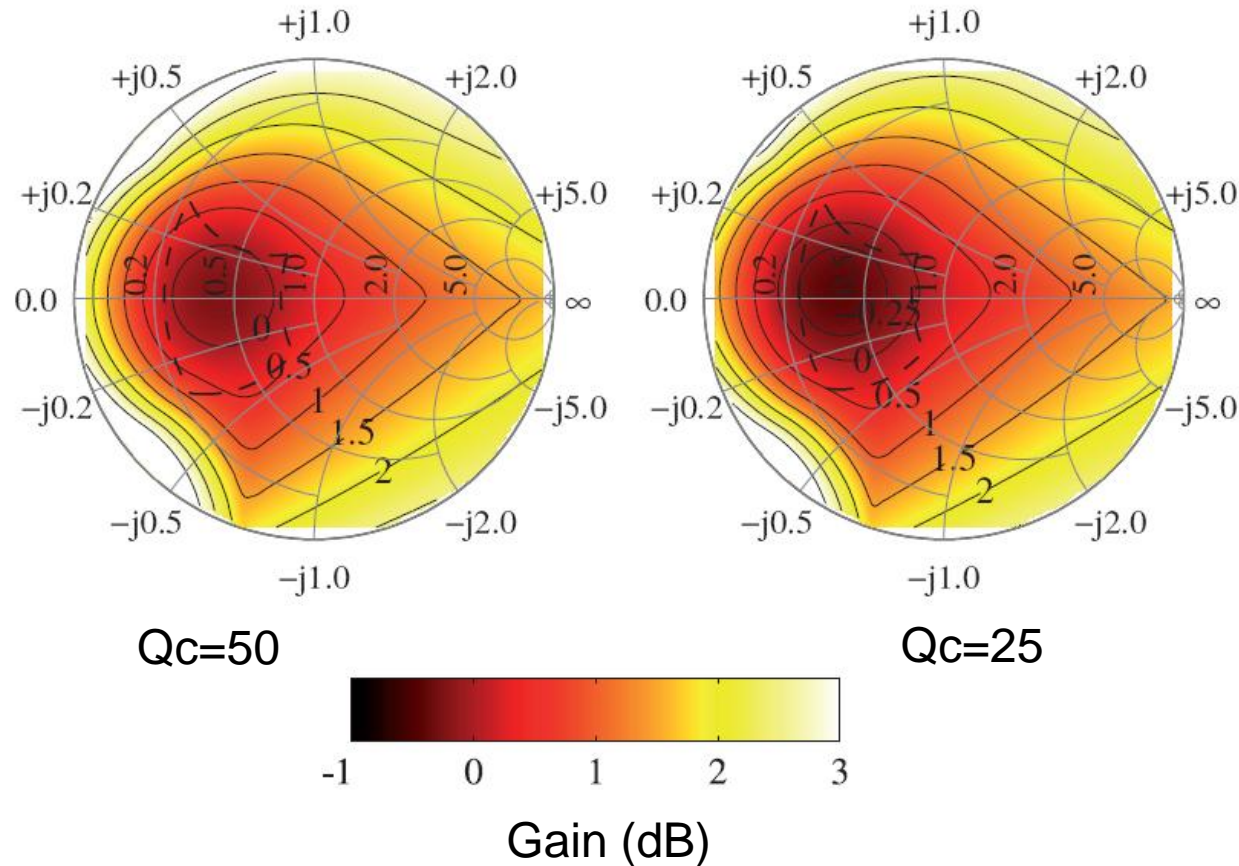


- Fixed MN with $Z_{in}=25\Omega$ SMD 0402 components
- Losses for minor impedance variations


L - Matching Area

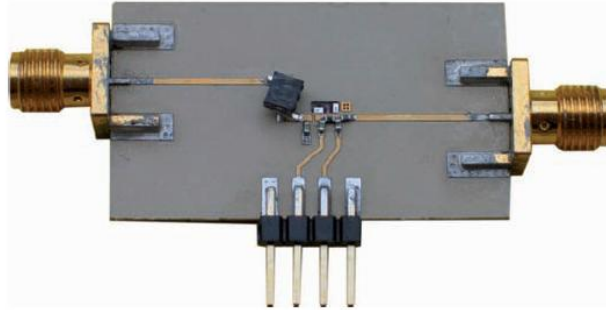


Bias

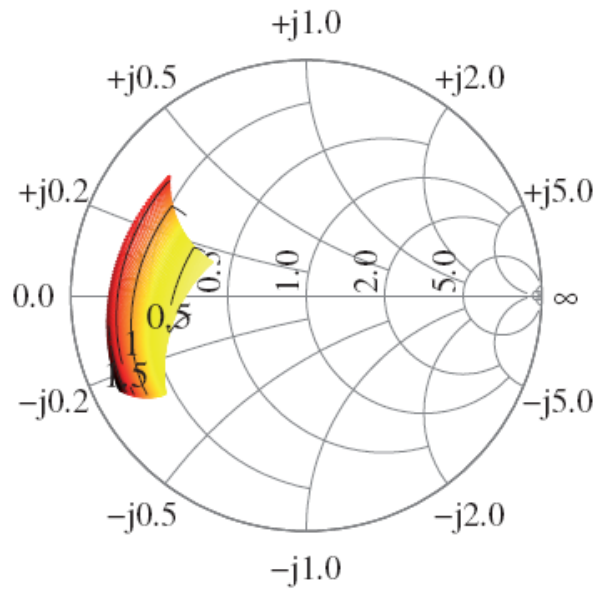

Simulated



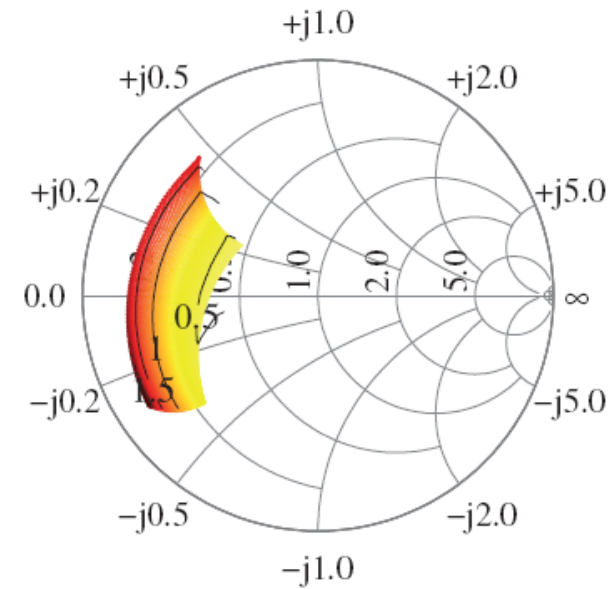


Measured

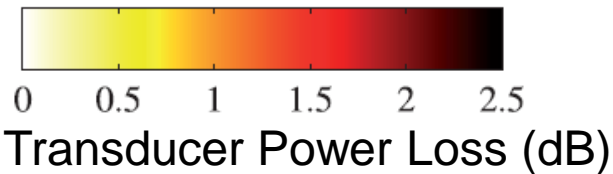


- Excellent agreement
- Dynamically adjustable PA impedance

Π - Matching Network

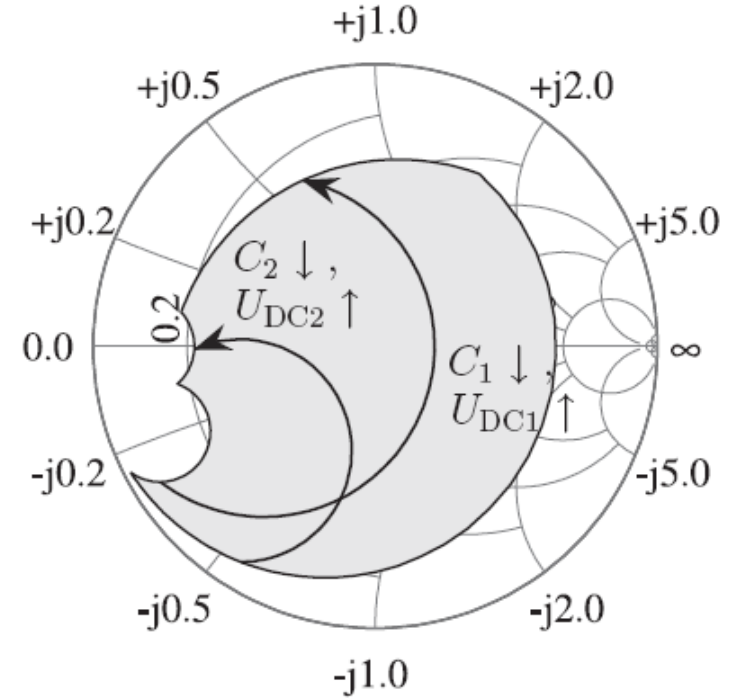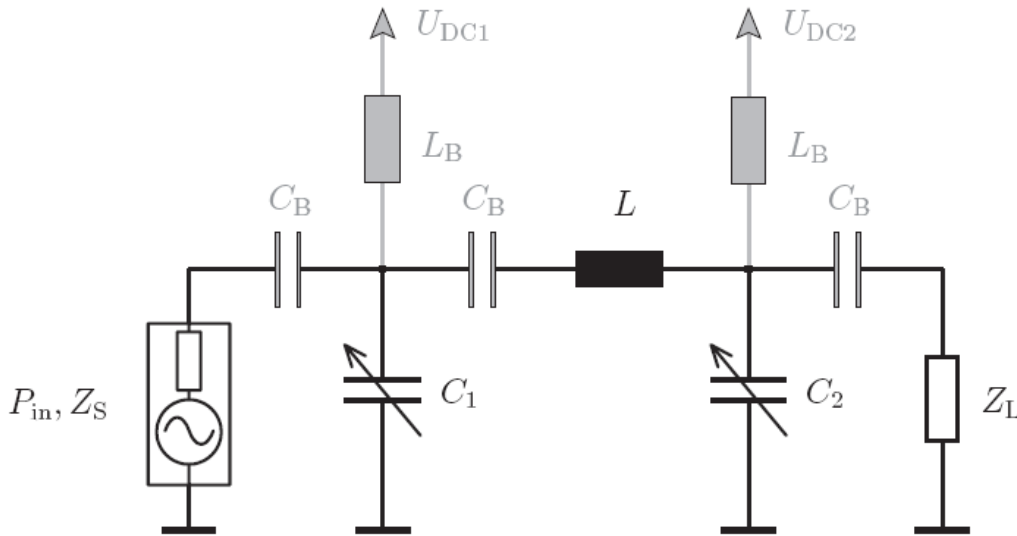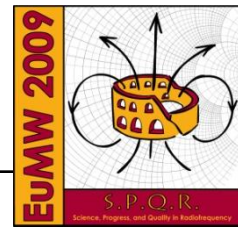


- High C value
- Suitable for low impedances
- Low IMD

Π – Network Gain

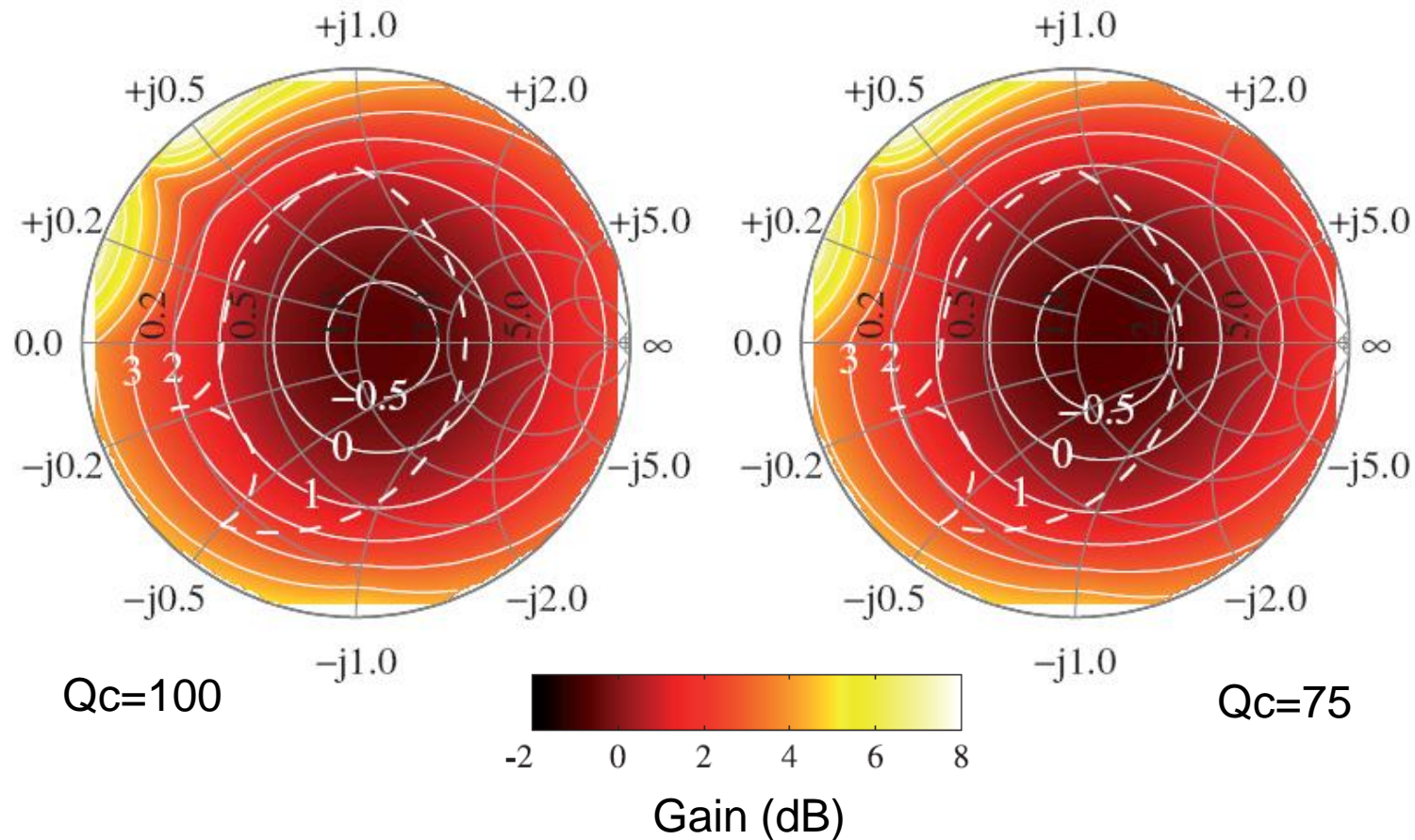


- Gain for significant impedance variations

Π – Matching Area

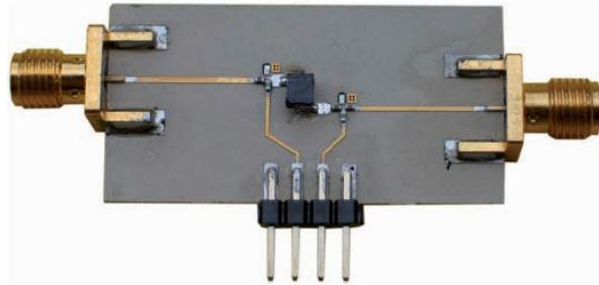



Bias

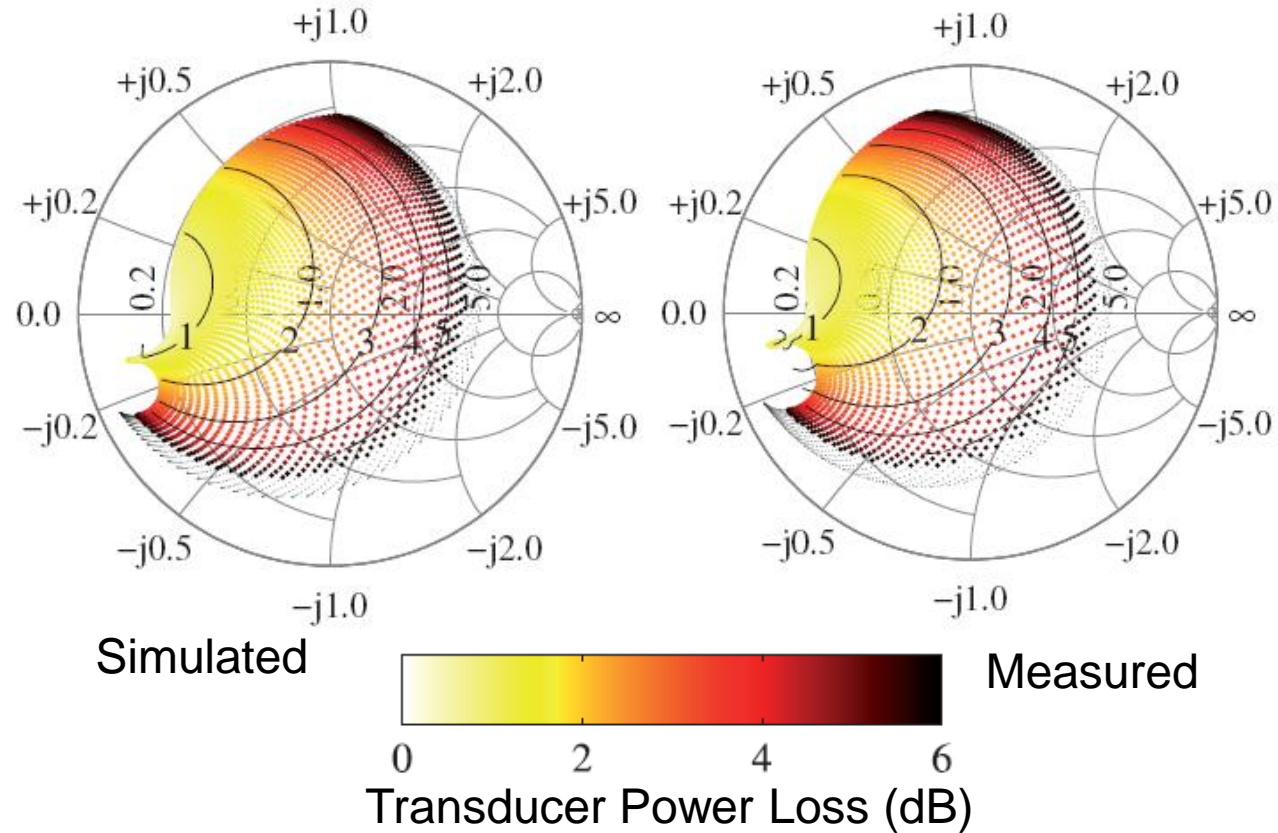


- Excellent agreement
- Losses increase for higher impedances



Assembly Parasitics

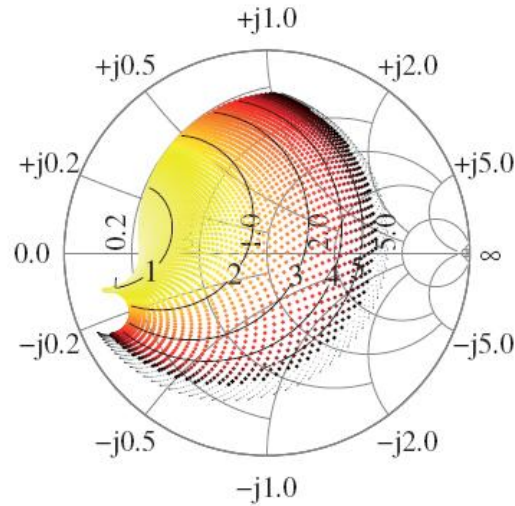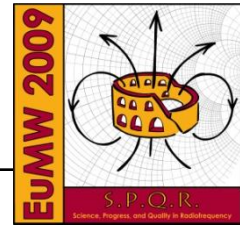


Simulated with bond wires

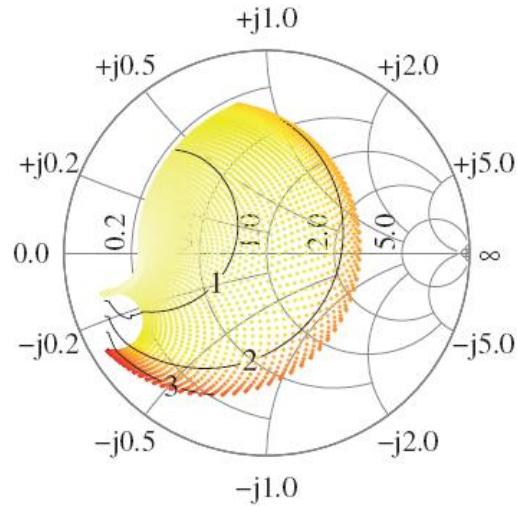




Simulated without bond wires

Measured

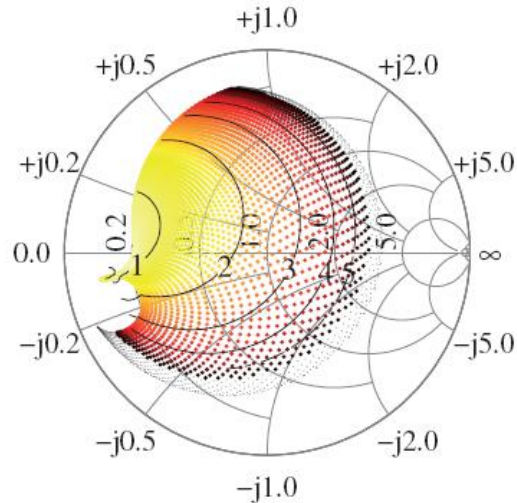


Transducer Power Loss (dB)

T – Matching Network

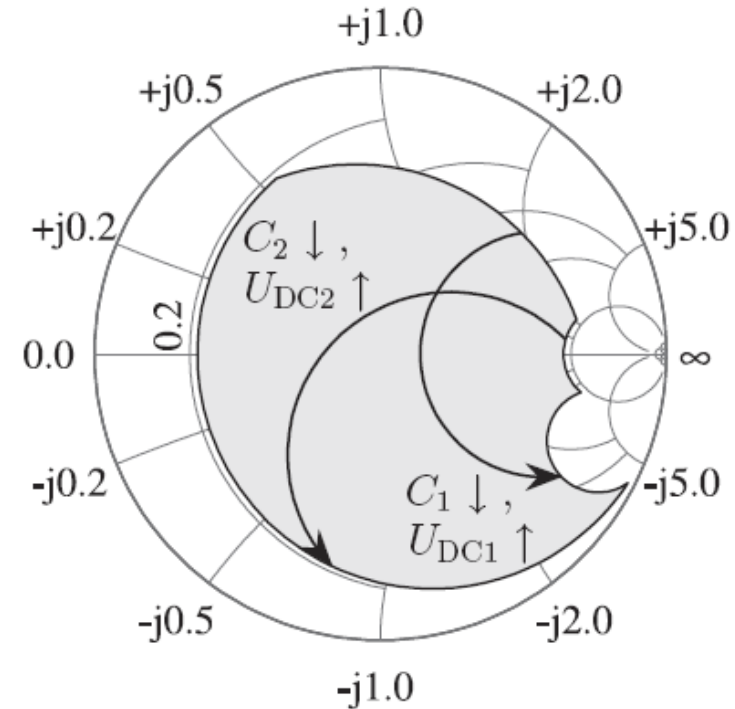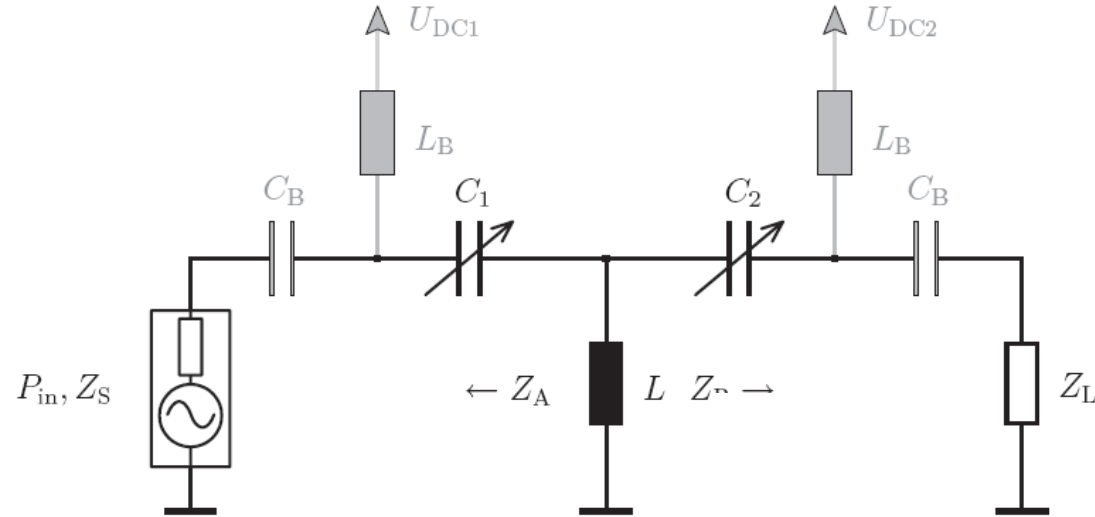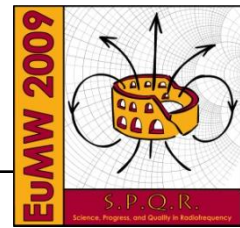


- Low C values
- Suitable for high impedances
- High IMD

T – Network Gain

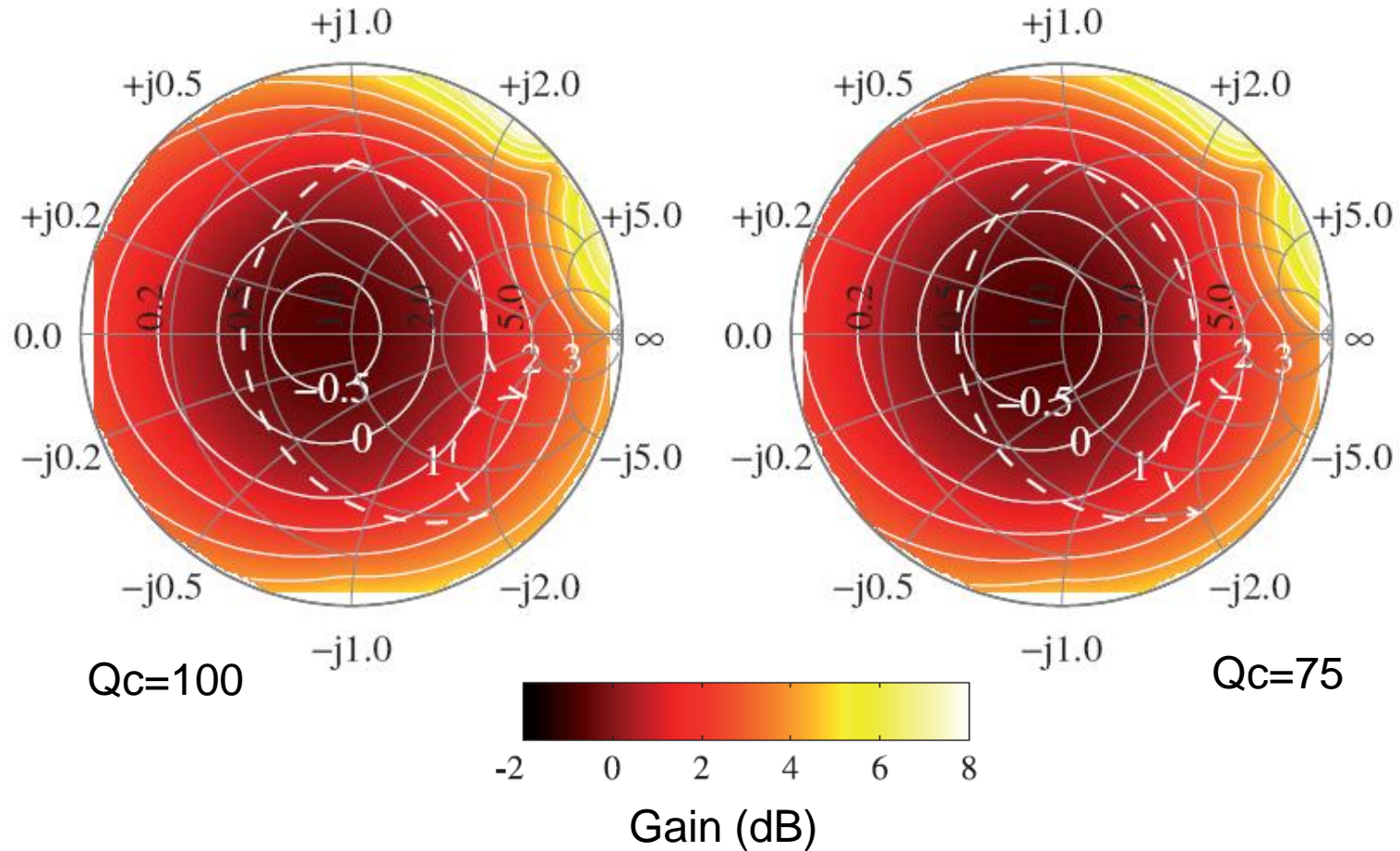


- Gain for significant impedance variation

T – Matching Area

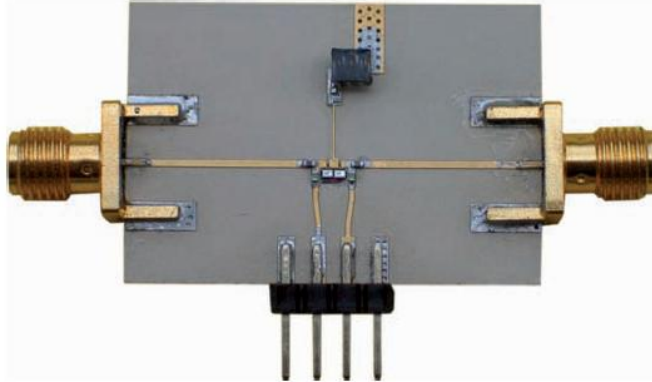


Bias

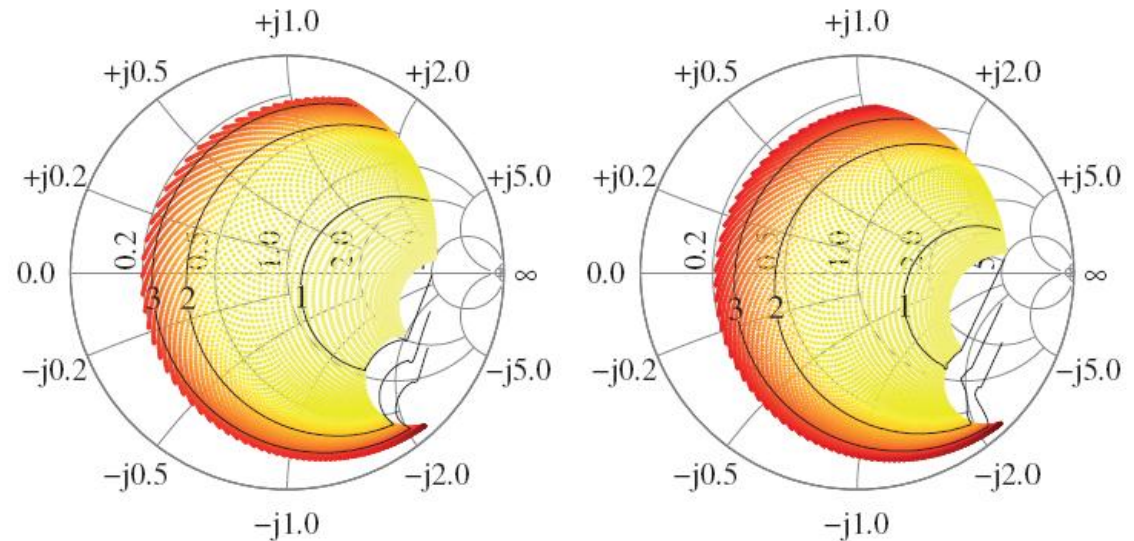



Simulated

Measured

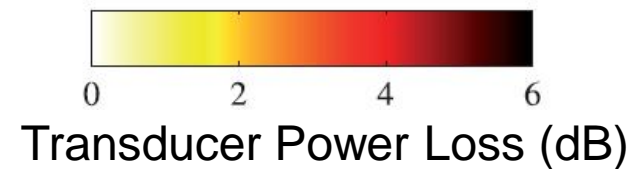




- Excellent agreement
- Higher losses for low impedances

Reflection – Matching Network

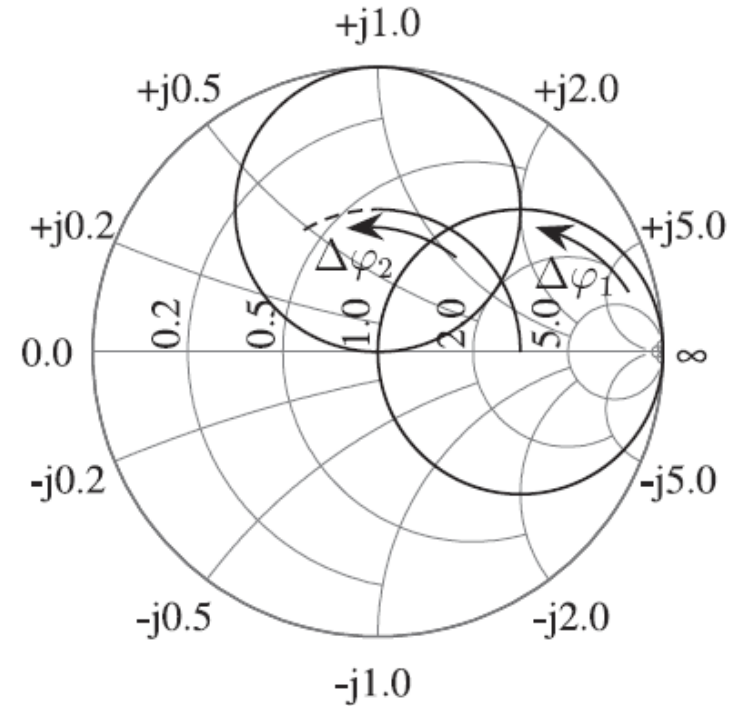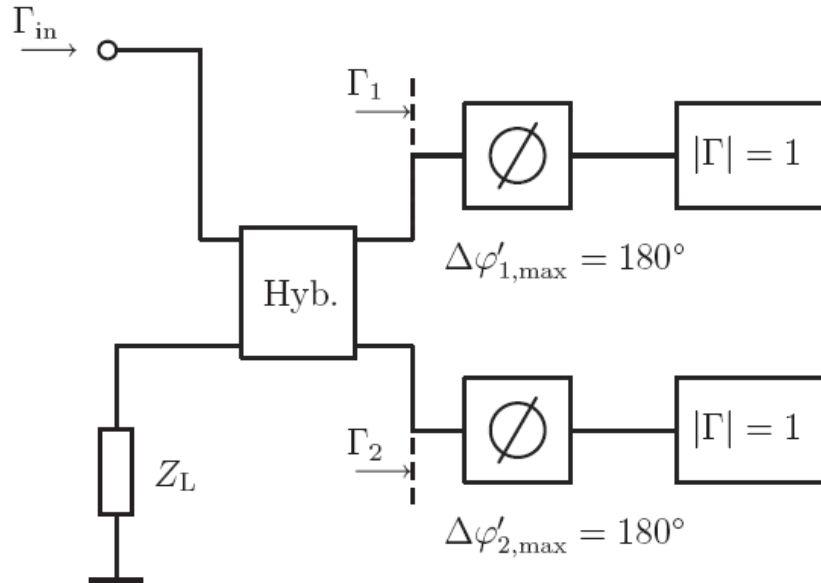



- Total Smith chart area coverage
- Hybrid coupler and phase shifters
- Large circuit dimension

Reflection Type Circuit

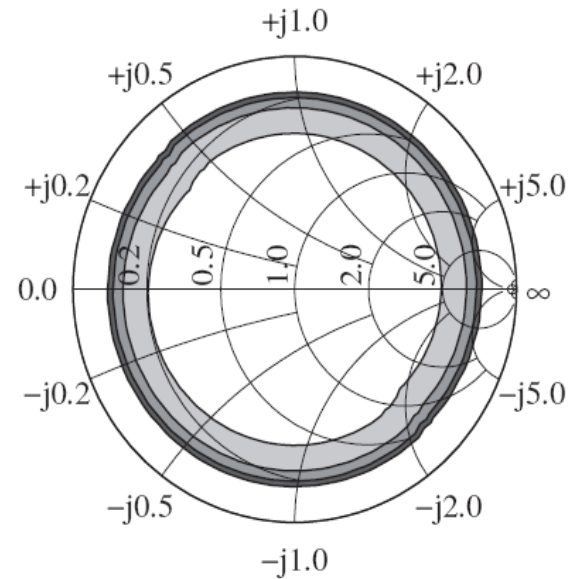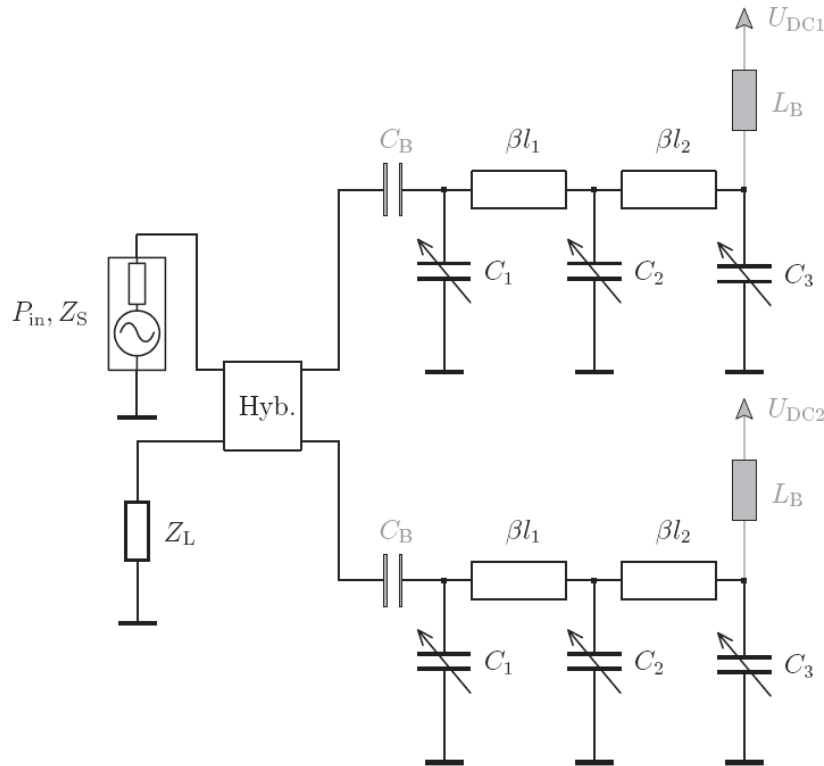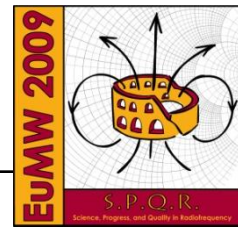


- High Q values for varactors lead to large matching area

Reflection – Network Gain

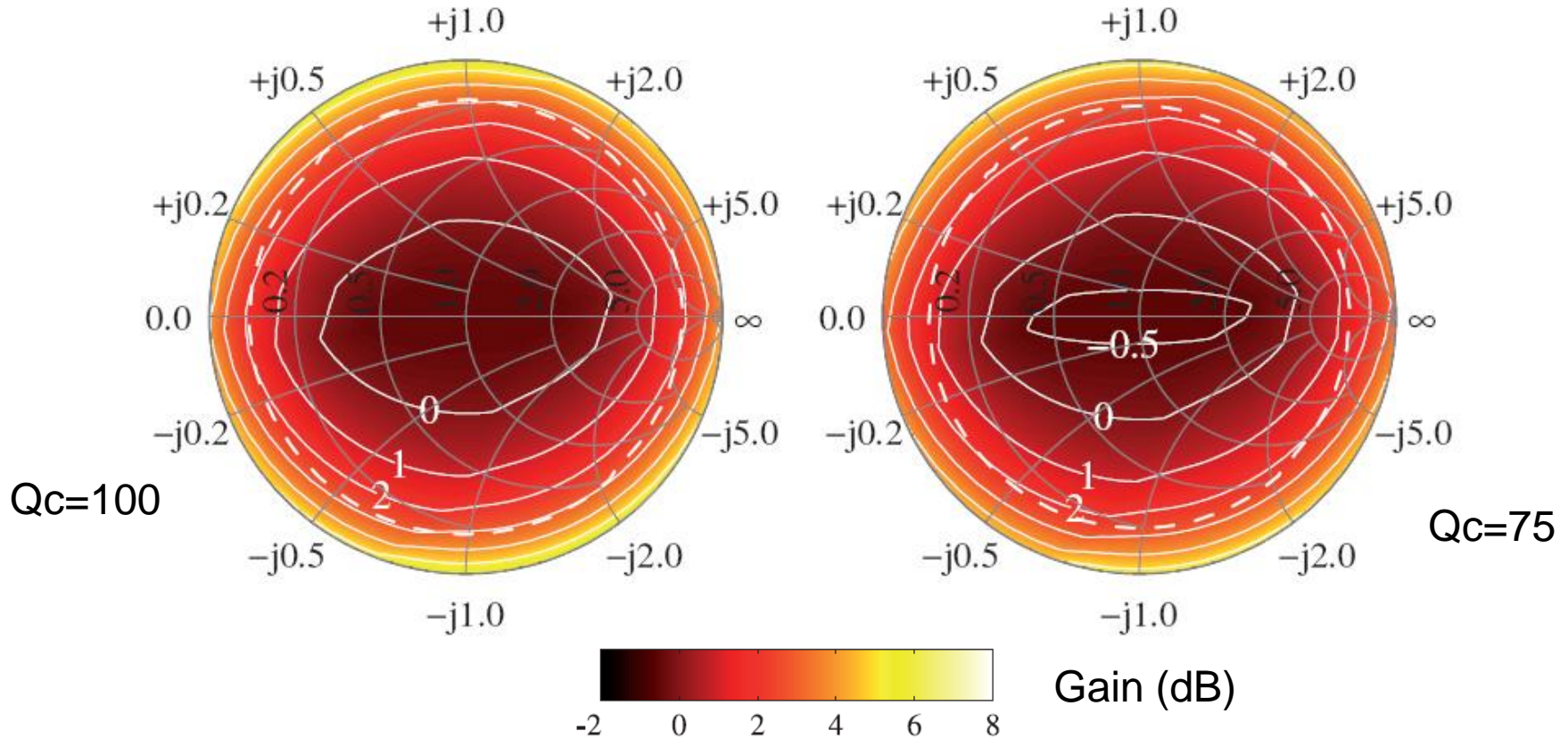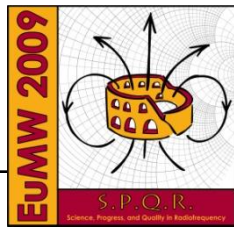


- Gain for significant impedance variation


Reflection – Matching Area

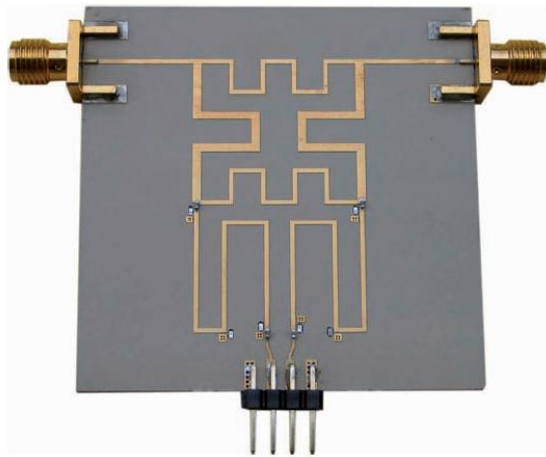

Bias

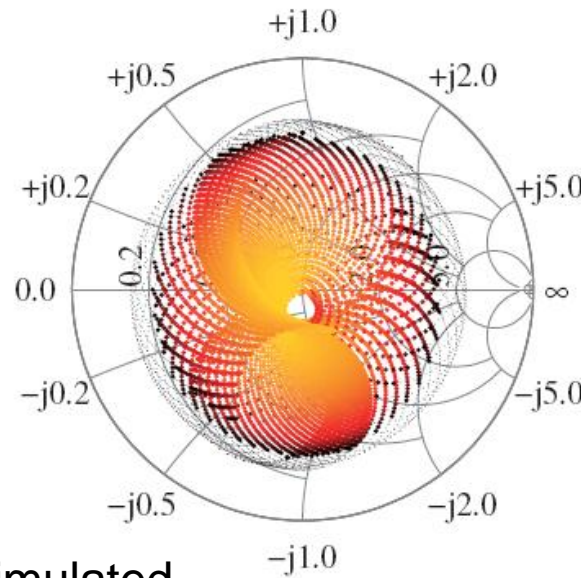

Simulated

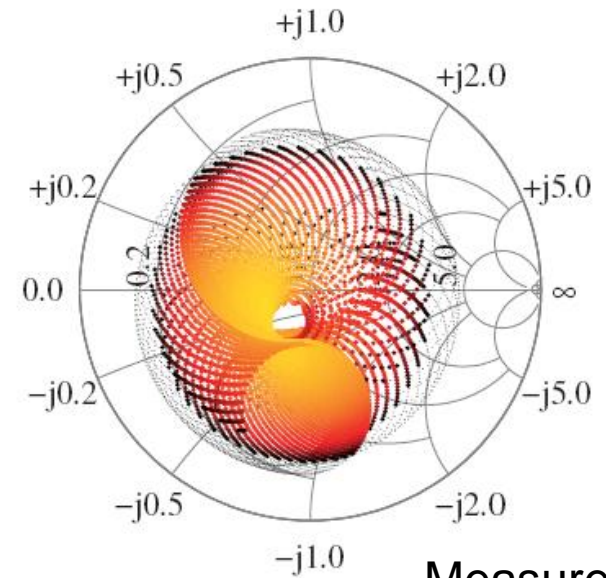

Measured




Transducer Power Loss (dB)

- Excellent agreement
- Symmetric matching area



Conclusion

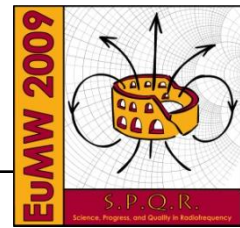

Conclusion

- Potential of ferroelectrics in tunable front-end
- Tunable microwave circuits
- Prototype implementation & results

Outlook

- Integration of tunable microwave subsystems in front-end architectures